
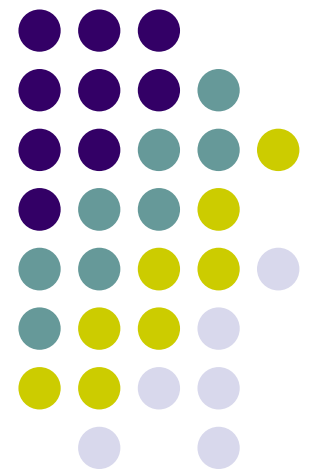


Digital Logic

 
From Boolean algebra to
implementing logic circuits





Outline

 
- Boolean algebra
- Logic gates
- Truth table
- Logic expressions
- Implementing digital logic using gates
- Karnaugh map – logic minimization
- Using NAND, NOR gates only.
- Binary numbers
- ADC – Analog to digital conversion



Logic circuits


- Boolean variables
 - Can have values of either TRUE (1), FALSE(0)
 - Can represent
 - either truth or falsehood of a statement
 - ON or OFF states of a switch
 - High(5V) or low(0V) of a voltage level

Logic operation

 

AND ($x.y$)			OR($x+y$)			NOT(x)	
x	y	$x.y$	x	y	$x+y$	x	\bar{x}
0	0	0	0	0	0	0	1
0	1	0	0	1	1	1	0
1	0	0	1	0	1		
1	1	1	1	1	1		

Basic laws of Boolean Algebra

 

$$0 + A = A$$

$$1 + A = 1$$


$$A + A = A$$

$$A + \overline{A} = 1$$

$$0.A = 0$$

$$1.A = A$$

Basic laws of Boolean Algebra

 

$$A.A = A$$


$$A.\overline{A} = 0$$

$$A = \overline{\overline{A}}$$

$$A + B = B + A$$

$$A.B = B.A$$

Basic laws of Boolean Algebra

 

$$A + (B + C) = (A + B) + C$$

$$(A.B).C = A.(B.C)$$


$$A.(B + C) = A.B + A.C$$

$$A + A.B = A$$

$$A.(A + B) = A$$


$$(A + B).(A + C) = A + B.C$$

$$A + \overline{A}.B = A + B$$

 


Logic Gates

 
- Electronic circuits used to perform boolean logic operations are known as logic gates.





AND

 



NOT

 

OR

  


NAND

  


NOR

DeMorgan's Theorem

 



$\overline{A+B} = \bar{A}.\bar{B}$ → Inverting a sum results in
 $\overline{A.B} = \bar{A} + \bar{B}$ product of inverted signals.
 
$$\text{NOR} : \overline{A+B} = \bar{A}.\bar{B}$$


 
$$\text{NAND} \quad \overline{A.B} = \bar{A} + \bar{B}$$



 


Universality of NAND gates


- AND, OR, NOT gates can be obtained from NAND gate


$$A \text{ --- } \boxed{\text{NAND}} \text{ --- } \bar{A} \quad \approx \quad \overline{A \cdot A} = \bar{A}$$
 
$$A \cdot B = \overline{\overline{A \cdot B}}$$


 
$$A + B = \overline{\overline{A + B}} = \overline{\bar{A} \cdot \bar{B}}$$



 

Universality of OR gates


- AND, OR, NOT gates can be obtained from NOR gate

$$\overline{A + A} = \bar{A} \quad \text{as} \quad A + A = A; \quad \begin{array}{c} A \\ \text{---} \end{array} \begin{array}{c} \diagup \\ \diagdown \end{array} \begin{array}{c} \diagdown \\ \diagup \end{array} \begin{array}{c} \text{---} \end{array} \bar{A}$$

$$A \cdot B = \overline{\overline{A \cdot B}} = \overline{\bar{A} + \bar{B}}; \quad \begin{array}{c} A \\ \text{---} \end{array} \begin{array}{c} \diagup \\ \diagdown \end{array} \begin{array}{c} \diagdown \\ \diagup \end{array} \begin{array}{c} \text{---} \end{array} \begin{array}{c} \diagup \\ \diagdown \end{array} \begin{array}{c} \diagdown \\ \diagup \end{array} \begin{array}{c} \text{---} \end{array} \begin{array}{c} \diagup \\ \diagdown \end{array} \begin{array}{c} \diagdown \\ \diagup \end{array} \begin{array}{c} \text{---} \end{array} A \cdot B$$

$$A + B = \overline{\overline{A + B}}; \quad \begin{array}{c} A \\ \text{---} \end{array} \begin{array}{c} \diagup \\ \diagdown \end{array} \begin{array}{c} \diagdown \\ \diagup \end{array} \begin{array}{c} \text{---} \end{array} \begin{array}{c} \diagup \\ \diagdown \end{array} \begin{array}{c} \diagdown \\ \diagup \end{array} \begin{array}{c} \text{---} \end{array} A + B$$


Truth table and logic expression

 

- Consider a logic circuit having two inputs A, B and one output C.
- The output becomes 1 when only one input is TRUE (1), but is FALSE(0) other wise.

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

TRUTH table

 

PRODUCT terms

- For each row in the Truth table, with '1' at the output column, we can create a PRODUCT term of all inputs.
 - Take the input, if the entry for it is 1
 - Take the input with a bar, if the entry for it is 0
- The logic expression will be SUM of these PRODUCTs (SOP)

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

$$\begin{array}{l} \bar{A}B \\ A\bar{B} \end{array}$$

$$C = \bar{A}B + A\bar{B}$$



SUM terms

- For each row in the Truth table, with '0' at the output column, we can create a SUM term of all inputs.
 - Take the input, if the entry for it is 0
 - Take the input with a bar, if the entry for it is 1
- The logic expression will be PRODUCT of SUMs (POS).

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

→ $(A + B)$


→ $(\bar{A} + \bar{B})$

$$C = (A + B) \cdot (\bar{A} + \bar{B})$$


Exclusive OR




A	B	$C = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

 
 
$$\begin{aligned} A \oplus B &= \bar{A}B + A\bar{B} \\ &= (A + B) \cdot (\bar{A} + \bar{B}) \end{aligned}$$



Truth table – Logic expressions

 

$$(A + B + C)$$

$$(A + \bar{B} + \bar{C})$$

$$(\bar{A} + \bar{B} + C)$$

$$(\bar{A} + \bar{B} + \bar{C})$$

A	B	C	W
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$\bar{A} \cdot \bar{B} \cdot C$$

$$\bar{A} \cdot B \cdot \bar{C}$$

$$A \cdot \bar{B} \cdot \bar{C}$$


$$A \cdot \bar{B} \cdot C$$

Sum of Products (SOP)

$$W = \bar{A} \cdot \bar{B} \cdot C + \bar{A} \cdot B \cdot \bar{C} + A \cdot \bar{B} \cdot \bar{C} + A \cdot \bar{B} \cdot C$$

Product of Sums (POS)

 
$$W = (A + B + C) \cdot (A + \bar{B} + \bar{C}) \cdot (\bar{A} + \bar{B} + C) \cdot (\bar{A} + \bar{B} + \bar{C})$$



Example – sop, pos

①


A	B	W
0	0	1
0	1	0
1	0	1
1	1	1

 

SOP for W?
POS


②

X	Y	Z	P
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 


SOP for P?
POS

 Design logic circuits: Implementing logic expressions




 - Logic expressions are in either Sum of Product (SOP) or Product of Sums (POS) form
- Implement the sum term using OR gates and product term using AND gates
- Hence, using AND, OR and NOT gates we can implement any logic expressions




Implementing sop and pos

 
$$\textcircled{1} \quad W = A \cdot \bar{B} + \bar{A} \cdot \bar{B}$$



 
$$\textcircled{2} \quad Z = (A + B) \cdot (\bar{A} + B)$$



 Design logic circuits: Implementing logic expressions




 - As designer, our aim will be to use minimum number of gates.
- We need to minimize the SOP and POS expressions.
- There are two ways for this:
 - Boolean algebra laws
 - Graphical method – Karnaugh map




Karnaugh Maps

 - It is a graphical representation of the truth table – each row in truth table corresponds to one cell in the K-map.
- The adjacent (horizontal or vertical) cells have only one variable changing from 0 to 1 or vice versa.



Truth table to K-map


more examples

 

A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

AB		00	01	11	10
0	0	0	0	0	1
1	0	0	1	0	1

BC		0	1
00	0	0	1
01	0	0	1
11	1	0	0
10	0	0	0

 

Grouping adjacent cells


- Group adjacent cells containing same values
- Group in powers of 2 (2^n) i.e. in 2, 4, 8 etc.
- The bigger the group smaller the term – a group with 2^n terms has n terms less

AB		00	01	11	10
CD	00	0	1	1	0
	01	0	0	0	0
	11	1	1	1	1
	10	0	0	0	0


CD

$$\begin{aligned}\bar{A}B\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} &= \\ &= (\bar{A} + A)B\bar{C}\bar{D} \\ &= 1 \cdot B\bar{C}\bar{D} = B\bar{C}\bar{D}\end{aligned}$$

Variables with both 0 and 1 go.

 

Adjacent cells

 

Leftmost column $AB = 00$

Rightmost column $AB = 10$

As only A changes from 0 to 1; the left most column and right most column are adjacent


column are adjacent

* Topmost row and bottom most row are also adjacent.


* The four corners can be grouped together

$$MSOP = B \cdot D + \bar{B} \cdot \bar{D}, \quad MPOS = (\bar{B} + D) \cdot (B + \bar{D})$$

K-Map for minimizing

 


A	B	C	W
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

 


- * Try to form as big a group as possible
- * One cell can be part of more than one group if necessary.

 
Logic design using only NAND or only NOR gates




- NAND, NOR gates are universal gates
- The AND, OR, NOT can be converted into NAND/NOR gates


NOT can be made of NAND gate

 

 
$A \cdot B = \overline{\overline{A \cdot B}}$ \Rightarrow  can be replaced by



 
$A + B = \overline{\overline{A + B}} = \overline{\overline{A} \cdot \overline{B}}$ \Rightarrow  can be replaced by




Alternate NAND NOR symbols

 

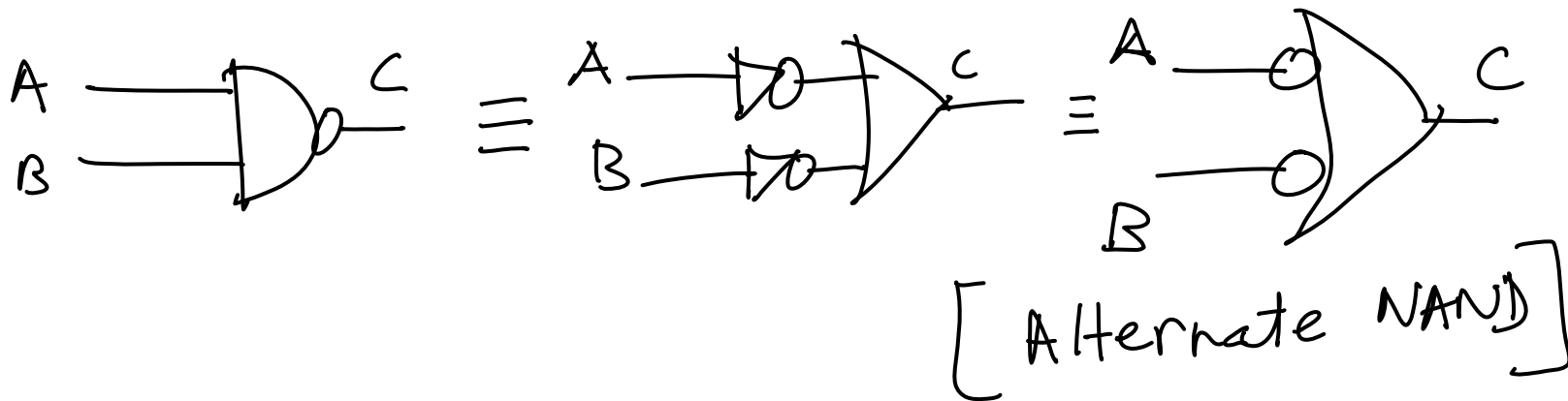
$$C = \overline{A \cdot B} = \overline{A} + \overline{B} \quad (\text{DeMorgan's law}).$$



 
$$D = \overline{A + B} = \overline{A} \cdot \overline{B} \quad (\text{DeMorgan's law})$$



 


From AND, OR , NOT to NAND only


$$Z = AB + \bar{A}$$

 

|||

 


 - For AND gate, put an inverter (bubble) at its output.
- For OR gate, put bubbles at the inputs.
- At any point, we can put two bubbles without changing anything.




From AND, OR , NOT to NOR only

$$Z = A B + \bar{A}$$

 


III

 

- For OR gate, put an inverter (bubble) at its output.
- For AND gate, put bubbles at the inputs.
- At any point, we can put two bubbles without changing anything.



- [illegible]

 


Convert decimal to binary

- Keep dividing the decimal number by 2 until you get 1. Arrange the remainders from right to left. Fill the remaining bits with 0.

eg. to convert 102 to 8 bit binary,


$$\begin{array}{r|l} 2 & 102 \\ \hline 2 & 61 \\ \hline 2 & 30 \\ \hline 2 & 15 \\ \hline 2 & 7 \\ \hline 2 & 3 \\ \hline & 1 \end{array} \quad \begin{array}{l} 0 - \text{LSB} \\ 1 \\ 0 \\ 1 \\ 1 \\ 1 \end{array} \Rightarrow \underline{01111010}^{\text{LSB}}$$

 


Examples – binary number find the decimal value and vice versa

- 00001111
- 10000000
- 11111111
- 00001000

Analog to Digital converter

 

 - An analog-to-digital converter (abbreviated ADC, A/D or A to D) is a device which converts continuous signals to discrete digital numbers. The reverse operation is performed by a digital-to-analog converter (DAC).



Example

- If 0V-5V are converted to an 8-bit digital
 - 0V = bin 00000000 (decimal 0);
 - 5V = bin 11111111 (decimal 255);
 - The range 0-5 is divided into 256 values, i.e each division is equal to $5/255$ V.
 - An input value of say 2.5V would be decimal 102 i.e bin 01100110
 - Analog 4.5V would be decimal $4.5/(5/255)=229$ i.e. bin 11100101

Relating to the microcontroller experiment (Sample program)



- Connected an analog voltage (0-5V) to the AN0 (channel 0) of the PIC's ADC port.
- Connect 8 LEDs (each with a 220ohm resistor in series) from pins RD0, RD1... to RD7 to GND.
- Vary the analog input voltage.
- Observe different LEDs light up as the input voltage is varied.