

Engineering Electromagnetics

EE2011

LECTURE 1

Chen Xudong

Dept. of Electrical and Computer Engineering
National University of Singapore

Transmission Lines – Basic Theories


1. Introduction

Transmission Line (T-Lines) may encompass all structures and media that serve to transfer electromagnetic energy (or signal) between two points.


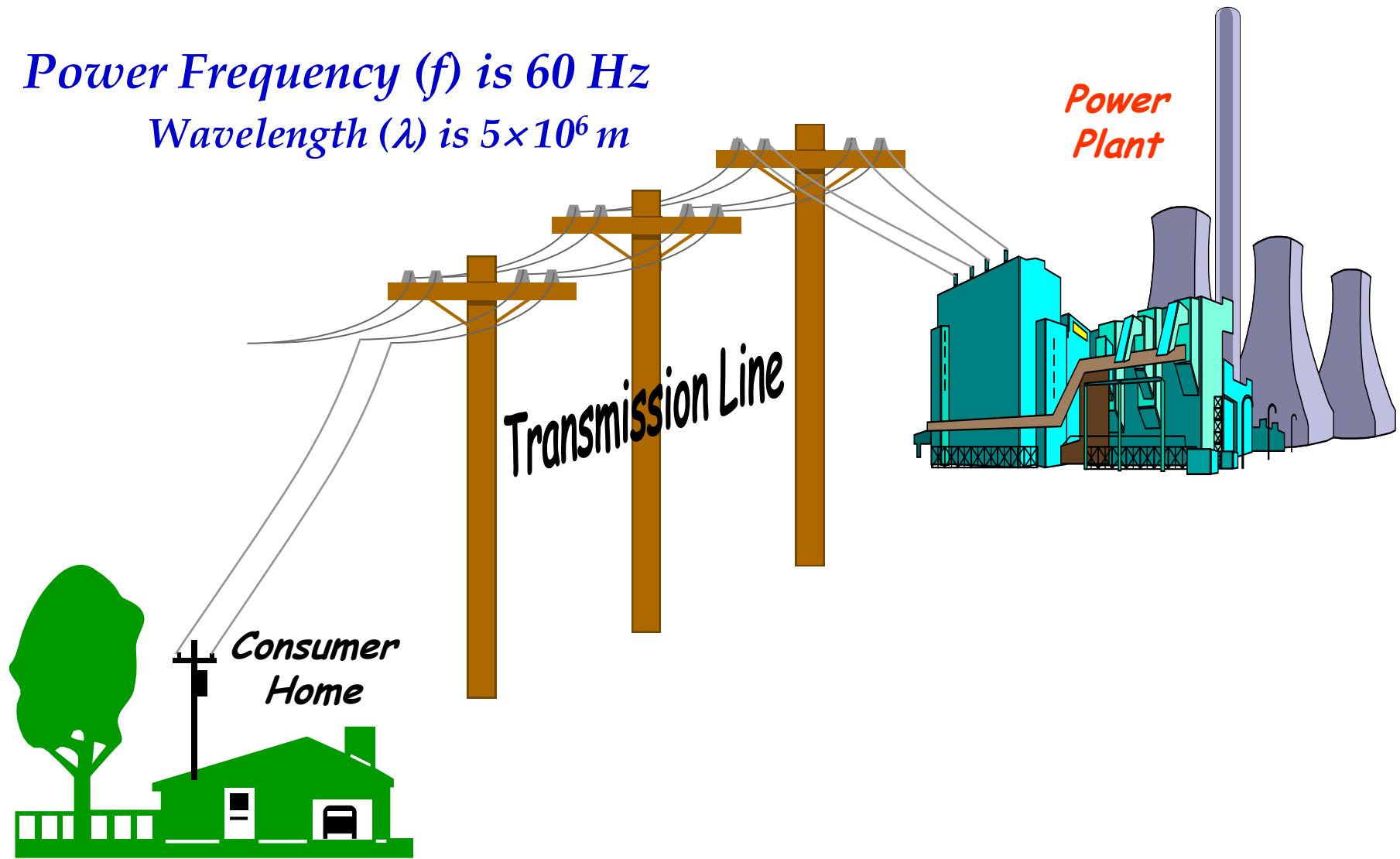
Examples:

- Electric lines for delivering electricity from power plants
- Coaxial cables or telephone wires carrying video or audio signals
- Optical fibers carrying light waves

Power Frequency (f) is 60 Hz
Wavelength (λ) is 5×10^6 m



Optical fiber

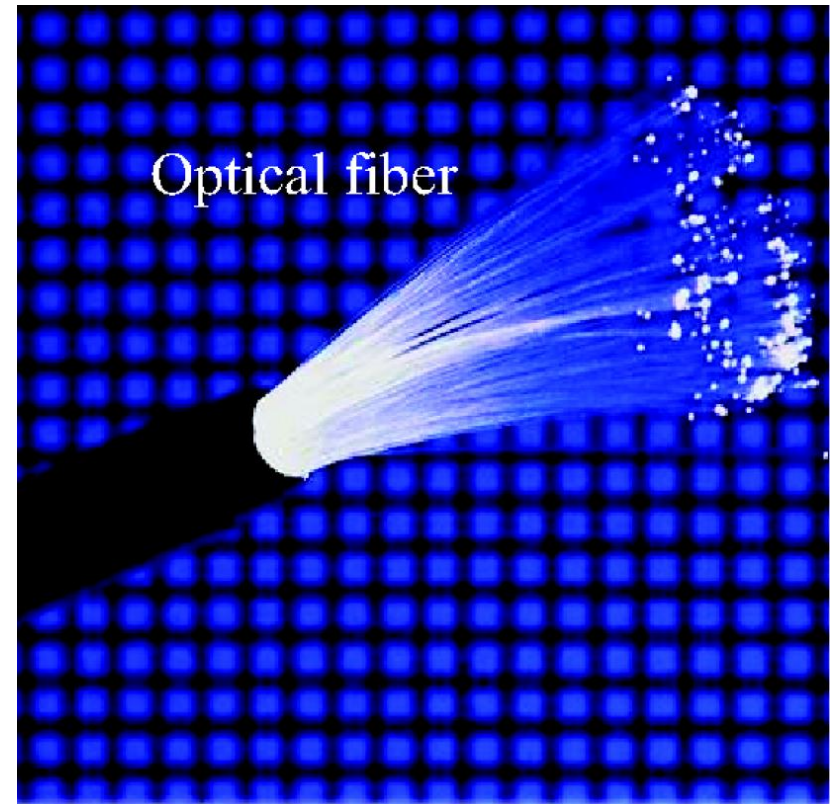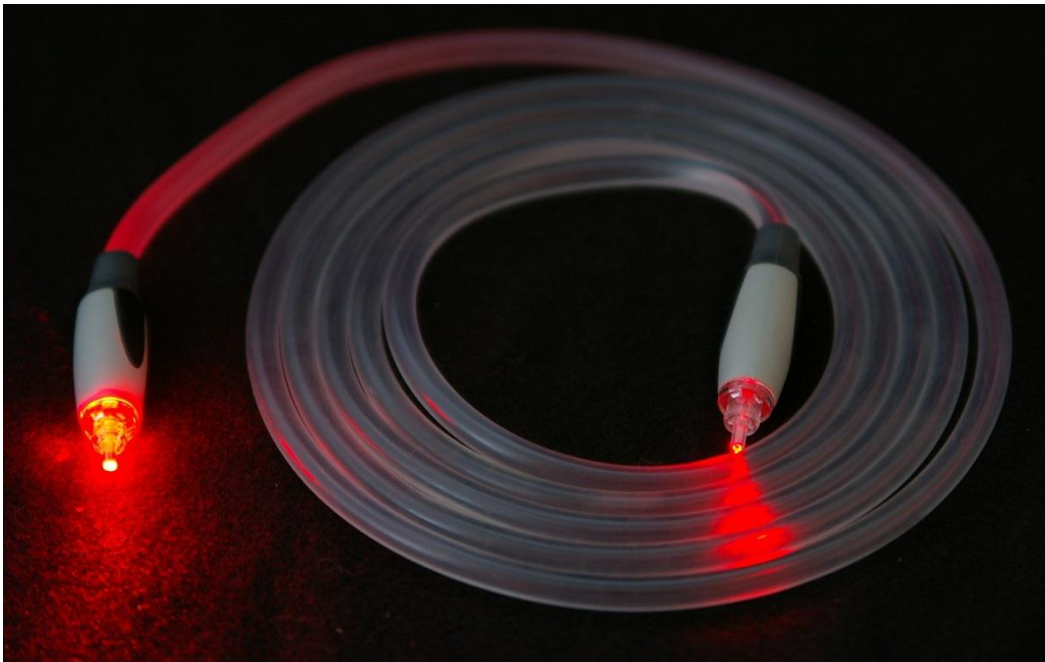


A transmission line is a two-port network connecting a generator circuit at the sending end to a load at the receiving end.




Note that the above symbol represents **the functionality** of the device, rather than its shape, size, material, or other attributes.


A few examples of Transmission Lines

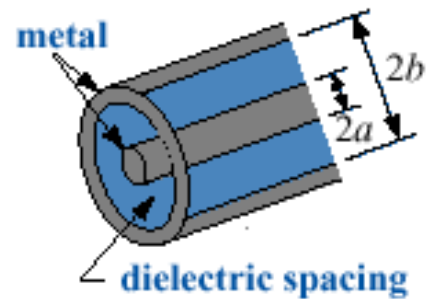


(a) Coaxial line

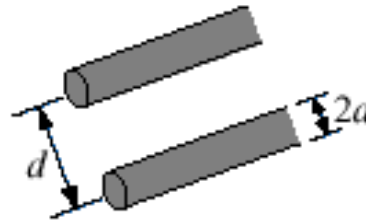


(b) Two-wire line

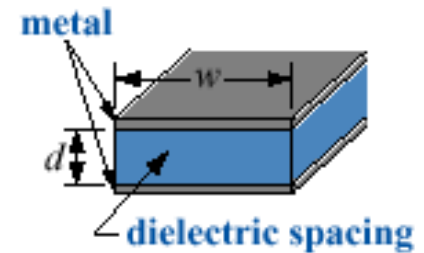

(c) Parallel-plate line

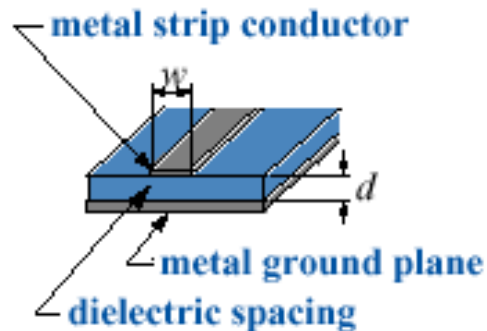


(d) Microstrip line

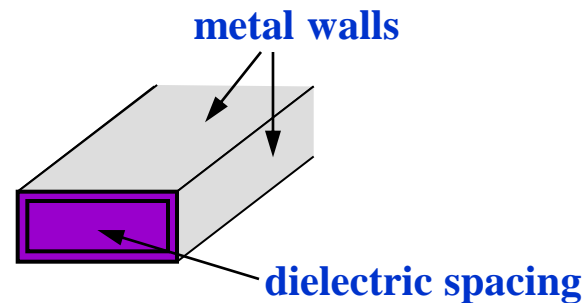

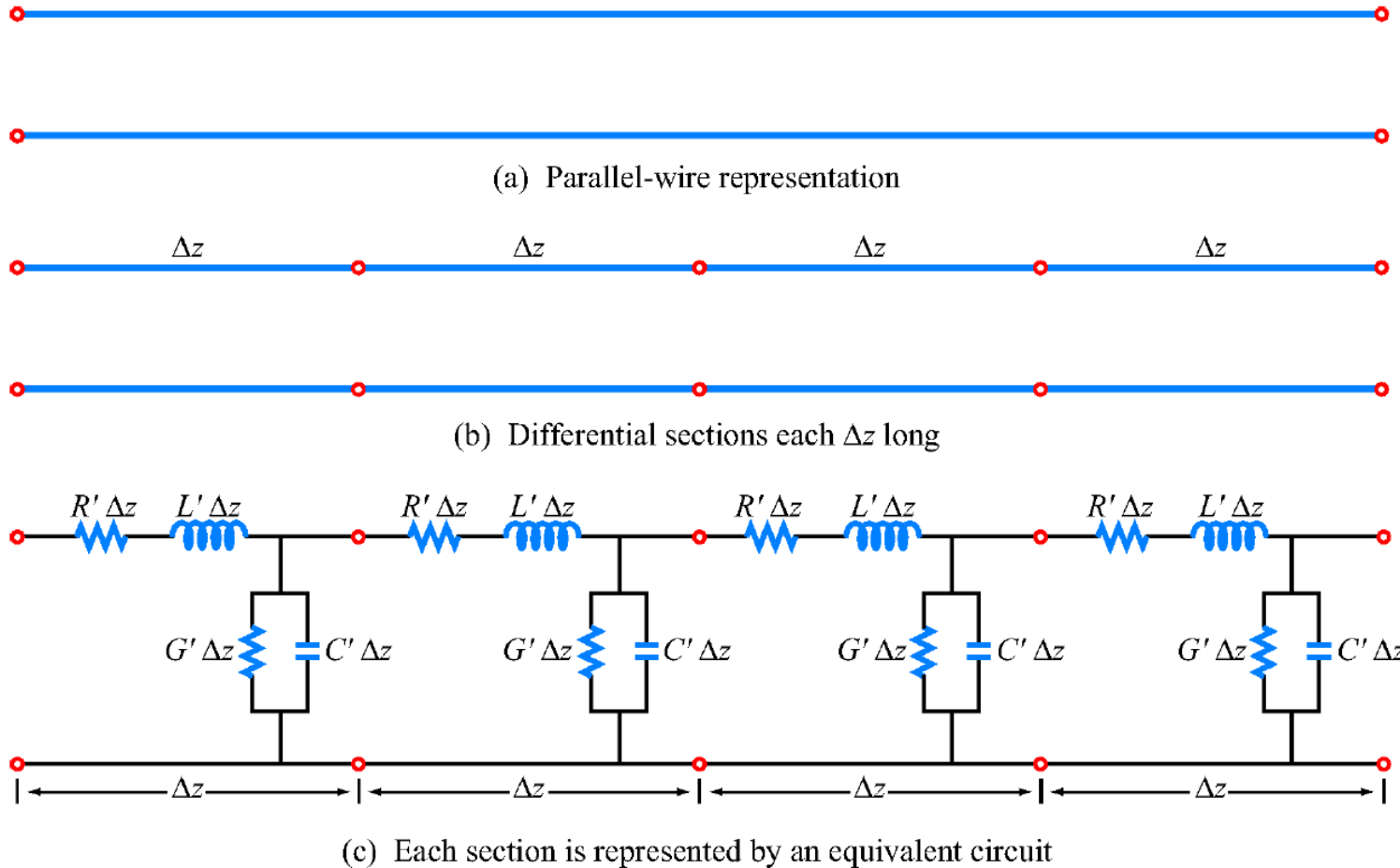(e) Rectangular Waveguide

Circuit approach to T-Lines: Lumped-Element Model



- (a) A transmission line is represented by the parallel-wire configuration;
- (b) The line is subdivided into **short** differential sections;
- (c) Each of small differential sections is represented by an equivalent circuit.

Schematically, we use a parallel-wire symbol to denote T-Lines of arbitrary types.

T-Lines of different types differ from each other in the following parameters:

R' : Resistance per unit length, in Ω / m

L' : Inductance per unit length, in H / m

G' : Conductance per unit length, in S / m

C' : Capacitance per unit length, in F / m

The prime superscript is used as a reminder that the line parameters are differential quantities whose units are per unit length.


Note: Regarding the derivation of the above parameters, it will be taught in Part YSP, and it will not be covered or tested in Part CXD.

Table 2-1: Transmission-line parameters R' , L' , G' , and C' for three types of lines.

Parameter	Coaxial	Two-Wire	Parallel-Plate	Unit
R'	$\frac{R_s}{2\pi} \left(\frac{1}{a} + \frac{1}{b} \right)$	$\frac{2R_s}{\pi d}$	$\frac{2R_s}{w}$	Ω/m
L'	$\frac{\mu}{2\pi} \ln(b/a)$	$\frac{\mu}{\pi} \ln \left[(D/d) + \sqrt{(D/d)^2 - 1} \right]$	$\frac{\mu h}{w}$	H/m
G'	$\frac{2\pi\sigma}{\ln(b/a)}$	$\frac{\pi\sigma}{\ln \left[(D/d) + \sqrt{(D/d)^2 - 1} \right]}$	$\frac{\sigma w}{h}$	S/m
C'	$\frac{2\pi\epsilon}{\ln(b/a)}$	$\frac{\pi\epsilon}{\ln \left[(D/d) + \sqrt{(D/d)^2 - 1} \right]}$	$\frac{\epsilon w}{h}$	F/m

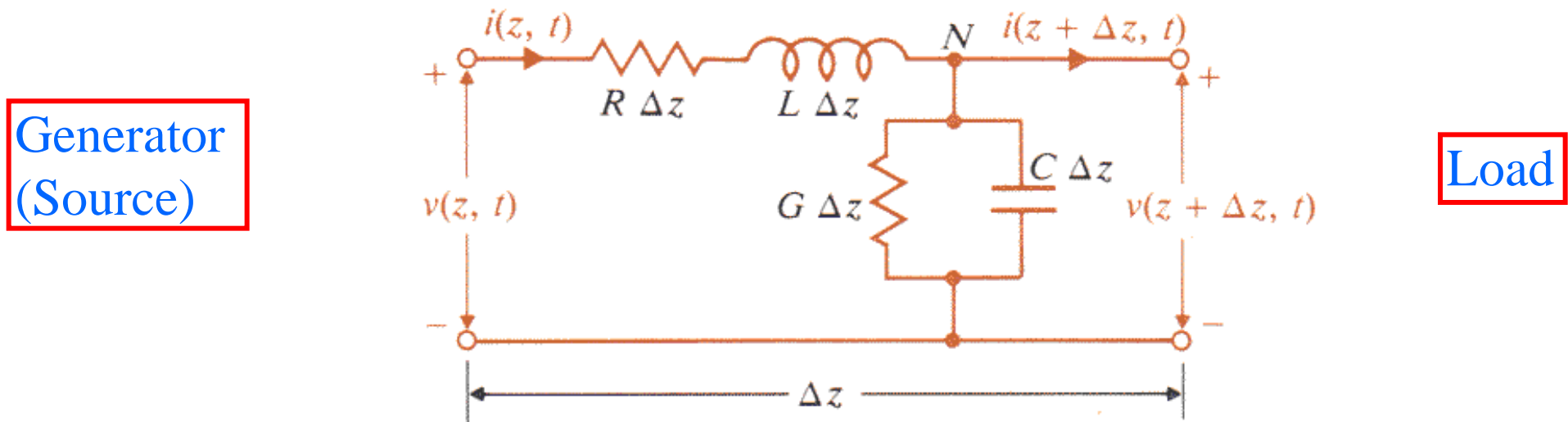2. Equations and solutions

Consider a **short** section Δz of a transmission line (For convenience, dropping the primes on R' , L' , G' , C' hereafter) :



Using **KVL** and **KCL** circuit theorems, we can derive the following differential equations for this section of T-Line.

$$\text{KVL: } v(z, t) - R\Delta z i(z, t) - L\Delta z \frac{\partial i(z, t)}{\partial t} - v(z + \Delta z, t) = 0$$

Upon dividing all terms by Δz and rearranging, we obtain

$$-\frac{v(z + \Delta z, t) - v(z, t)}{\Delta z} = Ri(z, t) + L \frac{\partial i(z, t)}{\partial t}$$

By letting $\Delta z \rightarrow 0$, it becomes

$$-\frac{\partial v(z, t)}{\partial z} = Ri(z, t) + L \frac{\partial i(z, t)}{\partial t}$$

$$\text{KCL: } i(z, t) - G\Delta z v(z + \Delta z, t) - C\Delta z \frac{\partial v(z + \Delta z, t)}{\partial t} - i(z + \Delta z, t) = 0$$

$$-\frac{\partial i(z, t)}{\partial z} = Gv(z, t) + C \frac{\partial v(z, t)}{\partial t}$$

The two equations in red box are the **Transmission Line Equations**

In terms of phasors (as mentioned in Lecture 0, the \sim on the top is dropped off for convenience), the T-Line equations can be written as:

$$-\frac{dV(z)}{dz} = (R + j\omega L)I(z)$$

$$-\frac{dI(z)}{dz} = (G + j\omega C)V(z)$$

By eliminating $I(z)$ or $V(z)$, we obtain respectively

$$\frac{d^2V(z)}{dz^2} = \gamma^2 V(z)$$

$$\frac{d^2I(z)}{dz^2} = \gamma^2 I(z)$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} = \alpha + j\beta$$

γ is the complex propagation constant whose real part α is the **attenuation constant** (Np/m) and whose imaginary part β is the **phase constant** (rad/m).

It is easily to verify that the solutions to transmission line equations are of the forms

$$\begin{aligned} V(z) &= V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z} \\ I(z) &= I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z} \end{aligned}$$

Forward travelling wave. Backward travelling wave.

$V_0^+, V_0^-, I_0^+, I_0^-$: wave amplitudes in the forward and backward directions at $z = 0$. (They are complex numbers in general.)

The relationships between V_0^+ and I_0^+ , V_0^- and I_0^- :

$$I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z}$$

Since $-\frac{dI(z)}{dz} = (G + j\omega C)V(z)$

$$\begin{aligned} V(z) &= \frac{1}{-(G + j\omega C)} \frac{\partial}{\partial z} (I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z}) \\ &= \frac{1}{-(G + j\omega C)} (-\gamma I_0^+ e^{-\gamma z} + \gamma I_0^- e^{+\gamma z}) \\ &= \frac{\gamma}{G + j\omega C} (I_0^+ e^{-\gamma z} - I_0^- e^{+\gamma z}) \end{aligned}$$

It can be rewritten as

$$\rightarrow = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

$$+\frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-} = \frac{\gamma}{G + j\omega C} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

3. Transmission Line Parameters

From the solutions to the transmission line equations, we have

$$+\frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-} = \frac{\gamma}{G + j\omega C} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

This ratio is defined as the **characteristic impedance** Z_0 .

Z_0 and γ are the two most important parameters of a T-line. They depend on the distributed parameters ($RLGC$) of the line itself and ω .

$$Z_0 = \frac{R + j\omega L}{\gamma} = \frac{\gamma}{G + j\omega C} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

Parameters for lossless transmission lines

In many practical situations, T-lines can be designed to exhibit very low losses, which can be well modelled as lossless T-Lines.

For lossless T-Lines, $R = G = 0$

$$\alpha = 0 \quad \beta = \omega\sqrt{LC} \quad \gamma = j\beta$$

$$Z_0 = \sqrt{L/C}$$

For lossless T-Lines, we often use k (wavenumber) instead of β . Thus,

$$\gamma = jk$$

Consequently, the wave solutions for $V(z)$ and $I(z)$ that are obtained earlier take the same format as the wave solutions introduced in Lecture 0.

$$V(z) = V_0^+ e^{-jkz} + V_0^- e^{+jkz}$$

$$I(z) = I_0^+ e^{-jkz} + I_0^- e^{+jkz}$$

From Lecture 0, we have

$$\lambda = \frac{2\pi}{k} = \frac{2\pi}{\omega\sqrt{LC}} = \frac{1}{f\sqrt{LC}} \quad (\text{wavelength along the T-Line})$$

$$u_p = \frac{\omega}{k} = \frac{1}{\sqrt{LC}} = \frac{c}{\sqrt{\epsilon_r}} \quad (\text{phase velocity})$$

where c is the **speed of light** in free space, 3×10^8 m/s, and

ϵ_r is the **relative permittivity** of the dielectric material filling the T-Line
will be taught in Part YSP and later lectures of Part CXD


From here onwards, we consider only lossless transmission lines

Further discussion on the meaning of k

k in spatial domain
is the counterpart of
 ω in temporal domain

Temporal domain	Spatial domain
$\omega = 2\pi / T$	$k = 2\pi / \lambda$
Unit: rad/s	Unit: rad/m
T is (temporal) period	λ is wavelength (or period in spatial domain)
ω means the number of revolutions in a period of 2π seconds, referred to as angular (temporal) frequency	k means the number of wavelengths in a distance of 2π meters, referred to as wavenumber (or spatial frequency)

4. Terminated Transmission Line

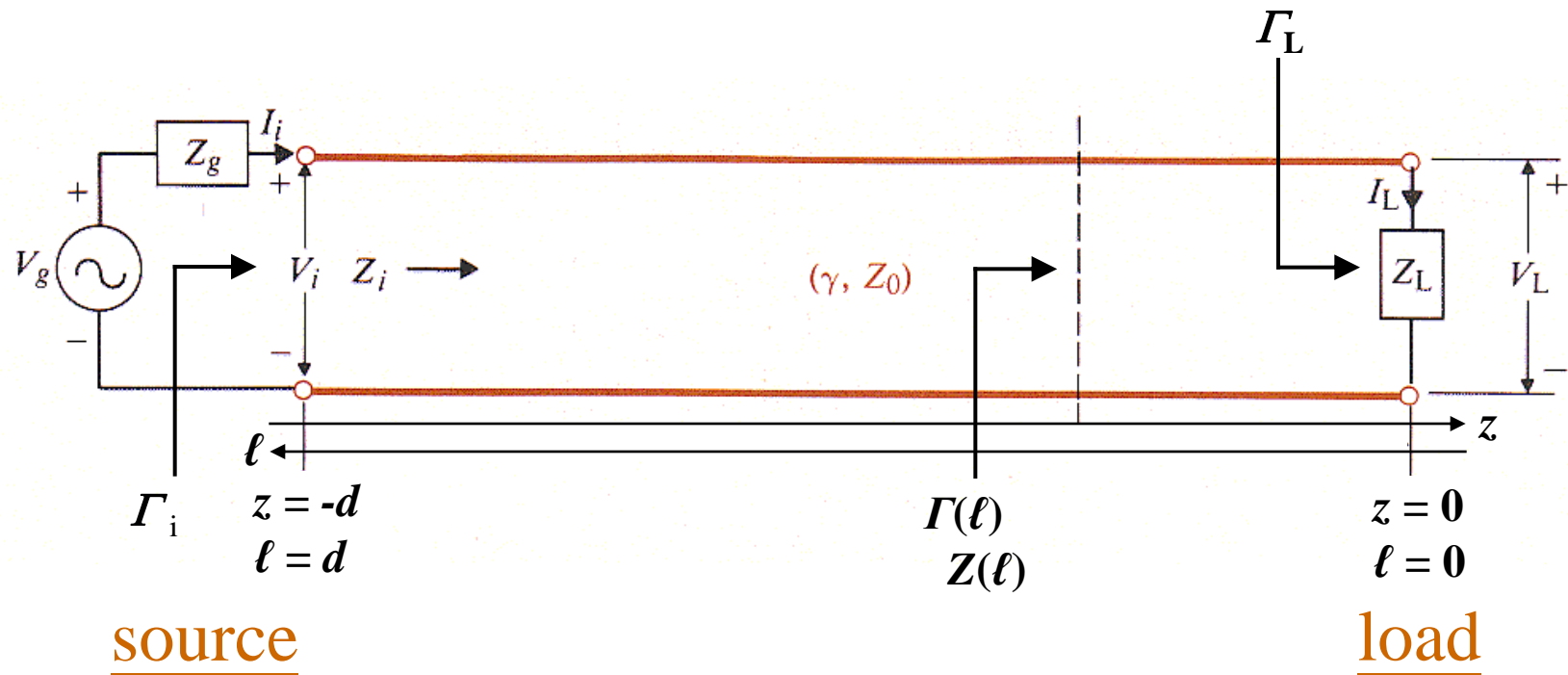

Note the two coordinate systems and their relation:

z = measuring from the left to the right

ℓ = measuring from the right to the left

$$\ell = -z$$

Note: Any position on T-Line has a nonnegative value of ℓ

Generally, Voltage and current along the line:

$$V(z) = V_0^+ e^{-jkz} + V_0^- e^{jkz}$$

$$I(z) = I_0^+ e^{-jkz} + I_0^- e^{jkz}$$

In the ℓ ($\ell = -z$) coordinate system,

$$V_0^+ e^{jk\ell} + V_0^- e^{-jk\ell} = V(\ell)$$

$$I_0^+ e^{jk\ell} + I_0^- e^{-jk\ell} = I(\ell)$$

At the position of the load ($\ell = 0$), we denote the voltage to be V_L and the current to be I_L . Then we have:

$$V_0^+ + V_0^- = V_L$$

$$\frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0} = I_L$$

$$\boxed{\frac{V_L}{I_L} = Z_L}$$

Two equations for two unknowns,
the solution is given by:

$$V_0^+ = \frac{1}{2} I_L (Z_L + Z_0)$$

$$V_0^- = \frac{1}{2} I_L (Z_L - Z_0)$$

Putting the expressions for V_0^+ and V_0^- into the equations for the voltage and current, we have:

$$\begin{aligned} V(\ell) &= \frac{1}{2} I_L [Z_L (e^{jk\ell} + e^{-jk\ell}) + Z_0 (e^{jk\ell} - e^{-jk\ell})] \\ &= I_L [Z_L \cos(k\ell) + jZ_0 \sin(k\ell)] \end{aligned}$$

$$\begin{aligned} I(\ell) &= \frac{1}{2} \frac{I_L}{Z_0} [Z_L (e^{jk\ell} - e^{-jk\ell}) + Z_0 (e^{jk\ell} + e^{-jk\ell})] \\ &= \frac{I_L}{Z_0} [Z_0 \cos(k\ell) + jZ_L \sin(k\ell)] \end{aligned}$$

To summarize: Once knowing the current or voltage at the load, we then obtain current and voltage everywhere on T-Line.

Using $V(\ell)$ and $I(\ell)$, we can define the **input impedance** $Z(\ell)$ at an arbitrary point ℓ on the transmission line as:

$$Z(\ell) = \frac{V(\ell)}{I(\ell)} = Z_0 \frac{Z_L + jZ_0 \tan(k\ell)}{Z_0 + jZ_L \tan(k\ell)}$$

Define a **reflection coefficient at the load $l = 0$** as Γ_L :

$$\begin{aligned}\Gamma_L &= \frac{\text{reflected voltage at } l = 0}{\text{incident voltage at } l = 0} \\ &= \frac{V_0^- e^{-jk \times 0}}{V_0^+ e^{+jk \times 0}} = \frac{V_0^-}{V_0^+} = \frac{(1/2)I_L (Z_L - Z_0)}{(1/2)I_L (Z_L + Z_0)} \\ &= \frac{Z_L - Z_0}{Z_L + Z_0}\end{aligned}$$

In fact, we can further define a **reflection coefficient $\Gamma(\ell)$ at any point ℓ** on the transmission line by:

$$\begin{aligned}\Gamma(\ell) &= \frac{\text{reflected voltage at point } \ell}{\text{incident voltage at point } \ell} \\ &= \frac{V_0^- e^{-jk\ell}}{V_0^+ e^{jk\ell}} = \frac{V_0^-}{V_0^+} e^{-j2k\ell} = \Gamma_L e^{-j2k\ell}\end{aligned}$$

Similar to the reflection coefficient at the load, we have


$$\Gamma(\ell) = \frac{Z(\ell) - Z_0}{Z(\ell) + Z_0}$$

At the position of the generator ($\ell = d$),

$$Z_i = Z(\ell = d) = Z_0 \frac{Z_L + jZ_0 \tan(kd)}{Z_0 + jZ_L \tan(kd)}$$

$$\Gamma(\ell = d) = \Gamma_i = \frac{Z_i - Z_0}{Z_i + Z_0} = \Gamma_L e^{-j2kd}$$

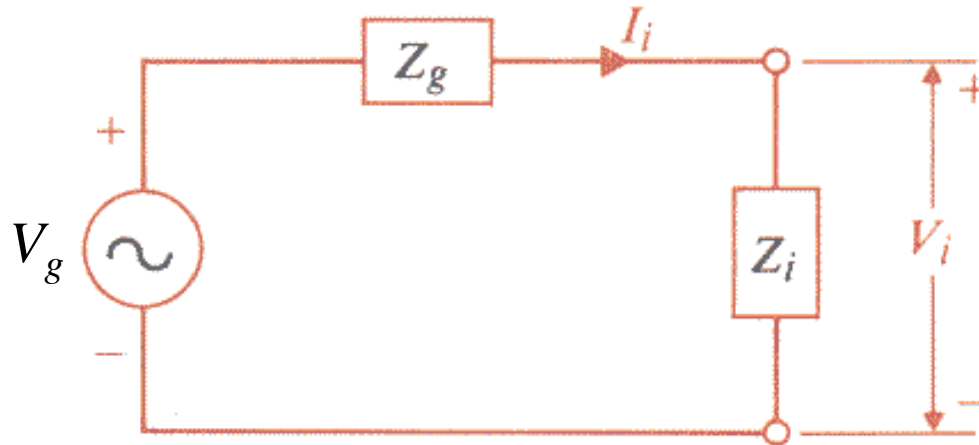By using the input impedance Z_i , the T-Line problem becomes a traditional circuit problem: Voltage divider.



Applying KCL and KVL to circuit:

$$I(d) = I_i = \frac{V_g}{Z_g + Z_i}$$

$$V(d) = V_i = I_i Z_i = \frac{Z_i}{Z_g + Z_i} V_g$$

As obtained in Page 22, At an arbitrary position $z = l$,

$$V(\ell) = I_L [Z_L \cos(k\ell) + jZ_0 \sin(k\ell)]$$

$$I(\ell) = \frac{I_L}{Z_0} [Z_0 \cos(k\ell) + jZ_L \sin(k\ell)]$$

We have, letting $l=d$,

$$I_L = \frac{V_i}{Z_L \cos(kd) + jZ_0 \sin(kd)}$$

Thus, complete solutions for voltage and current on T-Line are obtained

To summarize:

The input impedance

$$Z(\ell) = \frac{V(\ell)}{I(\ell)} = Z_0 \frac{Z_L + jZ_0 \tan(k\ell)}{Z_0 + jZ_L \tan(k\ell)}$$

replaces the T-Line together with terminated load by an equivalent impedance.


Thus, the T-Line problem becomes a circuit problem, where KCL & KVL are applicable.

When there are multiple T-Lines, we apply input impedance multiple times, eventually yielding a circuit problem.

Example 1

A $100\text{-}\Omega$ transmission line is connected to a load consisted of a $50\text{-}\Omega$ resistor in series with a 10-pF capacitor.

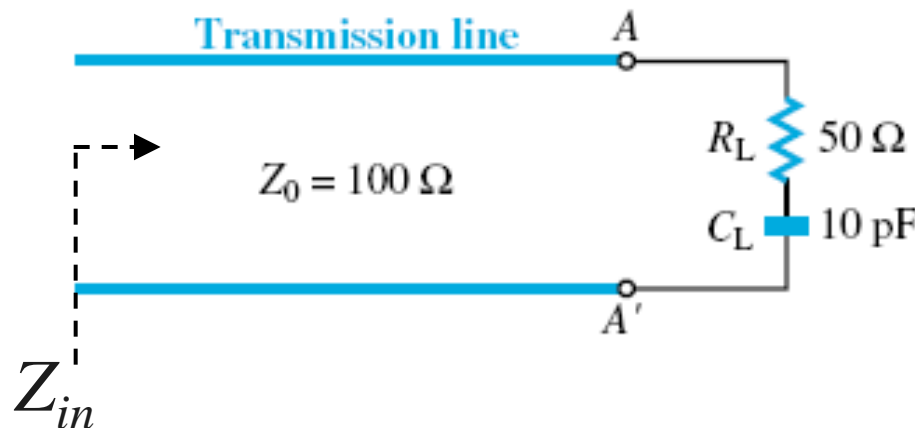- (a) Find the reflection coefficient Γ_L at the load for a 100-MHz signal.
- (b) Find the impedance Z_{in} at the input end of the transmission line if its length is 0.125λ .



Solutions

The following information is given

$$R_L = 50\Omega, \quad C_L = 10^{-11}\text{F}, \quad Z_0 = 100\Omega, \quad f = 100\text{MHz} = 10^8\text{Hz}$$

The load impedance is

$$\begin{aligned} Z_L &= R_L - j/\omega C_L \\ &= 50 - j \frac{1}{2\pi \times 10^8 \times 10^{-11}} = 50 - j159 \quad (\Omega) \end{aligned}$$

(a) Reflection coefficient at the load is

$$\Gamma_L = \frac{Z_L / Z_0 - 1}{Z_L / Z_0 + 1} = \frac{0.5 - j1.59 - 1}{0.5 - j1.59 + 1} = 0.76 \angle -60.70^\circ$$


(b) $d = 0.125\lambda$

$$\begin{aligned} Z_{in} &= Z(\ell = 0.125\lambda) \\ &= Z_0 \frac{Z_L + jZ_0 \tan(\pi/4)}{Z_0 + jZ_L \tan(\pi/4)} \quad \text{Note: } k\lambda = 2\pi \\ &= Z_0 \frac{Z_L + jZ_0}{Z_0 + jZ_L} \\ &= 14.3717 - j25.5544 \quad (\Omega) \\ &= 29.32 \angle -60.65^\circ \quad (\Omega) \end{aligned}$$

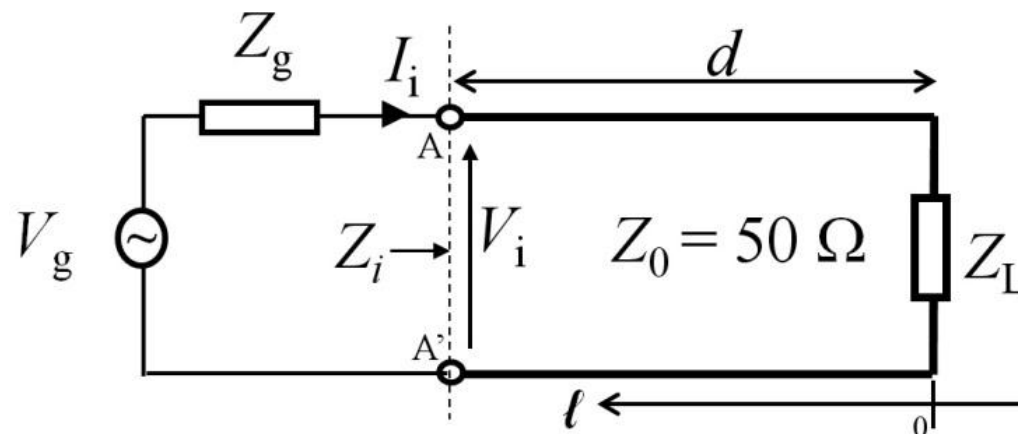Example 2

A lossless transmission line with $Z_0 = 50 \Omega$ and $d = 5.3\lambda$ connects a voltage V_g source to a terminal load of $Z_L = 100 \Omega$. It is known that $V_g = 100 \text{ V}$ and $Z_g = 25 \Omega$.

- Find the current I_i and voltage V_i at the left terminal of the transmission line.
- What are the current I_L and voltage V_L at the load?
- What are the current and voltage in the middle of transmission line?



Solutions

(a) The input impedance at the left terminal of the T-Line is

$$Z_i = Z_0 \frac{Z_L + jZ_0 \tan(kd)}{Z_0 + jZ_L \tan(kd)} = 50 \frac{100 + j50 \tan(5.3 \times 2\pi)}{50 + j100 \tan(5.3 \times 2\pi)} = 26.9 + j11.87 \Omega$$

From the resultant voltage divider, we obtain

$$I_i = \frac{V_g}{Z_g + Z_i} = \frac{100}{25 + (26.9 + j11.87)} = 1.8301 - j0.4184 \text{ A}$$

$$V_i = I_i Z_i = 54.2480 + j10.4592 \text{ V}$$

(b) From Page 26, at $l=d$,

$$I_L = \frac{V_i}{Z_L \cos(kd) + jZ_0 \sin(kd)}$$

Plugging in numbers, we have

$$I_L = -0.3666 - j0.9026 \text{ A}$$

$$V_L = I_L Z_L = -36.6581 - j90.2576 \text{ V}$$

(c) Letting $l=d/2$ and plugging numbers into

$$V(\ell) = I_L [Z_L \cos(k\ell) + jZ_0 \sin(k\ell)]$$

$$I(\ell) = \frac{I_L}{Z_0} [Z_0 \cos(k\ell) + jZ_L \sin(k\ell)]$$

we obtain

$$V(\ell = d/2) = -14.9629 + j67.8806 \text{ V}$$

$$I(\ell = d/2) = -1.2449 + j1.1237 \text{ A}$$

5. Voltage/current maxima and minima

$$V(\ell) = V_0^+ e^{j k \ell} + V_0^- e^{-j k \ell}$$

$$= V_0^+ e^{j k \ell} \left(1 + \frac{V_0^-}{V_0^+} e^{-j 2 k \ell} \right)$$

$$= V_0^+ e^{j k \ell} (1 + \Gamma_L e^{-j 2 k \ell})$$

$$\Gamma_L = |\Gamma_L| e^{j \theta_L}$$

$$|\Gamma_L| \leq 1$$



$$|V(\ell)| = |V_0^+| |1 + \Gamma_L e^{-j 2 k \ell}|$$

$$= |V_0^+| |1 + |\Gamma_L| e^{j(\theta_L - 2 k \ell)}|$$

$$= |V_0^+| |1 + \Gamma|$$

$$\Gamma = |\Gamma_L| e^{j(\theta_L - 2 k \ell)}$$

which is a complex number

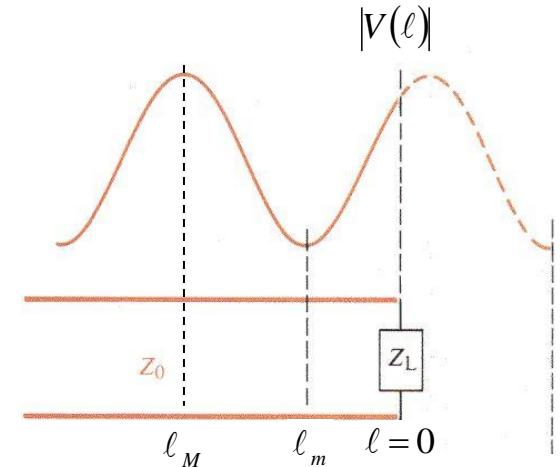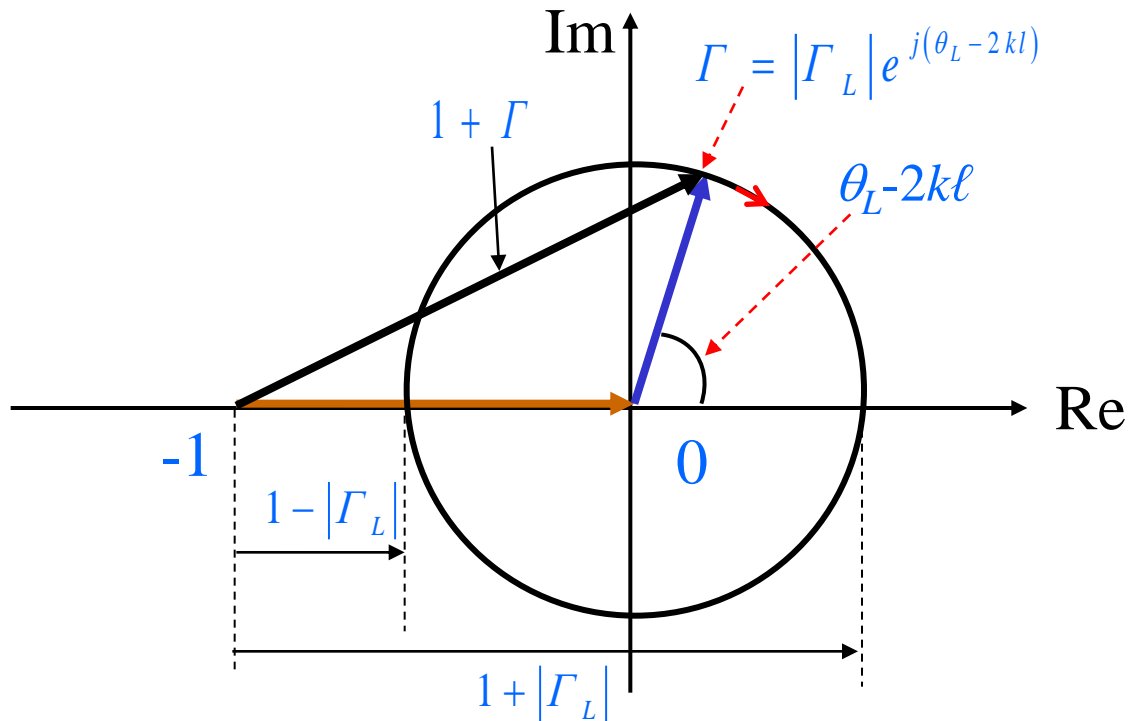

$|1 + \Gamma| = |\Gamma - (-1)|$ is the distance between Γ and -1 in complex plane

- (1) When ℓ increases, the angle $\theta_L - 2k\ell$ decreases, i.e., rotating clockwise.
- (2) Since $k\lambda = 2\pi$, when ℓ increases by λ , $|1 + \Gamma|$ experiences 2 periods since $2k\ell$ is in the exponent.

$|V(\ell)|$ is maximum when $|1 + \Gamma| = (1 + |\Gamma_L|)$

$$|V(\ell)|_{\max} \Rightarrow \theta_L - 2k\ell = -2n\pi$$

$$\Rightarrow \ell_M = \frac{\theta_L \lambda}{4\pi} + \frac{n\lambda}{2}, \quad \begin{cases} n = 0, 1, 2, \dots & \theta_L \geq 0 \\ n = 1, 2, \dots & \theta_L < 0 \end{cases}$$

Note: θ_L has to be specified in the range $[-\pi, \pi)$.

$|V(\ell)|$ is minimum when $|1 + \Gamma| = (1 - |\Gamma_L|)$

$$|V(\ell)|_{\min} \Rightarrow \theta_L - 2k\ell = -(2n+1)\pi$$

$$\Rightarrow \ell_m = \frac{\theta_L \lambda}{4\pi} + \frac{(2n+1)\lambda}{4}, \quad n = 0, 1, 2, \dots$$

Note: θ_L has to be specified in the range $[-\pi, \pi)$.

As current is

$$|I(\ell)| = |I_0^+| |1 - \Gamma_L e^{-j2k\ell}|$$

$$= \left| \frac{V_0^+}{Z_0} \right| |1 - \Gamma|$$

Current is maximum when voltage is minimum and minimum when voltage is maximum.

$$|I(\ell)|_{\max} \text{ at } \ell_M = \frac{\theta_L \lambda}{4\pi} + \frac{(2n+1)\lambda}{4}, \quad n = 0, 1, 2, \dots$$



$$|I(\ell)|_{\min} \text{ at } \ell_m = \frac{\theta_L \lambda}{4\pi} + \frac{n\lambda}{2}, \quad \begin{cases} n = 0, 1, 2, \dots & \theta_L \geq 0 \\ n = 1, 2, \dots & \theta_L < 0 \end{cases}$$

Define a voltage standing wave ratio (VSWR) as:

S = voltage standing wave ratio (VSWR)

$$= \frac{|V(\ell)|_{\max}}{|V(\ell)|_{\min}} = \frac{|V_0^+| (1 + |\Gamma_L|)}{|V_0^+| (1 - |\Gamma_L|)} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \quad (\text{dimensionless})$$

$$|\Gamma_L| = \frac{S - 1}{S + 1}$$

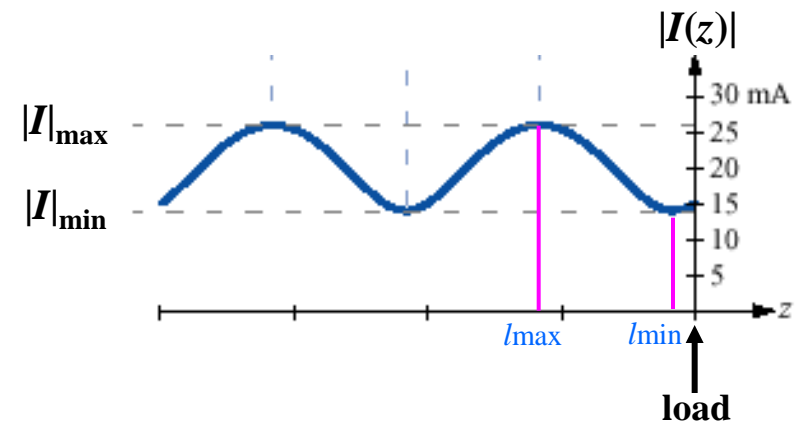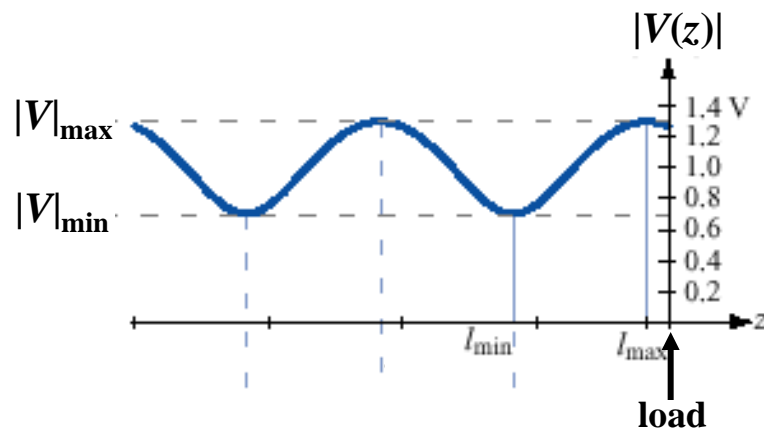

Special terminations

Γ_L	S	Z_L
0	1	$Z_L = Z_0$ (matched)
-1	∞	$Z_L = 0$ (short-circuited)
1	∞	$Z_L = \infty$ (open-circuited)


6. Power flow in a transmission line

Power flow at any point z on a transmission line is given by:

$$P_{av}(z) = \frac{1}{2} \operatorname{Re}\{V(z)I^*(z)\}$$

Since V and I correspond to E-field and H-field, the power flow corresponds to time-average Poynting power. It is not the power converted to heat by Joule's law.

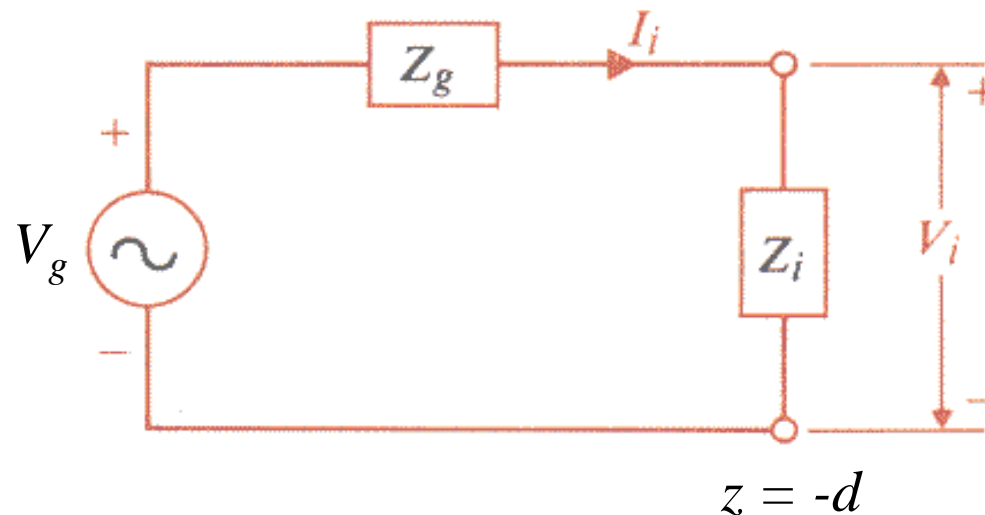At $z = -d$, the equivalent circuit is given by



Power delivered by the source:

$$P_s = \frac{1}{2} \operatorname{Re}\{V_g I_i^*\}$$

Power dissipated in the source impedance Z_g :

$$P_{Z_g} = \frac{1}{2} \operatorname{Re}\{V_{Z_g} I_{Z_g}^*\} = \frac{1}{2} \operatorname{Re}\{Z_g I_i I_i^*\} = \frac{1}{2} |I_i|^2 \operatorname{Re}\{Z_g\}$$

Power input to the transmission line:

$$\begin{aligned} P_i &= P_{av}(-d) = \frac{1}{2} \operatorname{Re}\{V(-d) I^*(-d)\} \\ &= \frac{1}{2} \operatorname{Re}\{V_i I_i^*\} = \begin{cases} = \frac{1}{2} \operatorname{Re}\{Z_i I_i I_i^*\} = \frac{1}{2} |I_i|^2 \operatorname{Re}\{Z_i\} \\ = \frac{1}{2} \operatorname{Re}\left\{V_i \frac{V_i^*}{Z_i^*}\right\} = \frac{1}{2} |V_i|^2 \operatorname{Re}\left\{\frac{1}{Z_i}\right\} \end{cases} \end{aligned}$$

Complex conjugate operator:
can be dropped off since

$$\begin{aligned} \operatorname{Re}\left\{\frac{1}{Z_i}\right\} &= \frac{1}{|Z_i|} \operatorname{Re}\left\{\frac{1}{e^{j\theta_{Z_i}}}\right\} \\ &= \frac{1}{|Z_i|} \operatorname{Re}\{\cos \theta_{Z_i} - j \sin \theta_{Z_i}\} \\ &= \frac{\cos \theta_{Z_i}}{|Z_i|} \end{aligned}$$

$$\begin{aligned} \text{and } \operatorname{Re}\left\{\frac{1}{Z_i^*}\right\} &= \frac{1}{|Z_i|} \operatorname{Re}\{\cos \theta_{Z_i} + j \sin \theta_{Z_i}\} \\ &= \frac{\cos \theta_{Z_i}}{|Z_i|} \end{aligned}$$

Power dissipated in the terminal impedance:

$$\begin{aligned} P_L &= P_{av}(0) = \frac{1}{2} \operatorname{Re}\{V(0)I^*(0)\} \\ &= \frac{1}{2} \operatorname{Re}\{V_L I_L^*\} = \begin{cases} = \frac{1}{2} |I_L|^2 \operatorname{Re}\{Z_L\} \\ = \frac{1}{2} |V_L|^2 \operatorname{Re}\left\{\frac{1}{Z_L}\right\} \end{cases} \end{aligned}$$

By the principle of conservation of power:


$$P_s = P_{Z_g} + P_i$$

$$P_i = P_L$$

We consider only lossless T-lines

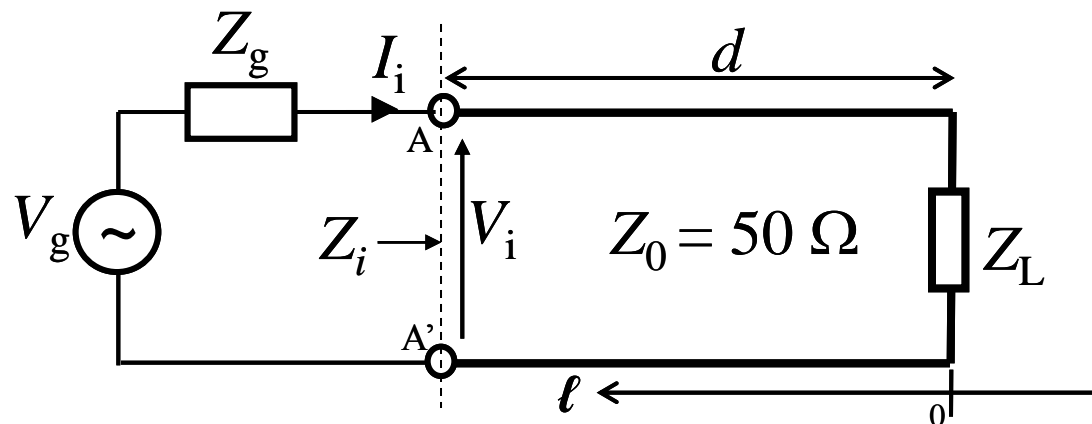Example 3

A lossless transmission line with $Z_0 = 50 \, \Omega$ and $d = 1.5 \, \text{m}$ connects a voltage V_g source to a terminal load of $Z_L = (50 + j50) \, \Omega$. If $V_g = 60 \, \text{V}$, operating frequency $f = 100 \, \text{MHz}$, and $Z_g = 50 \, \Omega$, find the distance of the first voltage maximum ℓ_M from the load. What is the power delivered to the load P_L ? Assume the speed of the wave along the transmission line equal to speed of light, c .



Solutions

The following information is given:

$$Z_0 = 50\Omega, \quad d = 1.5 \text{ m},$$

$$V_g = 60 \text{ V}, \quad Z_g = 50\Omega, \quad Z_L = 50 + j50\Omega,$$

$$f = 100\text{MHz} = 10^8\text{Hz}$$

$$u_p = c \quad \Rightarrow \quad \lambda = \frac{c}{10^8} = 3 \text{ m}$$

The reflection coefficient at the load is:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{50 + j50 - 50}{50 + j50 + 50} = 0.2 + j0.4 = 0.45e^{j1.11}$$

Therefore, $|\Gamma_L| = 0.45$, $\theta_L = 1.11 \text{ rad}$

Then,
$$\ell_M = \frac{\theta_L \lambda}{4\pi} + \frac{n\lambda}{2}, \quad \text{when } n = 0$$
$$= \frac{1.11\lambda}{4\pi} = 0.09\lambda = 0.27 \text{ m (from the load)}$$

The input impedance Z_i looking at the input to the transmission line is:

$$Z_i = Z_0 \frac{Z_L + jZ_0 \tan(kd)}{Z_0 + jZ_L \tan(kd)}$$

$$Z_i = 50 \frac{50 + j50 + j50 \tan\left(\frac{2\pi}{3} \times 1.5\right)}{50 + j(50 + j50) \tan\left(\frac{2\pi}{3} \times 1.5\right)} = 50 + j50 \Omega$$

The current at the input to the transmission line is :

$$I_i = \frac{V_g}{Z_g + Z_i} = \frac{60}{50 + 50 + j50} = 0.48 - j0.24 \text{ A}$$

As the transmission line is lossless, power delivered to the load P_L is equal to the power input to the transmission line P_i . Hence,

$$P_L = P_i = \frac{1}{2} |I_i|^2 \text{Re}\{Z_i\} = \frac{1}{2} \times 0.288 \times 50 = 7.2 \text{ W}$$


7. Special Cases of Terminations in a Transmission Line

7.1 Matched line


For a matched line, $Z_L = Z_0$. Then,

$$\left. \begin{aligned} Z(\ell) &= Z_0 \frac{Z_0 + jZ_0 \tan(k\ell)}{Z_0 + jZ_0 \tan(k\ell)} = Z_0 \\ \Gamma(\ell) &= \frac{Z(\ell) - Z_0}{Z(\ell) + Z_0} = 0 \end{aligned} \right\} \text{for any length } \ell \text{ of the line}$$


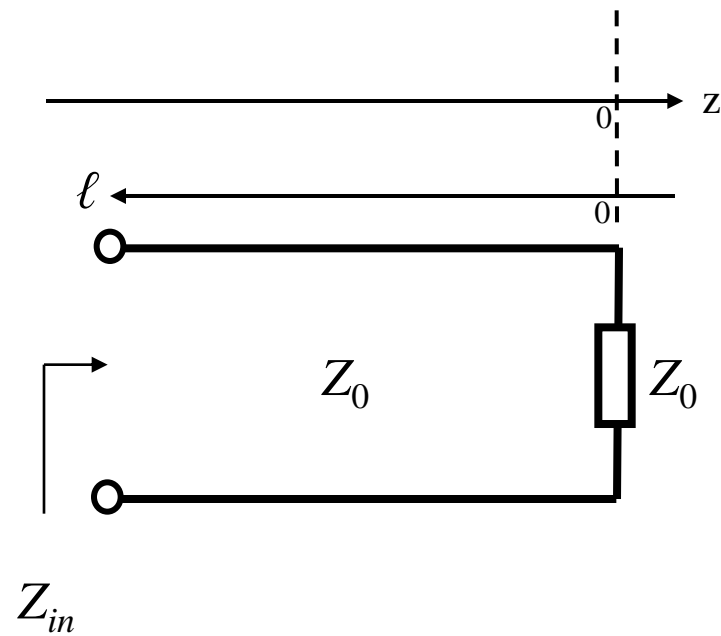
Thus, there is no reflection on a matched line. There is only an incident voltage.



Normalized voltage magnitude

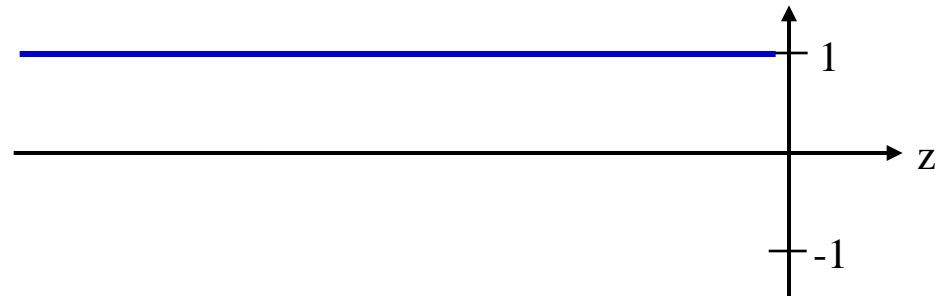

Normalized current magnitude

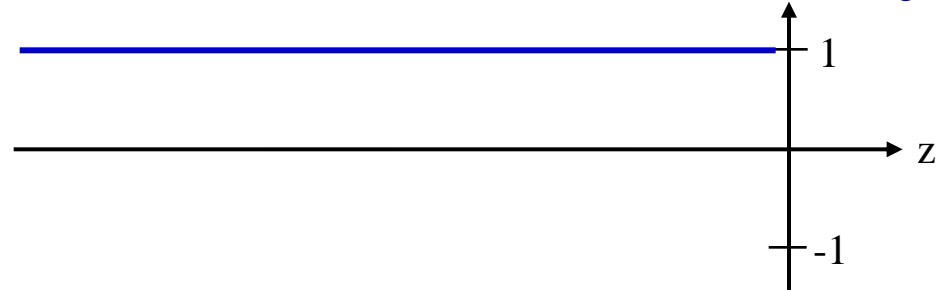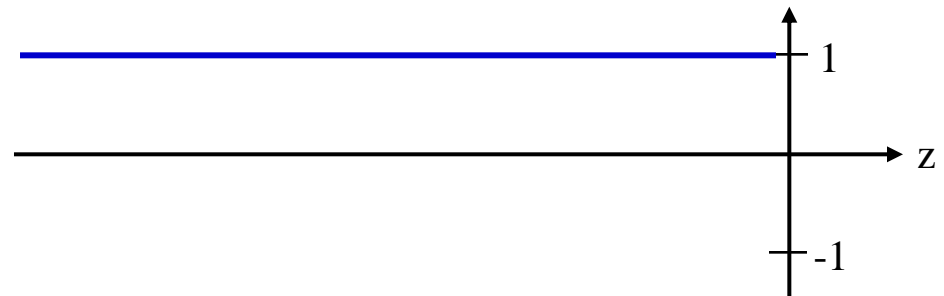Normalized impedance (Z_{in}/Z_0)

Note:

Normalized voltage = voltage/max. |voltage|


Normalized current = current/max. |current|

7.2 Short-circuited line

For a short circuit, $Z_L = 0$. Then

$$Z_{\text{in}}^{\text{sc}} = jZ_0 \tan(k\ell) = -jZ_0 \tan(kz)$$

Note $\ell = -z$

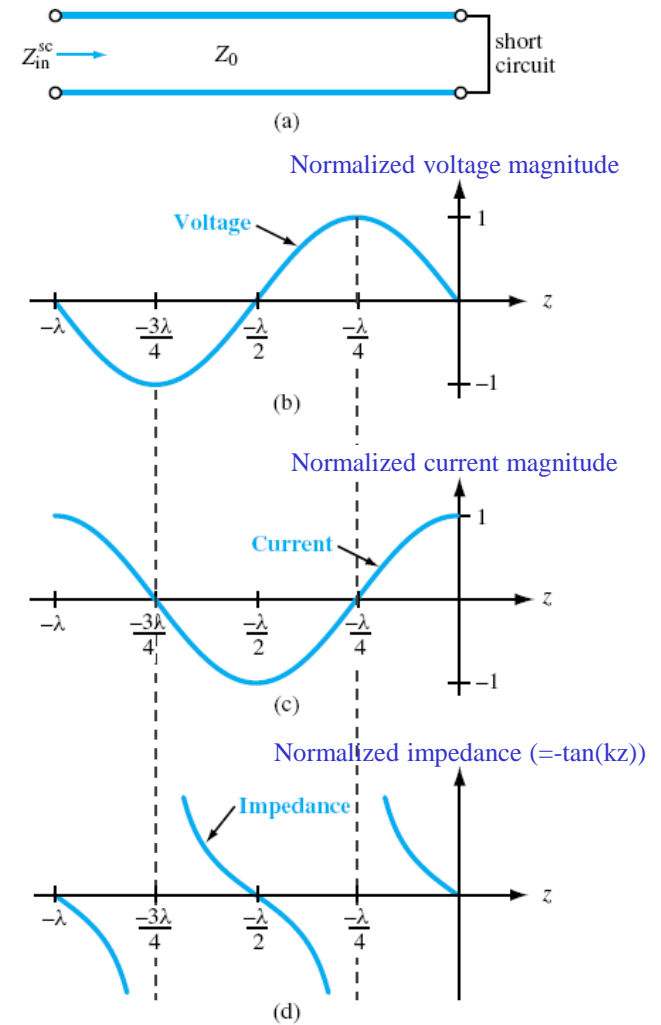


7.3 Open-circuited line

For an open circuit, $Z_L = \infty$. Then


$$Z_{\text{in}}^{\text{oc}} = -jZ_0 \cot(k\ell) = jZ_0 \cot(kz)$$

Note $\ell = -z$

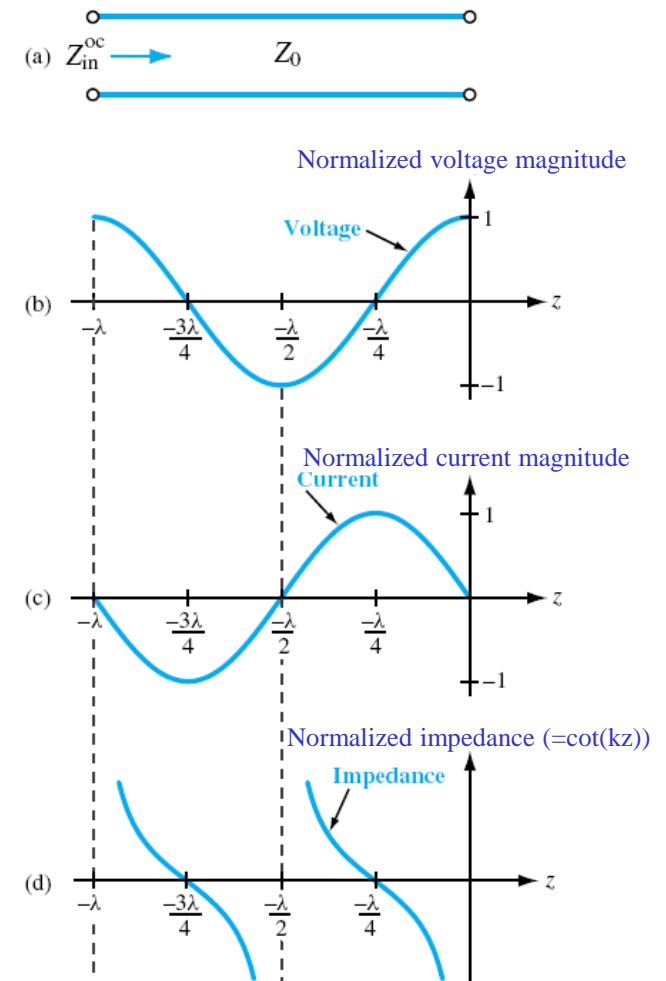

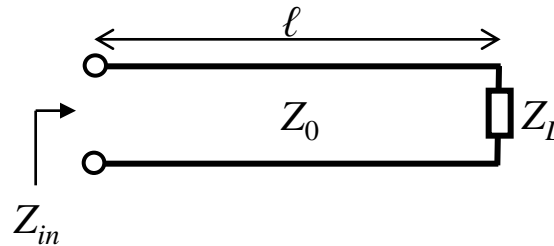
7.4 $\lambda/4$ transmission line terminated in Z_L

$$Z_{in} = Z(\ell = \lambda/4) = Z_0 \frac{Z_L + jZ_0 \tan(\pi/2)}{Z_0 + jZ_L \tan(\pi/2)} = \frac{Z_0^2}{Z_L}$$



7.5 $\lambda/2$ transmission line terminated in Z_L

$$Z_{in} = Z(\ell = \lambda/2) = Z_0 \frac{Z_L + jZ_0 \tan(\pi)}{Z_0 + jZ_L \tan(\pi)} = Z_L$$

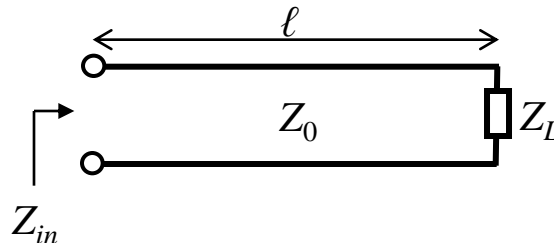

Example 4

The open-circuit and short-circuit impedances measured at the input terminals of a lossless transmission line of length 1.5 m (which is less than a quarter wavelength) are $-j54.6 \Omega$ and $j103 \Omega$, respectively.

- (a) Find Z_0 and k of the line.
- (b) Without changing the operating frequency, find the input impedance of a short-circuited line that is twice the given length.
- (c) How long should the short-circuited line be in order for it to appear as an open circuit at the input terminals?

Solution

The given quantities are

$$Z_{\text{in}}^{\text{oc}} = -j54.6 \, \Omega \quad Z_{\text{in}}^{\text{sc}} = j103 \, \Omega \quad \ell = 1.5 \text{m}$$

$$(a) \quad Z_{\text{in}}^{\text{sc}} = jZ_0 \tan(k\ell)$$

$$Z_{\text{in}}^{\text{oc}} = -jZ_0 \cot(k\ell)$$

$$Z_0 = \sqrt{Z_{\text{in}}^{\text{oc}} Z_{\text{in}}^{\text{sc}}} = 75 \, \Omega$$

$$k = \frac{1}{\ell} \tan^{-1} \sqrt{-Z_{\text{in}}^{\text{sc}} / Z_{\text{in}}^{\text{oc}}} = 0.628 \, \text{rad/m}$$

$$\lambda = \frac{2\pi}{k} = 10 \text{m}$$

(b) For a line twice as long, $\ell = 3 \text{ m}$ and $k\ell = 1.884 \text{ rad}$,

$$Z_{\text{in}}^{\text{sc}} = jZ_0 \tan k\ell = -j232 \, \Omega$$

(c) Short circuit input impedance

$$Z_{\text{in}}^{\text{sc}} = jZ_0 \tan(k\ell)$$

For open circuit $Z_{\text{in}}^{\text{sc}} = \infty$, $\Rightarrow k\ell = \pi/2 + n\pi$, $n = 0, 1, 2, \dots$

$$\ell = \frac{\pi/2 + n\pi}{k} = \frac{2n+1}{4} \lambda$$

□ Textbooks:

– *Fundamentals of Applied Electromagnetics*

F. T. Ulaby, E. Michielssen, U. Ravaioli,

Pearson Education, 2010, 6th edition

Suggested reading [textbook]:

- Page 62
- Section 2-2: Lumped-Element Model
- Section 2-3: Transmission Line Equations
- Section 2-4: Wave Propagation on a Transmission Line
- Section 2-6: The Lossless Transmission Line: General Considerations
- Section 2-7: Wave Impedance of the Lossless Line
- Section 2-8: Special Cases of the Lossless Line

Optional reading [textbook]:

- Section 2-1.1: The Role of Wavelength
- Section 2-1.2: Propagation Modes