

EE2011 Engineering Electromagnetics - Part CXD

Tutorial 1 - Solutions

Q1

(i) $\epsilon_r = 2.9$

$Z_0 = 75 \Omega$

$Z_L = 300 \Omega$

$l = 38 \text{ mm} = 0.038 \text{ m}$

since $u_p = \frac{\omega}{k} = \frac{c}{\sqrt{\epsilon_r}}$, we have

$$k = \frac{\omega}{c} \sqrt{\epsilon_r} = 71.33 \text{ rad/m}$$

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan(kl)}{Z_0 + jZ_L \tan(kl)} = 82.90 + j118.01 \Omega.$$

(ii)

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{300 - 75}{300 + 75} = 0.6 \angle 0^\circ = |\Gamma_L| e^{j\theta_L}$$

$$\therefore \theta_L = 0$$

$$\lambda = \text{wavelength along the coaxial line} = \frac{2\pi}{k} = \frac{2\pi}{71.33} = 88 \text{ mm}$$


$$\ell_M = \text{maximum voltage locations} = \frac{\theta_L \lambda}{4\pi} + \frac{n\lambda}{2} = 44n \text{ (mm)}, \quad n = 0, 1, 2, \dots$$

$$\ell_m = \text{maximum current locations}$$

$$= \text{minimum voltage locations}$$

$$= \frac{\theta_L \lambda}{4\pi} + \frac{(2n+1)\lambda}{4} = (22 + 44n) \text{ (mm)}, \quad n = 0, 1, 2, \dots$$

Note: the current maximum locations are shifted $\lambda/4 = 22 \text{ (mm)}$ from the voltage maximum locations.

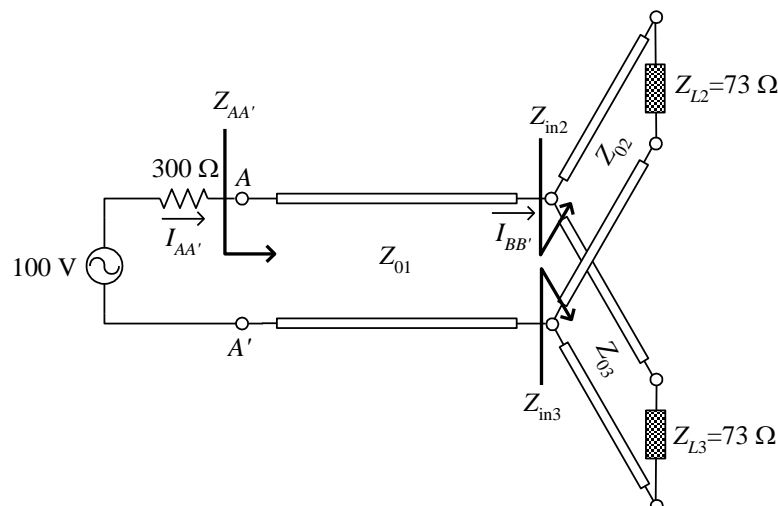Q2

$$Z_{in2} = Z_{02} \frac{Z_{L2} + jZ_{02} \tan(2\pi 3/8)}{Z_{02} + jZ_{L2} \tan(2\pi 3/8)} = 118.042 - j92.553 \Omega$$

$$Z_{in3} = Z_{03} \frac{Z_{L3} + jZ_{03} \tan(2\pi 3/8)}{Z_{03} + jZ_{L3} \tan(2\pi 3/8)} = 95.244 - j30.472 \Omega$$

Total impedance as seen from BB' :

$$Z_{BB'} = Z_{in2} // Z_{in3} = 54.818 - j26.575 \Omega$$

Total impedance as seen from AA' :

$$Z_{AA'} = Z_{01} \frac{Z_{BB'} + jZ_{01} \tan(2\pi 3/8)}{Z_{01} + jZ_{BB'} \tan(2\pi 3/8)} = 126.884 - j332.878 \Omega$$

$$\text{Total current at } AA': I_{AA'} = \frac{100 \angle 0^\circ}{300 + Z_{AA'}} = 0.1456 + j0.1136 = 0.1847 \angle 0.6623 \text{ A}$$

Average power supplied to transmission line at AA' :

$$P_{AA'} = \frac{1}{2} |I_{AA'}|^2 \text{Re}[Z_{AA'}] = \frac{1}{2} (0.1847)^2 (126.884) = 2.1643 \text{ W}.$$

Since transmission line 1 is lossless, the average power supplied to the parallel transmission lines at BB' is $P_{BB'} = P_{AA'} = 2.1643 \text{ W}$. The total average power supplied to the two antennas must therefore be equal to $P_{BB'}$, since transmission lines 2 and 3 are lossless.

But

$$P_{BB'} = \frac{1}{2} \text{Re}[V_{BB'} I_{BB'}^*] = \frac{1}{2} \text{Re}[V_{BB'} (V_{BB'}^* / Z_{BB'}^*)] = \frac{1}{2} |V_{BB'}|^2 \text{Re}[1/Z_{BB'}^*] = \frac{1}{2} |V_{BB'}|^2 (0.01477)$$

$$\rightarrow |V_{BB'}|^2 = 293.067$$

$$P_{L2} = \frac{1}{2} |V_{BB'}|^2 \text{Re}[1/Z_{in2}^*] = 0.7688 \text{ W}$$

$$P_{L3} = \frac{1}{2} |V_{BB'}|^2 \text{Re}[1/Z_{in3}^*] = 1.3956 \text{ W}$$

$$\text{Note that } P_{L2} + P_{L3} = P_{BB'} = 2.1643 \text{ W}$$

Q3

Let $T = \tan(kl) = \tan(2\pi l / \lambda)$.

$$Z_{in} = Z_0 \frac{(100 + j50) + jZ_0 T}{Z_0 + j(100 + j50)T} = \frac{100Z_0 + j(50Z_0 + Z_0^2 T)}{(Z_0 - 50T) + j100T} = 300 \Omega$$

$$\rightarrow 100Z_0 + j(50Z_0 + Z_0^2 T) = (300Z_0 - 15000T) + j30000T \quad \text{----- (*)}$$

Considering the real part of the above equation:

$$100Z_0 = 300Z_0 - 15000T \rightarrow Z_0 = 75T$$

Putting this condition into the imaginary part of equation (*),

$$50Z_0 + Z_0^2 T = 30000T \rightarrow 3750T + 5625T^3 = 30000T \rightarrow T = 2.1602$$

$$\text{Thus } \tan(2\pi l/\lambda) = 2.1602$$

$$\Rightarrow 2\pi l/\lambda = \tan^{-1}(2.1602) + n\pi, \quad n = 0, 1, 2, \dots$$

\Rightarrow The minimum (l/λ) corresponds to $n = 0$.

Hence,

$$l/\lambda = \frac{\tan^{-1}(2.1602)}{2\pi} = 0.181$$

and

$$Z_0 = 75T = 163.018 \, \Omega$$

Note: the wavelength λ here is the effective wavelength in the transmission line and is not the free space wavelength λ_0 .

Q4

(i)

Given:

$$Z_{in} = 12.5 - j12.7 \, \Omega$$

$$Z_L = 100 - j100 \, \Omega$$

$$Z_g = 50 \, \Omega$$

$$Z_0 = 50 \, \Omega$$

$$f = 10^9 \, \text{Hz/s}$$

To find the length l ,

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 T}{Z_0 + jZ_L T} \quad \text{where } T = \tan(\beta l)$$

$$\therefore T = \frac{-jZ_0(Z_L - Z_{in})}{Z_{in}Z_L - Z_0^2} = 1.7341$$

$$\beta l = 1.0477$$

$$\lambda = c/f = 0.3 \, \text{m} \quad \beta = 2\pi/\lambda = 20.944 \, \text{rad/m}$$

$$\therefore l = 0.05 \, \text{m} = 5 \, \text{cm}$$

(The length of the transmission line is $0.05/0.3 = 0.167\lambda$)

(ii)

$$v_g(t) = 5 \cos(2\pi \times 10^9 t)$$

$$V_g = 5 \angle 0^\circ$$

$$I_{\text{in}} = \frac{V_g}{Z_g + Z_{\text{in}}} = 0.0768 + j0.0156 = 0.0784 \angle 0.2005 \text{ A}$$

But looking at the input end ($\ell = l$) of the transmission line:

$$I_{\text{in}} = I(\ell = l) = \frac{I_L}{Z_0} [Z_0 \cos(\beta l) + jZ_L \sin(\beta l)] = I_L (2.2321 + j1.7326) \text{ A}$$

$$\therefore I_L = 0.0249 - j0.0123 = 0.0277 \angle -0.4597 \text{ A}$$

$$i_L(t) = \text{Re} \left[I_L e^{j2\pi \times 10^9 t} \right] = 0.0277 \cos(2\pi \times 10^9 t - 0.4597) \text{ A}$$