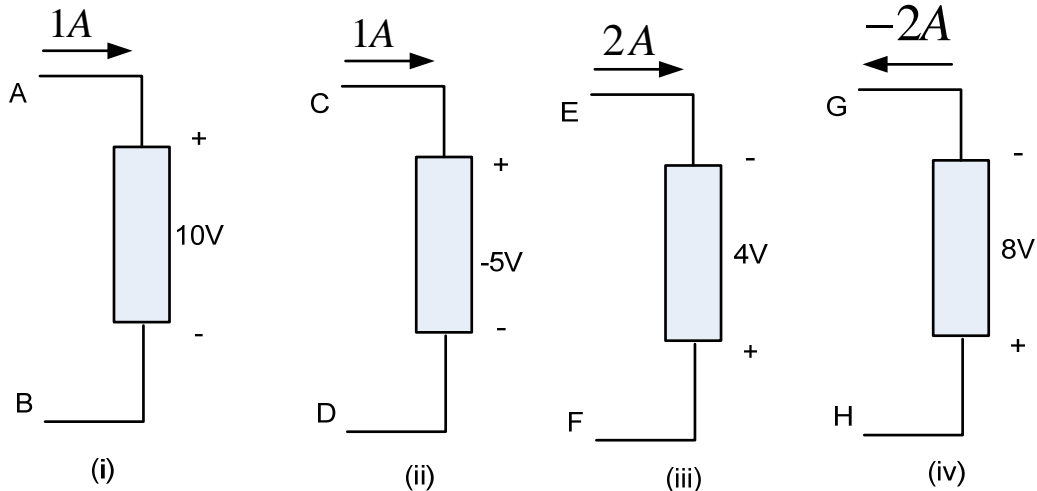



Extra Practice Questions

1) For the elements given below:




- a) State for which elements is Passive sign convention followed?
- b) Find the power associated with the each element.
- c) Which elements are passive?
- d) For each element, name the terminal that is at a higher voltage.

2) For the figure,

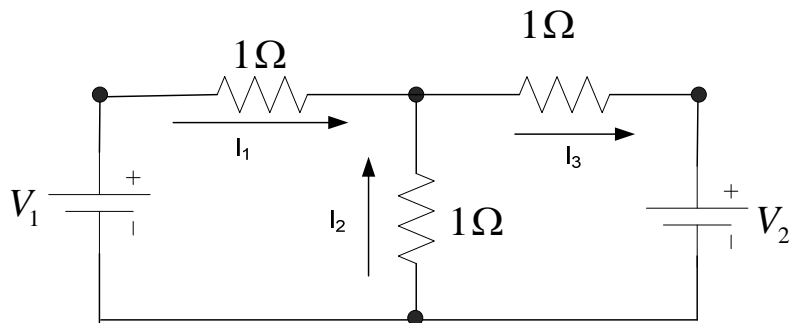


- a) Are the current directions for I_2 and I_3 correct?
- b) Can we conclude if the voltage source V_2 is taking power or giving power before solving the circuit?
- c) If $I_1 = -3A$, $I_2 = 4A$, find I_3 .
- d) If $V_1 = 10V$, find V_2 .

3) In the circuit given,

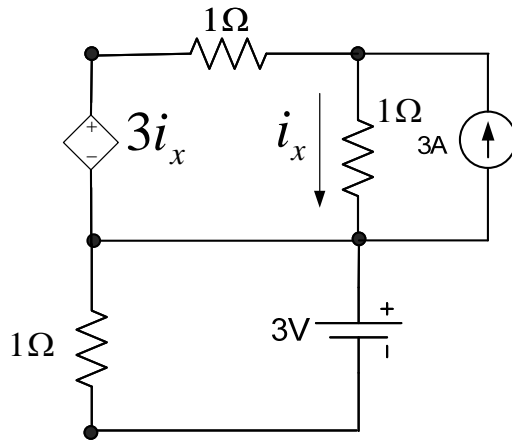

Use node voltage analysis to solve the circuit. Find the value of current i_x .

4) In the circuit given,

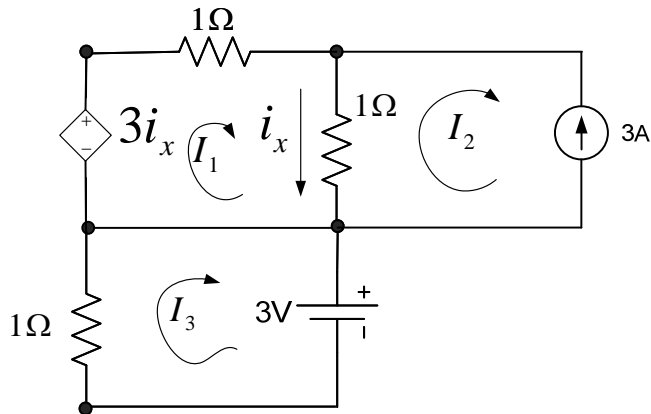


a) Find the values of I_1 , I_2 and I_3 .


b) Find the value of i_x .

c) What is the power associated with the current source?

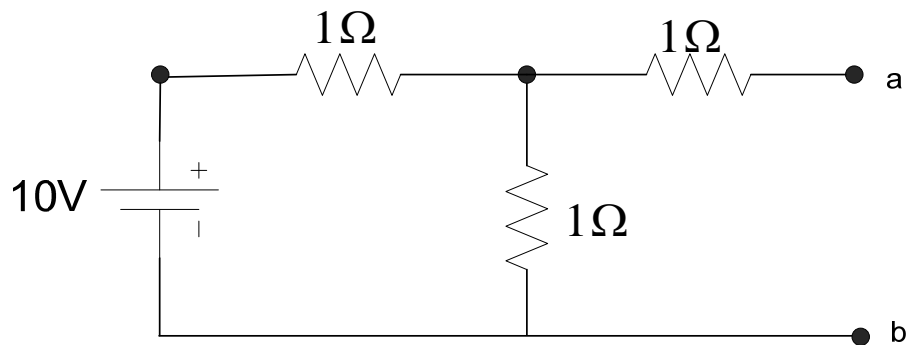- 5) In the circuit given, Find the Thevenin equivalent between terminals a and b.



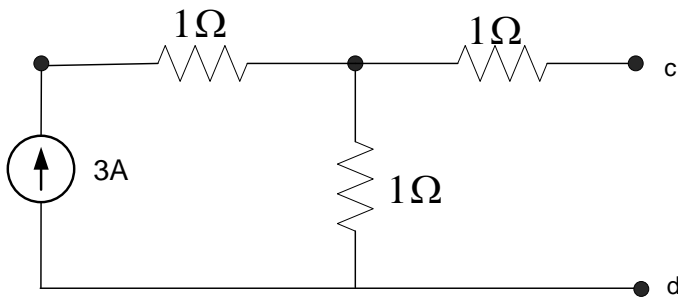- 6) Find the Norton equivalent of the circuit between points c and d.



- 7) Find the Thevenin equivalent of the circuit between terminals e and f.

