

## CHAPTER 6

### Exercises

**E6.1** (a) The frequency of  $v_{in}(t) = 2 \cos(2\pi \cdot 2000t)$  is 2000 Hz. For this frequency  $H(f) = 2\angle 60^\circ$ . Thus,  $V_{out} = H(f)V_{in} = 2\angle 60^\circ \times 2\angle 0^\circ = 4\angle 60^\circ$  and we have  $v_{out}(t) = 4 \cos(2\pi \cdot 2000t + 60^\circ)$ .

(b) The frequency of  $v_{in}(t) = \cos(2\pi \cdot 3000t - 20^\circ)$  is 3000 Hz. For this frequency  $H(f) = 0$ . Thus,  $V_{out} = H(f)V_{in} = 0 \times 2\angle 0^\circ = 0$  and we have  $v_{out}(t) = 0$ .

**E6.2** The input signal  $v(t) = 2 \cos(2\pi \cdot 500t + 20^\circ) + 3 \cos(2\pi \cdot 1500t)$  has two components with frequencies of 500 Hz and 1500 Hz. For the 500-Hz component we have:

$$V_{out,1} = H(500)V_{in} = 3.5\angle 15^\circ \times 2\angle 20^\circ = 7\angle 35^\circ$$

$$v_{out,1}(t) = 7 \cos(2\pi \cdot 500t + 35^\circ)$$

For the 1500-Hz component:

$$V_{out,2} = H(1500)V_{in} = 2.5\angle 45^\circ \times 3\angle 0^\circ = 7.5\angle 45^\circ$$

$$v_{out,2}(t) = 7.5 \cos(2\pi \cdot 1500t + 45^\circ)$$

Thus the output for both components is

$$v_{out}(t) = 7 \cos(2\pi \cdot 500t + 35^\circ) + 7.5 \cos(2\pi \cdot 1500t + 45^\circ)$$

**E6.3** The input signal  $v(t) = 1 + 2 \cos(2\pi \cdot 1000t) + 3 \cos(2\pi \cdot 3000t)$  has three components with frequencies of 0, 1000 Hz and 3000 Hz.

For the dc component, we have

$$v_{out,1}(t) = H(0) \times v_{in,1}(t) = 4 \times 1 = 4$$

For the 1000-Hz component, we have:

$$V_{out,2} = H(1000)V_{in,2} = 3\angle 30^\circ \times 2\angle 0^\circ = 6\angle 30^\circ$$

$$v_{out,2}(t) = 6 \cos(2\pi \cdot 1000t + 30^\circ)$$

For the 3000-Hz component:

$$V_{out,3} = H(3000)V_{in,3} = 0 \times 3\angle 0^\circ = 0$$

$$v_{out,3}(t) = 0$$

Thus, the output for all three components is

$$v_{out}(t) = 4 + 6 \cos(2\pi \cdot 1000t + 30^\circ)$$

**E6.4** Using the voltage-division principle, we have:

$$V_{\text{out}} = V_{\text{in}} \times \frac{R}{R + j2\pi fL}$$

Then the transfer function is:

$$H(f) = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{R}{R + j2\pi fL} = \frac{1}{1 + j2\pi fL/R} = \frac{1}{1 + jf/f_B}$$

**E6.5** From Equation 6.9, we have  $f_B = 1/(2\pi RC) = 200 \text{ Hz}$ , and from Equation

$$6.9, \text{ we have } H(f) = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{1}{1 + jf/f_B}.$$

For the first component of the input, the frequency is 20 Hz,

$$H(f) = 0.995 \angle -5.71^\circ, \quad V_{\text{in}} = 10 \angle 0^\circ, \text{ and } V_{\text{out}} = H(f)V_{\text{in}} = 9.95 \angle -5.71^\circ$$

Thus the first component of the output is

$$v_{\text{out},1}(t) = 9.95 \cos(40\pi t - 5.71^\circ)$$

For the second component of the input, the frequency is 500 Hz,

$$H(f) = 0.371 \angle -68.2^\circ, \quad V_{\text{in}} = 5 \angle 0^\circ, \text{ and } V_{\text{out}} = H(f)V_{\text{in}} = 1.86 \angle -68.2^\circ$$

Thus the second component of the output is

$$v_{\text{out},2}(t) = 1.86 \cos(40\pi t - 68.2^\circ)$$

For the third component of the input, the frequency is 10 kHz,

$$H(f) = 0.020 \angle -88.9^\circ, \quad V_{\text{in}} = 5 \angle 0^\circ, \text{ and } V_{\text{out}} = H(f)V_{\text{in}} = 0.100 \angle -88.9^\circ$$

Thus the third component of the output is

$$v_{\text{out},3}(t) = 0.100 \cos(2\pi \times 10^4 t - 88.9^\circ)$$

Finally, the output with for all three components is:

$$v_{\text{out}}(t) = 9.95 \cos(40\pi t - 5.71^\circ) + 1.86 \cos(40\pi t - 68.2^\circ) \\ + 0.100 \cos(2\pi \times 10^4 t - 88.9^\circ)$$

**E6.6**  $|H(f)|_{\text{dB}} = 20 \log|H(f)| = 20 \log(50) = 33.98 \text{ dB}$

**E6.7** (a)  $|H(f)|_{\text{dB}} = 20 \log|H(f)| = 15 \text{ dB}$

$$\log|H(f)| = 15/20 = 0.75$$

$$H(f) = 10^{0.75} = 5.623$$

$$\begin{aligned} \text{(b)} \quad |H(f)|_{\text{dB}} &= 20 \log |H(f)| = 30 \text{ dB} \\ \log |H(f)| &= 30/20 = 1.5 \\ H(f) &= 10^{1.5} = 31.62 \end{aligned}$$

- E6.8**
- (a)  $1000 \times 2^2 = 4000 \text{ Hz}$  is two octaves higher than 1000 Hz.
  - (b)  $1000 / 2^3 = 125 \text{ Hz}$  is three octaves lower than 1000 Hz.
  - (c)  $1000 \times 10^2 = 100 \text{ kHz}$  is two decades higher than 1000 Hz.
  - (d)  $1000 / 10 = 100 \text{ Hz}$  is one decade lower than 1000 Hz.

- E6.9**
- (a) To find the frequency halfway between two frequencies on a logarithmic scale, we take the logarithm of each frequency, average the logarithms, and then take the antilogarithm. Thus

$$f = 10^{[\log(100) + \log(1000)]/2} = 10^{2.5} = 316.2 \text{ Hz}$$

is half way between 100 Hz and 1000 Hz on a logarithmic scale.

(b) To find the frequency halfway between two frequencies on a linear scale, we simply average the two frequencies. Thus  $(100 + 1000)/2 = 550 \text{ Hz}$  is halfway between 100 and 1000 Hz on a linear scale.

- E6.10** To determine the number of decades between two frequencies we take the difference between the common (base-ten) logarithms of the two frequencies. Thus 20 Hz and 15 kHz are  $\log(15 \times 10^3) - \log(20) = 2.875$  decades apart.

Similarly, to determine the number of octaves between two frequencies we take the difference between the base-two logarithms of the two frequencies. One formula for the base-two logarithm of  $z$  is

$$\log_2(z) = \frac{\log(z)}{\log(2)} \cong 3.322 \log(z)$$

Thus the number of octaves between 20 Hz and 15 kHz is

$$\frac{\log(15 \times 10^3)}{\log(2)} - \frac{\log(20)}{\log(2)} = 9.551$$

- E6.11** The transfer function for the circuit shown in Figure 6.17 in the book is

$$H(f) = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{1/(j2\pi fC)}{R + 1/(j2\pi fC)} = \frac{1}{1 + j2\pi RCf} = \frac{1}{1 + jf/f_b}$$

in which  $f_B = 1/(2\pi RC) = 1000$  Hz. Thus the magnitude plot is approximated by 0 dB below 1000 Hz and by a straight line sloping downward at 20 dB/decade above 1000 Hz. This is shown in Figure 6.18a in the book.

The phase plot is approximated by  $0^\circ$  below 100 Hz, by  $-90^\circ$  above 10 kHz and by a line sloping downward between  $0^\circ$  at 100 Hz and  $-90^\circ$  at 10 kHz. This is shown in Figure 6.18b in the book.

- E6.12** Using the voltage division principle, the transfer function for the circuit shown in Figure 6.19 in the book is

$$H(f) = \frac{V_{out}}{V_{in}} = \frac{R}{R + 1/(j2\pi fC)} = \frac{j2\pi RC}{1 + j2\pi RCf} = \frac{j(f/f_B)}{1 + j(f/f_B)}$$

in which  $f_B = 1/(2\pi RC)$ .

- E6.13** Using the voltage division principle, the transfer function for the circuit shown in Figure 6.22 in the book is

$$H(f) = \frac{V_{out}}{V_{in}} = \frac{j2\pi fL}{R + j2\pi fL} = \frac{j2\pi fL/R}{1 + j2\pi fL/R} = \frac{j(f/f_B)}{1 + j(f/f_B)}$$

in which  $f_B = R/(2\pi L)$ .

- E6.14** A first-order filter has a transfer characteristic that decreases by 20 dB/decade below the break frequency. To attain an attenuation of 50 dB the signal frequency must be  $50/20 = 2.5$  decades below the break frequency. 2.5 decades corresponds to a frequency ratio of  $10^{2.5} = 316.2$ . Thus to attenuate a 1000 Hz signal by 50 dB the high-pass filter must have a break frequency of 316.2 kHz. Solving Equation 6.22 for capacitance and substituting values, we have

$$C = \frac{1}{2\pi f_B R} = \frac{1}{2\pi \times 1000 \times 316.2 \times 10^3} = 503.3 \text{ pF}$$

- E6.15**  $C = \frac{1}{\omega_0^2 L} = \frac{1}{(2\pi f_0)^2 L} = \frac{1}{(2\pi 10^6)^2 10 \times 10^{-6}} = 2533 \text{ pF}$

$$R = \omega_0 L / Q_s = 1.257 \Omega$$

$$B = f_0 / Q_s = 20 \text{ kHz}$$

$$f_L \cong f_0 - B/2 = 990 \text{ kHz}$$

$$f_H \cong f_0 + B/2 = 1010 \text{ kHz}$$

**E6.16** At resonance we have

$$\mathbf{V}_R = \mathbf{V}_s = 1\angle 0^\circ$$

$$\mathbf{V}_L = j\omega_0 L \mathbf{I} = j\omega_0 L \mathbf{V}_s / R = jQ_s \mathbf{V}_s = 50\angle 90^\circ \text{ V}$$

$$\mathbf{V}_C = (1 / j\omega_0 C) \mathbf{I} = (1 / j\omega_0 C) \mathbf{V}_s / R = -jQ_s \mathbf{V}_s = 50\angle -90^\circ \text{ V}$$

**E6.17** 
$$L = \frac{1}{\omega_0^2 C} = \frac{1}{(2\pi f_0)^2 C} = \frac{1}{(2\pi \times 5 \times 10^6)^2 470 \times 10^{-12}} = 2.156 \mu\text{H}$$

$$Q_s = f_0 / B = (5 \times 10^6) / (200 \times 10^3) = 25$$

$$R = \frac{1}{\omega_0 C Q_s} = \frac{1}{2\pi \times 5 \times 10^6 \times 470 \times 10^{-12} \times 25} = 2.709 \Omega$$

**E6.18** 
$$f_0 = \frac{1}{2\pi\sqrt{LC}} = 711.8 \text{ kHz} \quad Q_p = \frac{R}{\omega_0 L} = 22.36 \quad B = f_0 / Q_p = 31.83 \text{ kHz}$$

**E6.19** 
$$Q_p = f_0 / B = 50 \quad L = \frac{R}{\omega_0 Q_p} = 0.3183 \mu\text{H} \quad C = \frac{Q_p}{\omega_0 R} = 795.8 \text{ pF}$$

**E6.20** A second order lowpass filter with  $f_0 = 5 \text{ kHz}$  is needed. The circuit configuration is shown in Figure 6.34a in the book. The normalized transfer function is shown in Figure 6.34c. Usually we would want a filter without peaking and would design for  $Q = 1$ . Given that  $L = 5 \text{ mH}$ , the other component values are

$$R = \frac{2\pi f_0 L}{Q} = 157.1 \Omega \quad C = \frac{1}{(2\pi f_0)^2 L} = 0.2026 \mu\text{F}$$

The circuit is shown in Figure 6.39 in the book.

**E6.21** We need a bandpass filter with  $f_L = 45 \text{ kHz}$  and  $f_H = 55 \text{ kHz}$ . Thus we have

$$f_0 \cong \frac{f_L + f_H}{2} = 50 \text{ kHz} \quad B = f_H - f_L = 10 \text{ kHz} \quad Q = f_0 / B = 5$$

$$R = \frac{2\pi f_0 L}{Q} = 62.83 \Omega \quad C = \frac{1}{(2\pi f_0)^2 L} = 10.13 \text{ nF}$$

The circuit is shown in Figure 6.40 in the book.

**E6.22** The files Example\_6\_8 and Example\_6\_9 can be found in the MATLAB folder on the OrCAD disk. The results should be similar to Figures 6.42 and 6.44.

**E6.23** (a) Rearranging Equation 6.56, we have

$$\frac{\tau}{T} = \frac{a}{1-a} = \frac{0.9}{1-0.9} = 0.9$$

Thus we have  $\tau = 9T$ .

(b) From Figure 6.49 in the book we see that the step response of the digital filter reaches 0.632 at approximately  $n = 9$ . Thus the speed of response of the  $RC$  filter and the corresponding digital filter are comparable.

**E6.24** Writing a current equation at the node joining the resistance and capacitance, we have

$$\frac{y(t)}{R} + C \frac{d[y(t) - x(t)]}{dt} = 0$$

Multiplying both sides by  $R$  and using the fact that the time constant is  $\tau = RC$ , we have

$$y(t) + \tau \frac{dy(t)}{dt} - \tau \frac{dx(t)}{dt} = 0$$

Next we approximate the derivatives as

$$\frac{dx(t)}{dt} \cong \frac{\Delta x}{\Delta t} = \frac{x(n) - x(n-1)}{T} \quad \text{and} \quad \frac{dy(t)}{dt} \cong \frac{\Delta y}{\Delta t} = \frac{y(n) - y(n-1)}{T}$$

which yields

$$y(n) + \tau \frac{y(n) - y(n-1)}{T} - \tau \frac{x(n) - x(n-1)}{T} = 0$$

Solving for  $y(n)$ , we obtain

$$y(n) = a_1 y(n-1) + b_0 x(n) + b_1 x(n-1)$$

in which

$$a_1 = b_0 = -b_1 = \frac{\tau/T}{1 + \tau/T}$$

**E6.25** (a) Solving Equation 6.58 for  $d$  and substituting values, we obtain

$$d = \frac{f_s}{2f_{notch}} = \frac{10^4}{2 \times 500} = 10$$

(b) Repeating for  $f_{notch} = 300$  Hz, we have

$$d = \frac{f_s}{2f_{\text{notch}}} = \frac{10^4}{2 \times 300} = 16.67$$

However,  $d$  is required to be an integer value so we cannot obtain a notch filter for 300 Hz exactly for this sampling frequency. (Possibly other more complex filters could provide the desired performance.)

### Answers for Selected Problems



**P6.8\***  $v_{out}(t) = 10 + 3.5 \cos(2\pi 2500t - 15^\circ) + 2.5 \cos(2\pi 7500t - 135^\circ)$

**P6.11\***  $H(5000) = 0.5 \angle 45^\circ$

**P6.12\***  $f = 250 \text{ Hz}$   $H(250) = \frac{V_{out}}{V_{in}} = 3 \angle -45^\circ$

**P6.13\***  $v_o(t) = 2$

**P6.14\***  $H(f) = \frac{-j}{2\pi f}$

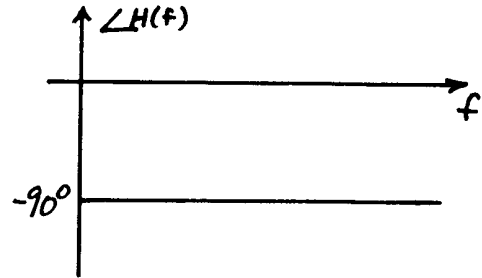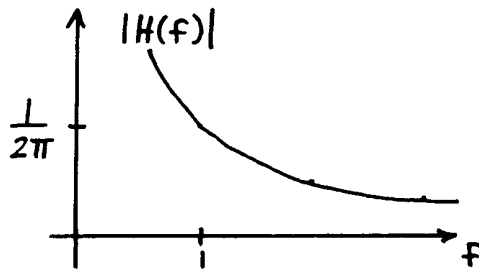

**P6.23\*** For  $\angle H(f) = -1^\circ$ , we have  $f = 0.01746f_B$ .


For  $\angle H(f) = -10^\circ$ , we have  $f = 0.1763f_B$ .

For  $\angle H(f) = -89^\circ$ , we have  $f = 57.29f_B$ .

**P6.25\***  $v_{out}(t) = 4.472 \cos(500\pi t - 26.57^\circ) + 3.535 \cos(1000\pi t - 45^\circ) + 2.236 \cos(2000\pi t - 63.43^\circ)$

P6.30\*  $f_B = 11.94 \text{ Hz}$
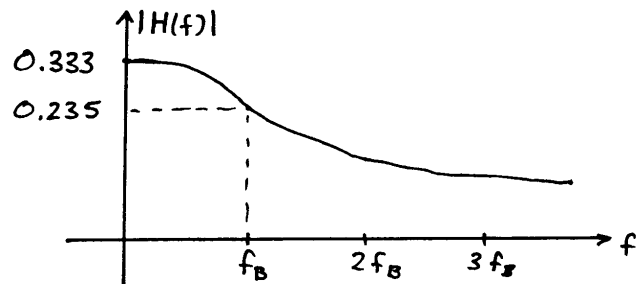
$$\frac{V_{out}}{V_{in}} = \frac{1/3}{1 + j(f/f_B)}$$




P6.40\* (a)  $|H(f)| = 0.3162$  (b)  $|H(f)| = 3.162$

P6.41\* (a) 547.7 Hz (b) 1550 Hz


P6.46\* (a)  $H(f) = \frac{1}{[1 + j(f/f_B)]^2}$  (b)  $f_{3dB} = 0.6436 f_B$

P6.52\*

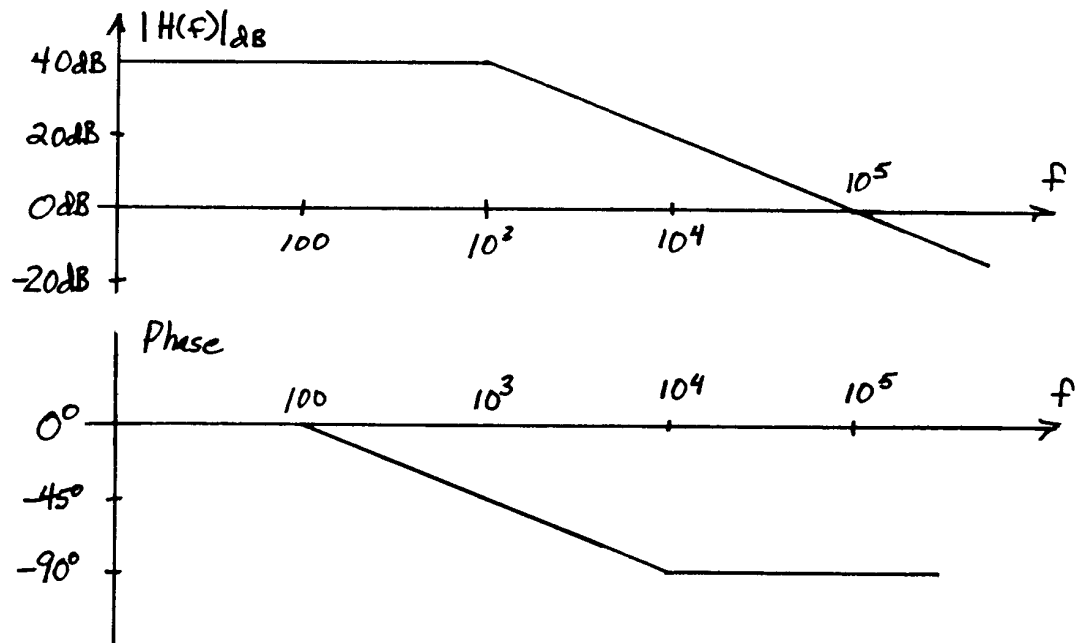




P6.60\*

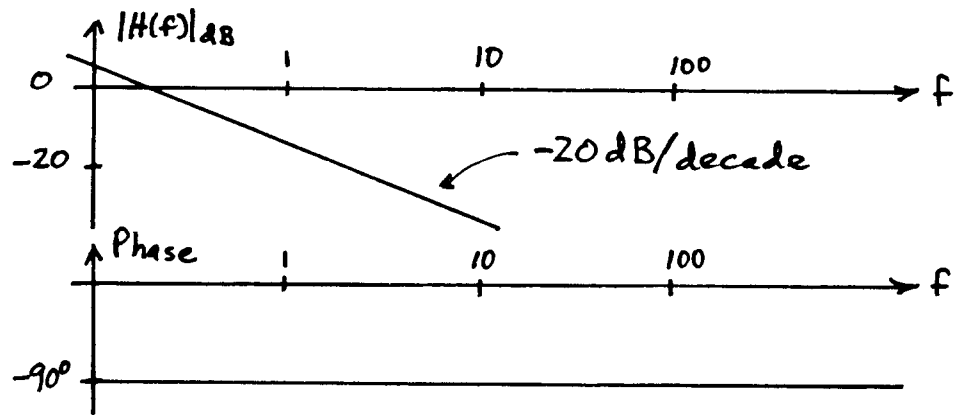

P6.64\*

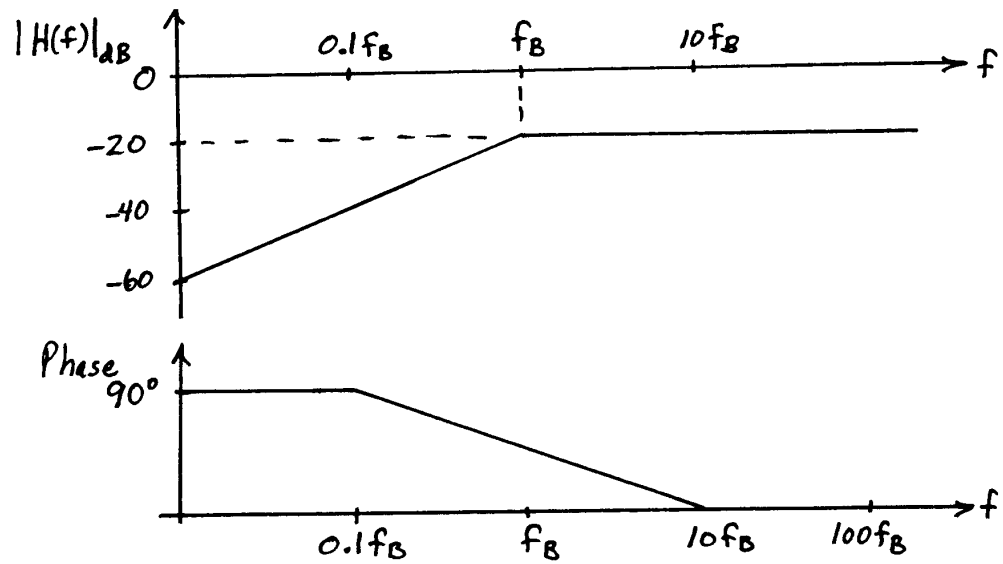

P6.65\*  $v_{out}(t) = 3.536 \cos(2000\pi t + 45^\circ)$

P6.72\*


$$\begin{aligned} f_0 &= 1.125 \text{ MHz} \\ Q_s &= 10 \\ B &= 112.5 \text{ kHz} \\ f_H &\cong 1.181 \text{ MHz} \\ f_L &\cong 1.069 \text{ MHz} \end{aligned}$$

$$\begin{aligned} V_L &= 10 \angle 90^\circ \\ V_R &= 1 \angle 0^\circ \\ V_C &= 10 \angle -90^\circ \end{aligned}$$


P6.75\*  $L = 79.57 \mu\text{H}$      $V_C = 20 \angle -90^\circ$   
 $C = 318.3 \text{ pF}$

P6.79\*  $f_0 = 1.592 \text{ MHz}$   
 $Q_p = 10.00$   
 $B = 159.2 \text{ kHz}$


P6.84\* Bandpass filter:

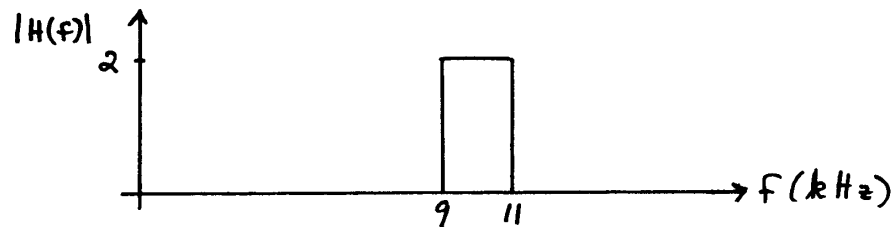

Band-reject filter:

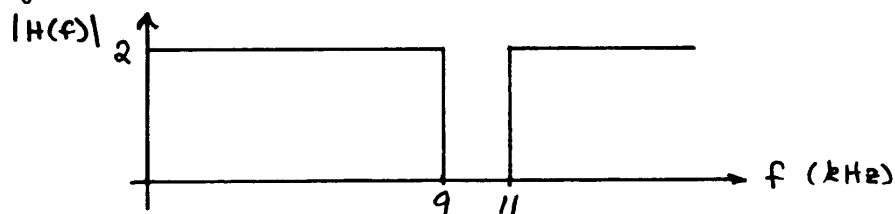

P6.88\*

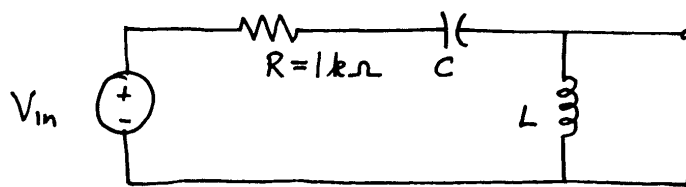

$L = 1.592 \text{ mH}$      $C = 1592 \text{ pF}$

P6.104\*  $L = \frac{Q_s}{\omega_0}$     and     $C = \frac{1}{\omega_0 Q_s}$

$$y(n) = \frac{\omega_0 T + 2Q_s}{Q_s + \omega_0^2 T^2 Q_s + \omega_0 T} y(n-1) - \frac{Q_s}{Q_s + \omega_0^2 T^2 Q_s + \omega_0 T} y(n-2) + \frac{\omega_0 T}{Q_s + \omega_0^2 T^2 Q_s + \omega_0 T} [x(n) - x(n-1)]$$

## Practice Test

**T6.1** All real-world signals (which are usually time-varying currents or voltages) are sums of sinewaves of various frequencies, amplitudes, and phases. The transfer function of a filter is a function of frequency that shows how the amplitudes and phases of the input components are altered to produce the output components.

**T6.2** Applying the voltage-division principle, we have:

$$H(f) = \frac{V_{out}}{V_{in}} = \frac{j2\pi fL}{R + j2\pi fL} = \frac{j2\pi fL/R}{1 + j2\pi fL/R} = \frac{j(f/f_B)}{1 + j(f/f_B)}$$

in which  $f_B = R/2\pi L = 1000$  Hz. The input signal has components with frequencies of 0 (dc), 500 Hz, and 1000 Hz. The transfer function values for these frequencies are:  $H(0) = 0$ ,  $H(500) = 0.4472\angle 63.43^\circ$ , and  $H(1000) = 0.7071\angle 45^\circ$ . Applying the transfer function values to each of the input components, we have  $H(0) \times 3 = 0$ ,  $H(500) \times 4\angle 0^\circ = 1.789\angle 63.43^\circ$ , and  $H(1000) \times 5\angle -30^\circ = 3.535\angle 15^\circ$ . Thus, the output is

$$v_{out}(t) = 1.789 \cos(1000\pi t - 63.43^\circ) + 3.535 \cos(2000\pi t + 15^\circ)$$

**T6.3** (a) The slope of the low-frequency asymptote is +20 dB/decade.  
 (b) The slope of the high-frequency asymptote is zero.  
 (c) The coordinates at which the asymptotes meet are  $20\log(50) = 34$  dB and 200 Hz.  
 (d) This is a first-order highpass filter.  
 (e) The break frequency is 200 Hz.

**T6.4** (a)  $f_0 = \frac{1}{2\pi\sqrt{LC}} = 1125 \text{ Hz}$

(b)  $Q_s = \frac{2\pi f_0 L}{R} = 28.28$

(c)  $B = \frac{f_0}{Q_s} = 39.79 \text{ Hz}$

(d) At resonance, the impedance equals the resistance, which is  $5 \Omega$ .

(e) At dc, the capacitance becomes an open circuit so the impedance is infinite.

(f) At infinite frequency the inductance becomes an open circuit, so the impedance is infinite.

**T6.5** (a)  $f_0 = \frac{1}{2\pi\sqrt{LC}} = 159.2 \text{ kHz}$

(b)  $Q_p = \frac{R}{2\pi f_0 L} = 10.00$

(c)  $B = \frac{f_0}{Q_p} = 15.92 \text{ kHz}$

(d) At resonance, the impedance equals the resistance which is  $10 \text{ k}\Omega$ .

(e) At dc, the inductance becomes a short circuit, so the impedance is zero.

(f) At infinite frequency the capacitance becomes a short circuit, so the impedance is zero.

**T6.6** (a) This is a first-order circuit because there is a single energy-storage element ( $L$  or  $C$ ). At very low frequencies, the capacitance approaches an open circuit, the current is zero,  $V_{\text{out}} = V_{\text{in}}$  and  $|H| = 1$ . At very high frequencies, the capacitance approaches a short circuit,  $V_{\text{out}} = 0$ , and  $|H| = 0$ . Thus, we have a first-order lowpass filter.

(b) This is a second-order circuit because there are two energy-storage elements ( $L$  or  $C$ ). At very low frequencies, the capacitance approaches an open circuit, the inductance approaches a short circuit, the current is zero,  $V_{\text{out}} = V_{\text{in}}$  and  $|H| = 1$ . At very high frequencies, the inductance approaches an open circuit, the capacitance approaches a short circuit,  $V_{\text{out}} = 0$ , and  $|H| = 0$ . Thus we have a second-order lowpass filter.

(c) This is a second-order circuit because there are two energy-storage elements ( $L$  or  $C$ ). At very low frequencies, the inductance approaches a short circuit,  $V_{out} = V_{in}$  and  $|H| = 1$ . At very high frequencies, the capacitance approaches a short circuit,  $V_{out} = V_{in}$  and  $|H| = 1$ . At the resonant frequency, the  $LC$  combination becomes an open circuit, the current is zero,  $V_{out} = 0$ , and  $|H| = 0$ . Thus, we have a second-order band-reject (or notch) filter.

(d) This is a first-order circuit because there is a single energy-storage element ( $L$  or  $C$ ). At very low frequencies, the inductance approaches a short circuit,  $V_{out} = 0$ , and  $|H| = 0$ . At very high frequencies the inductance approaches an open circuit, the current is zero,  $V_{out} = V_{in}$  and  $|H| = 1$ . Thus we have a first-order highpass filter.

**T6.7** One set of commands is:

```
f = logspace(1,4,400);
H = 50*i*(f/200)./(1+i*f/200);
semilogx(f,20*log10(abs(H)))
```

Other sets of commands are also correct. You can use MATLAB to see if your commands give a plot equivalent to:

