


**Problem 2.1** A transmission line of length  $l$  connects a load to a sinusoidal voltage source with an oscillation frequency  $f$ . Assuming the velocity of wave propagation on the line is  $c$ , for which of the following situations is it reasonable to ignore the presence of the transmission line in the solution of the circuit:

- (a)  $l = 20 \text{ cm}$ ,  $f = 20 \text{ kHz}$ ,
- (b)  $l = 50 \text{ km}$ ,  $f = 60 \text{ Hz}$ ,
- (c)  $l = 20 \text{ cm}$ ,  $f = 600 \text{ MHz}$ ,
- (d)  $l = 1 \text{ mm}$ ,  $f = 100 \text{ GHz}$ .

**Solution:** A transmission line is negligible when  $l/\lambda \leq 0.01$ .

- (a)  $\frac{l}{\lambda} = \frac{lf}{u_p} = \frac{(20 \times 10^{-2} \text{ m}) \times (20 \times 10^3 \text{ Hz})}{3 \times 10^8 \text{ m/s}} = 1.33 \times 10^{-5} \text{ (negligible).}$
  - (b)  $\frac{l}{\lambda} = \frac{lf}{u_p} = \frac{(50 \times 10^3 \text{ m}) \times (60 \times 10^0 \text{ Hz})}{3 \times 10^8 \text{ m/s}} = 0.01 \text{ (borderline).}$
  - (c)  $\frac{l}{\lambda} = \frac{lf}{u_p} = \frac{(20 \times 10^{-2} \text{ m}) \times (600 \times 10^6 \text{ Hz})}{3 \times 10^8 \text{ m/s}} = 0.40 \text{ (nonnegligible).}$
  - (d)  $\frac{l}{\lambda} = \frac{lf}{u_p} = \frac{(1 \times 10^{-3} \text{ m}) \times (100 \times 10^9 \text{ Hz})}{3 \times 10^8 \text{ m/s}} = 0.33 \text{ (nonnegligible).}$
-

**Problem 2.3** Show that the transmission line model shown in Fig. P2.3 yields the same telegrapher's equations given by Eqs. (2.14) and (2.16).

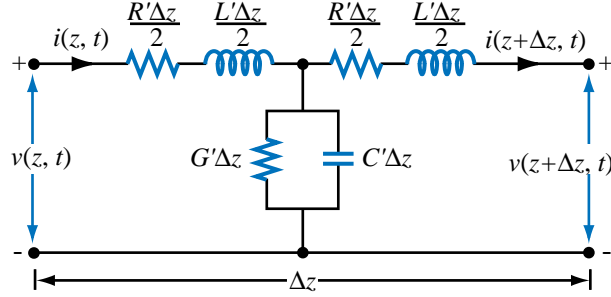

**Figure P2.3:** Transmission line model.

**Solution:** The voltage at the central upper node is the same whether it is calculated from the left port or the right port:

$$\begin{aligned} v(z + \tfrac{1}{2}\Delta z, t) &= v(z, t) - \tfrac{1}{2}R'\Delta z i(z, t) - \tfrac{1}{2}L'\Delta z \frac{\partial}{\partial t} i(z, t) \\ &= v(z + \Delta z, t) + \tfrac{1}{2}R'\Delta z i(z + \Delta z, t) + \tfrac{1}{2}L'\Delta z \frac{\partial}{\partial t} i(z + \Delta z, t). \end{aligned}$$

Recognizing that the current through the  $G' \parallel C'$  branch is  $i(z, t) - i(z + \Delta z, t)$  (from Kirchhoff's current law), we can conclude that

$$i(z, t) - i(z + \Delta z, t) = G'\Delta z v(z + \tfrac{1}{2}\Delta z, t) + C'\Delta z \frac{\partial}{\partial t} v(z + \tfrac{1}{2}\Delta z, t).$$

From both of these equations, the proof is completed by following the steps outlined in the text, ie. rearranging terms, dividing by  $\Delta z$ , and taking the limit as  $\Delta z \rightarrow 0$ .

---

**Problem 2.4** A 1-GHz parallel-plate transmission line consists of 1.2-cm-wide copper strips separated by a 0.15-cm-thick layer of polystyrene. Appendix B gives  $\mu_c = \mu_0 = 4\pi \times 10^{-7}$  (H/m) and  $\sigma_c = 5.8 \times 10^7$  (S/m) for copper, and  $\epsilon_r = 2.6$  for polystyrene. Use Table 2-1 to determine the line parameters of the transmission line. Assume  $\mu = \mu_0$  and  $\sigma \simeq 0$  for polystyrene.

**Solution:**

$$R' = \frac{2R_s}{w} = \frac{2}{w} \sqrt{\frac{\pi f \mu_c}{\sigma_c}} = \frac{2}{1.2 \times 10^{-2}} \left( \frac{\pi \times 10^9 \times 4\pi \times 10^{-7}}{5.8 \times 10^7} \right)^{1/2} = 1.38 \quad (\Omega/\text{m}),$$

$$L' = \frac{\mu d}{w} = \frac{4\pi \times 10^{-7} \times 1.5 \times 10^{-3}}{1.2 \times 10^{-2}} = 1.57 \times 10^{-7} \quad (\text{H}/\text{m}),$$

$$G' = 0 \quad \text{because } \sigma = 0,$$

$$C' = \frac{\epsilon w}{d} = \epsilon_0 \epsilon_r \frac{w}{d} = \frac{10^{-9}}{36\pi} \times 2.6 \times \frac{1.2 \times 10^{-2}}{1.5 \times 10^{-3}} = 1.84 \times 10^{-10} \quad (\text{F}/\text{m}).$$


---

**Problem 2.13** In addition to not dissipating power, a lossless line has two important features: (1) it is dispersionless ( $\mu_p$  is independent of frequency) and (2) its characteristic impedance  $Z_0$  is purely real. Sometimes, it is not possible to design a transmission line such that  $R' \ll \omega L'$  and  $G' \ll \omega C'$ , but it is possible to choose the dimensions of the line and its material properties so as to satisfy the condition

$$R'C' = L'G' \quad (\text{distortionless line}).$$

Such a line is called a *distortionless* line because despite the fact that it is not lossless, it does nonetheless possess the previously mentioned features of the loss line. Show that for a distortionless line,

$$\alpha = R' \sqrt{\frac{C'}{L'}} = \sqrt{R'G'}, \quad \beta = \omega \sqrt{L'C'}, \quad Z_0 = \sqrt{\frac{L'}{C'}}.$$

**Solution:** Using the distortionless condition in Eq. (2.22) gives

$$\begin{aligned} \gamma &= \alpha + j\beta = \sqrt{(R' + j\omega L')(G' + j\omega C')} \\ &= \sqrt{L'C'} \sqrt{\left(\frac{R'}{L'} + j\omega\right) \left(\frac{G'}{C'} + j\omega\right)} \\ &= \sqrt{L'C'} \sqrt{\left(\frac{R'}{L'} + j\omega\right) \left(\frac{R'}{L'} + j\omega\right)} \\ &= \sqrt{L'C'} \left(\frac{R'}{L'} + j\omega\right) = R' \sqrt{\frac{C'}{L'}} + j\omega \sqrt{L'C'}. \end{aligned}$$

From  $R'C' = L'G'$ ,  
we get  
 $R'/L' = G'/C'$

Hence,

$$\alpha = \Re(\gamma) = R' \sqrt{\frac{C'}{L'}}, \quad \beta = \Im(\gamma) = \omega \sqrt{L'C'}, \quad u_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{L'C'}}.$$

Similarly, using the distortionless condition in Eq. (2.29) gives

$$Z_0 = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} = \sqrt{\frac{L'}{C'}} \sqrt{\frac{R'/L' + j\omega}{G'/C' + j\omega}} = \sqrt{\frac{L'}{C'}}.$$


---

**Problem 2.12** Generate a plot of  $Z_0$  as a function of strip width  $w$ , over the range from 0.05 mm to 5 mm, for a microstrip line fabricated on a 0.7-mm-thick substrate with  $\epsilon_r = 9.8$ .

**Solution:**

