


EE1002 AY2010/11 Sem1

Tutorial 6

1. The current through a 0.5 H inductor is given by $i_L(t) = 2 \cos(377t + \pi/6)$.
 - a. What is the impedance of the inductor?
 - b. Write the expression for the voltage across the inductor.
 - c. Write the phasors for the inductor voltage and current?
 - d. Draw the phasor diagram for the inductor voltage and current.

2. The voltage across a 100 μ F capacitor takes the following values
 $v_c(t) = 40 \sin(20t - \pi/2)$ V.
 - a. What is the impedance of the capacitor?
 - b. Write the expression for the current through the capacitor in each case.
 - a. Write the phasors for the capacitor voltage and current.
 - b. Draw the phasor diagram for the capacitor voltage and current.

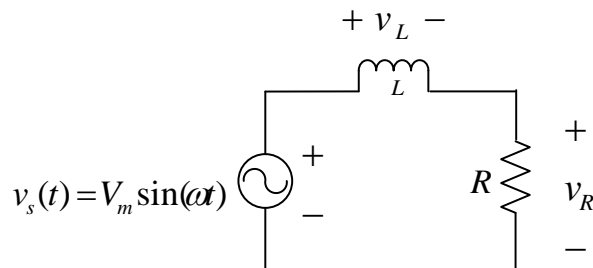3. In the figure given,
 - a) Find the expression for v_R .
 - b) Sketch the phase difference between v_R and v_s . Which of the two is leading?



4. Determine the current $i(t)$ in the circuit shown in the figure.

$$v_s(t) = 636 \cos\left(3000t + \frac{\pi}{12}\right)$$

$$R_1 = 2.3k\Omega, R_2 = 1.1k\Omega$$

$$L = 190mH, C = 55nF$$

