

# EE1002 AY2010/11 Sem1

## Tutorial 3

1. Determine, using superposition, the voltage across  $R$  in the circuit of Figure Q1.

$$I_B = 3A, R_B = 1\Omega, V_G = 15V, R_G = 1\Omega, R = 2\Omega$$

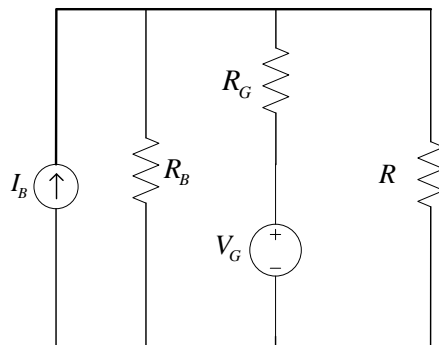


Fig. Q1

2. Find the Thevenin equivalent circuit that the load ( $R_L$ ) sees for the circuit of Figure Q2.

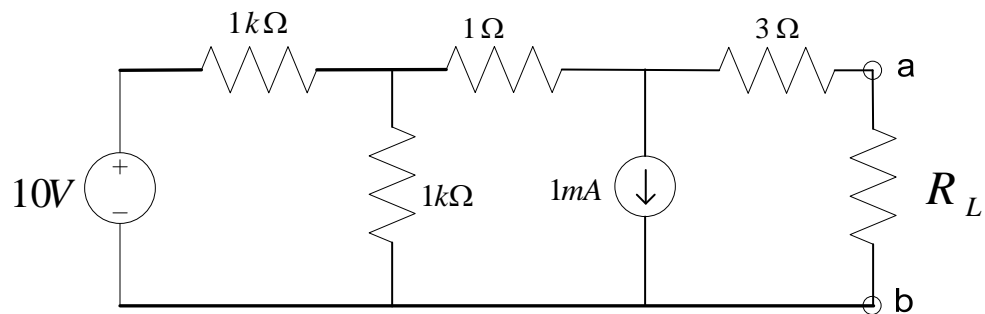


Fig. Q2

3. The circuit shown in Figure Q3 is in the form of what is known as differential amplifier. Find the expression for  $v_0$  in terms of  $v_1$  and  $v_2$  using Thevenin's or Norton's theorem. Assume that the voltage sources  $v_1$  and  $v_2$  do not source any current.

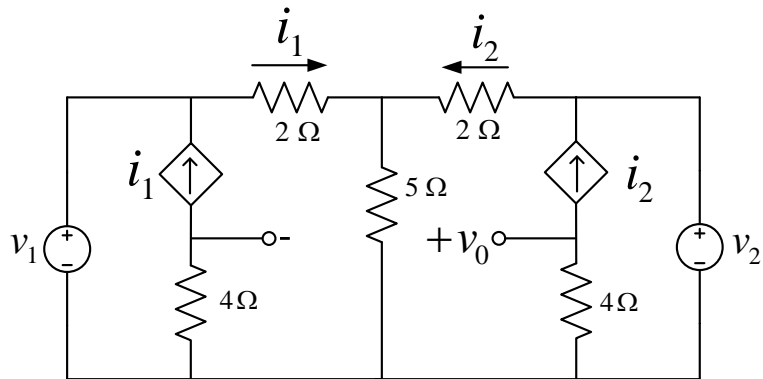


Fig. Q3

- 4.
- Obtain the Thevenin's equivalent for the circuit (Figure Q5), which contains a dependent voltage source.
  - What should be the optimum value of a load resistor  $R_L$  to be connected between **a** and **b** so that the power delivered to it by the network is maximum?
  - What is the maximum power?
  - Also verify that the power delivered is less than the maximum power when  $R_L = 0.8 R_{Lop}$  and  $1.2 R_{Lop}$ ; where  $R_{Lop}$  is the optimum  $R_L$  for maximum power transfer.

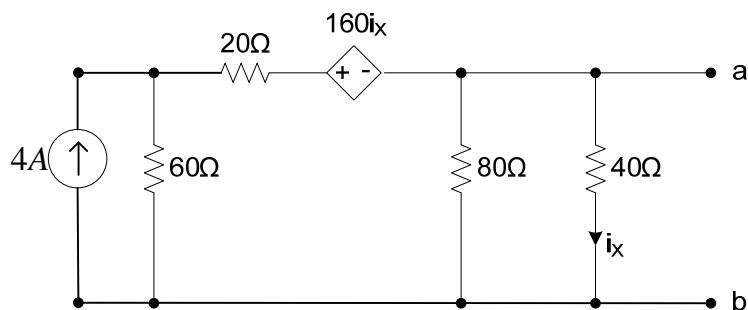


Fig. Q4

5. In the circuit given in Figure Q4,  $V_s$  models the voltage produced by the generator in a power plant, and  $R_s$  model the losses in the generator, distribution wire, and transformers. The three resistances model the various loads connected to the system by a customer. How much does the voltage across the total load change when the customer connects the third load  $R_3$  in parallel with the other two loads?

$$V_s = 110V, R_s = 19m\Omega, R_1 = R_2 = 930m\Omega, R_3 = 100m\Omega$$

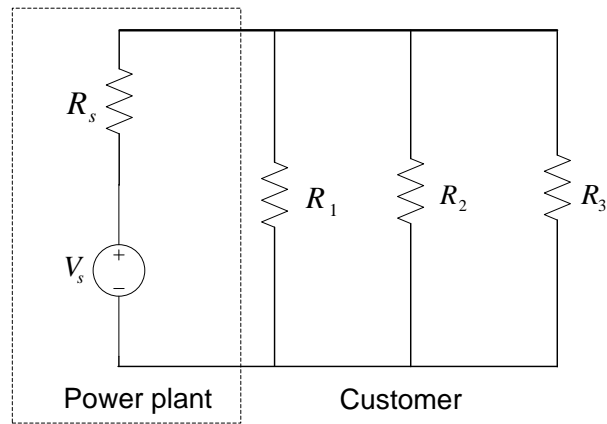


Fig. Q5