

CG1108 Sem 2 AY2010/11

Part2

Lecture 5



Contact details



Office address: E4-08-02

Email : elesahoo@nus.edu.sg

Phone : 65166470

H/P: 92222094

Mid-term Announcement

Date : 5 Mar 2011 (Saturday)
Time : 10am – 11am
Venue : LT6 and E3-06-01
Syllabus : Up to DC transients
(Lecture 1 to Lecture 5)

$$+ \frac{1}{C} \int i_C dt$$

$$i_C = C \frac{dv_C}{dt}$$

Topics learnt so far




$$v = iR$$

$$I = \frac{V}{R}, V = IR$$


$$v_L = L \frac{di_L}{dt}$$

KCL to S.W.

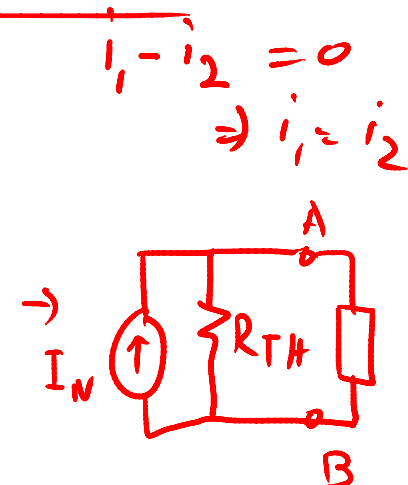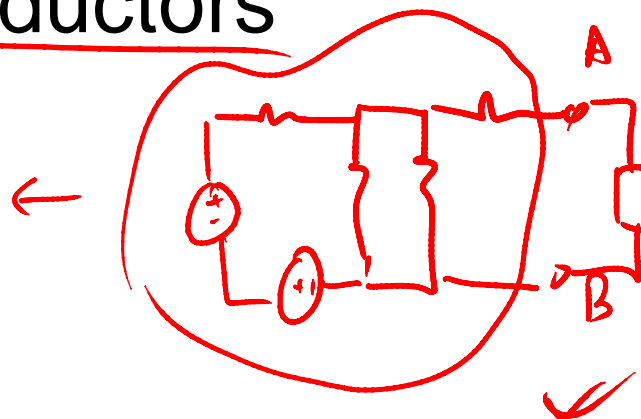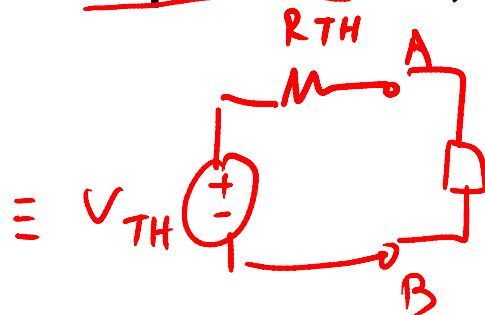- Ohm's Law ✓
- KVL, KCL Super node
- Node analysis, Mesh analysis
- ✓ Thevenin equivalent, Norton equivalent
- Capacitors, Inductors




Remaining topics

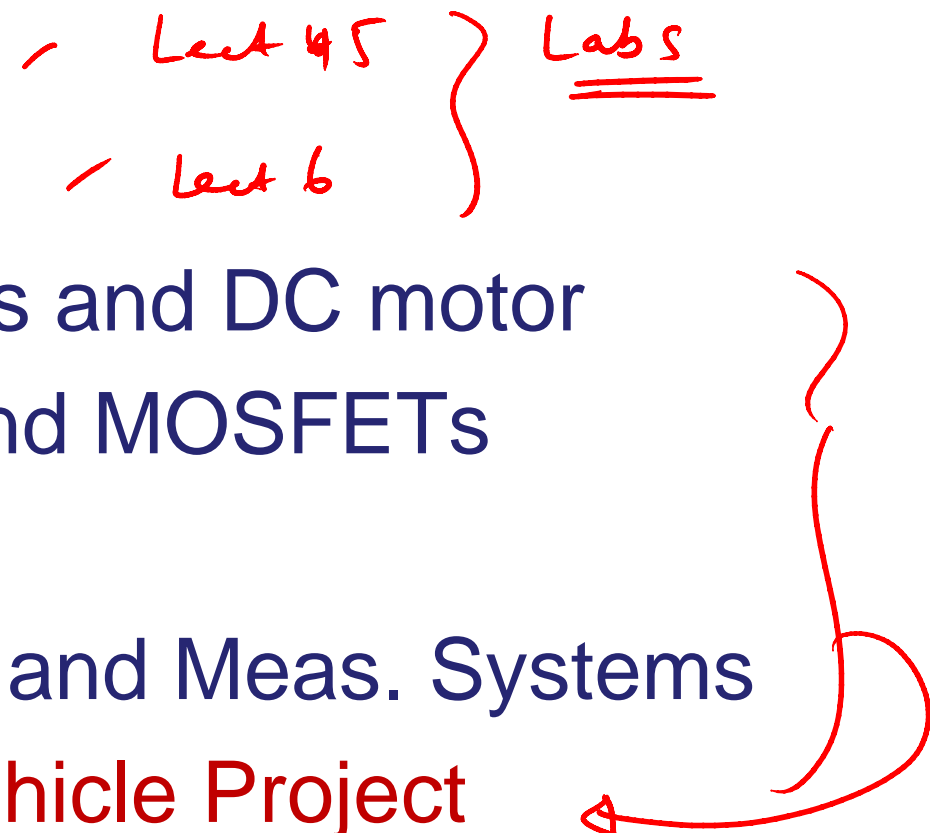- DC transients ✓ Lect 45
 - AC steady-state ✓ Lect 6
 - Magnetic circuits and DC motor
 - Diodes, BJTs and MOSFETs
 - Digital Logic
 - Instrumentation and Meas. Systems
 - Autonomous Vehicle Project
- Labs
- 

Mode of learning

- Review past material ✓
- Introduce the concepts ✓
- Isolate and deal with the mathematics
- Solve examples ✓
- Onto the hands-on part in the lab ✓
- Tutorial


Review

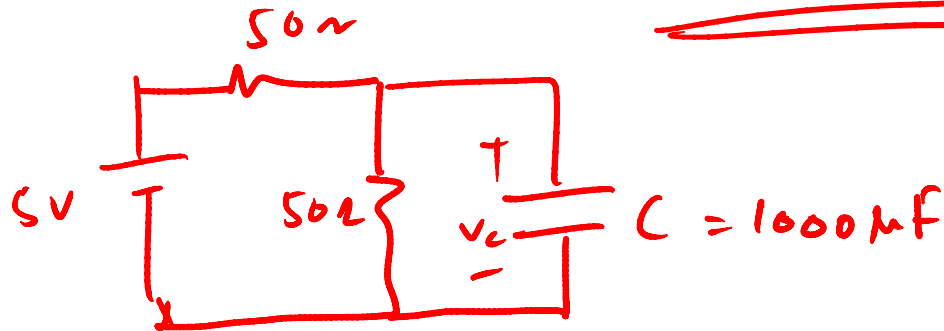

$$V_C = 2.5V$$


$$i_C = C \frac{dV_C}{dt}$$

$$V_L = L \frac{di}{dt}$$

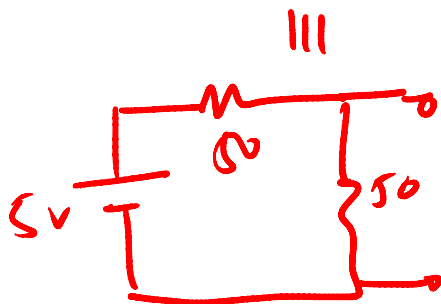

$V_C = 2.5V$ at Steady-state.


$$\frac{d}{dt}(x) = 0$$

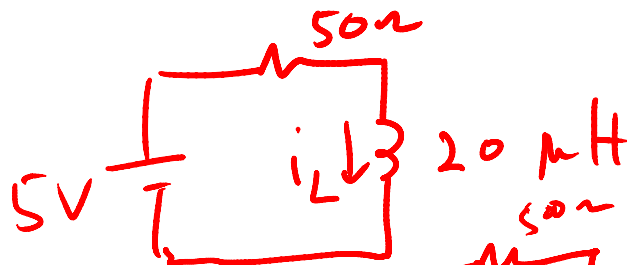

$$i_L =$$

open circuited $\rightarrow i_C (s.s.) = 0$

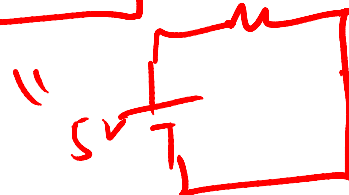short circuited $\rightarrow V_L (s.s.) = 0$



$$I = \frac{5}{50} = 0.1A$$

DC
Steady-state

DC Transients


- Learning objectives:
 - Understand the meaning of transients. ✓
 - Write differential equations for circuits containing inductors and capacitors.
 - Solving differential equations to find the time value of voltages and currents
 - Use of Oscilloscope and Signal generator

Transients

- The time-varying voltages and currents resulting from the adding or removing voltage and current source to circuits containing energy storage elements, are called **transients**. ✓
- Voltage and current in such circuits are represented by **First-order differential equations**.

First order RC circuit

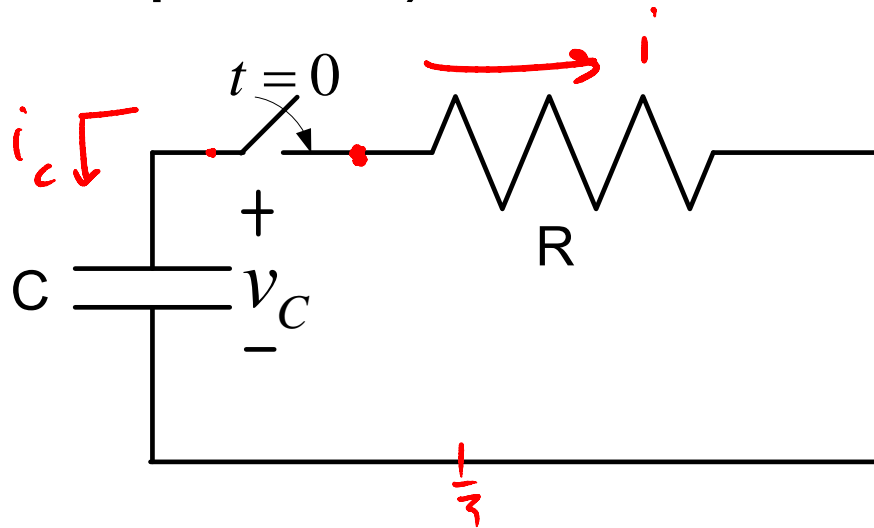- Circuits with resistors and a single energy storage element (either inductor or capacitor) are said to be first-order circuit.




$$C \frac{dv_C(t)}{dt} + \frac{v_C(t)}{R} = 0 \quad \checkmark$$

$$\checkmark \quad \underline{RC} \frac{dv_C(t)}{dt} + \underline{v_C(t)} = 0 \quad \checkmark$$

$$i_C = C \frac{dv_C}{dt}$$

$$i_C + i = 0$$
$$i = \frac{v_C}{R}$$

RC Circuit with a DC source

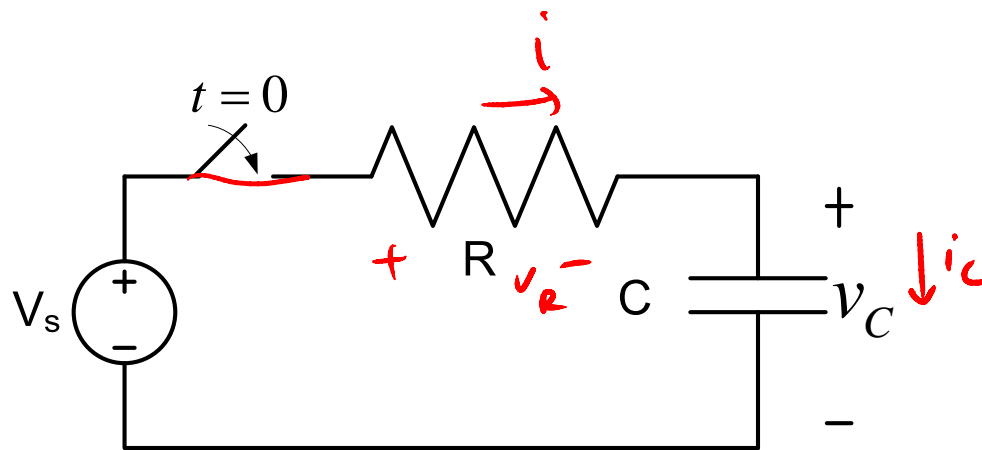

$$-V_s + v_R + v_C = 0 \quad \checkmark \text{ KVL}$$

$$v_R = iR = RC \frac{dv_C}{dt} \quad \checkmark$$


$$-V_s + RC \frac{dv_C}{dt} + v_C = 0$$

$$\checkmark \quad \underline{RC \frac{dv_C}{dt} + v_C = V_s}$$

v_C is the time-varying
qty.

$$v_{C,ss} = V_s$$

RL circuit with DC source

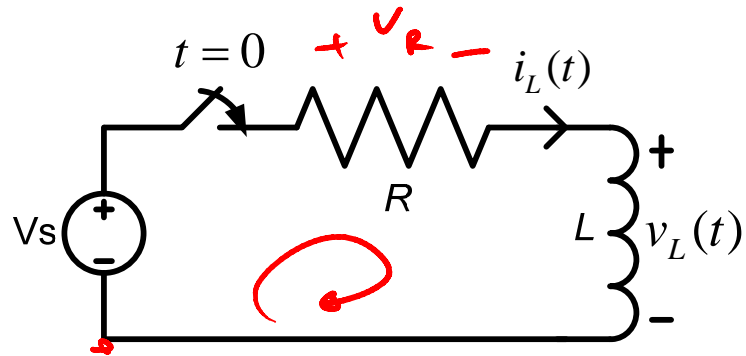

$$-V_s + v_R + v_L = 0 \quad \underline{\text{KVL}}$$

$$-V_s + iR + L \frac{di}{dt} = 0$$

$$\left(\frac{L}{R} \right) \frac{di}{dt} + i = \frac{V_s}{R}$$

$$i_{ss} = \frac{V_s}{R}$$

First order circuits with general sources

$$\tau \frac{dx(t)}{dt} + x(t) = \underline{f(t)}$$

$f(t)$ is known as the forcing function

Steady-state is defined when time rate of the signal is zero.

$$\frac{dx(t)}{dt} = 0, \quad \underline{x_{ss} = f(t)}$$

Solution of Differential eqn

$$\tau \frac{dx(t)}{dt} + x(t) = f(t)$$

- Two parts of the general solution
 - Complementary solution (homogeneous eqn) ✓
 - Particular solution (forced solution) ✓

$$x(t) = x_c(t) + x_p(t) \quad ✓$$

Homogeneous equation

$$\tau \frac{dx_c(t)}{dt} + x_c(t) = 0 \quad \leftarrow \text{Homogeneous eqn.}$$

$$\int \frac{dx_c(t)/dt}{x_c(t)} = \int \frac{-1}{\tau} dt$$

$$\ln[x_c(t)] = \frac{-t}{\tau} + c$$

$$x_c(t) = e^c e^{-t/\tau} = K e^{-t/\tau}$$

- Determine the homogeneous solution by applying the initial condition to the complete solution

Particular solution

- The particular solution is obtained from the forcing function.
- It is normally of the same functional form as the forcing function and its derivatives. ✓
- A table containing various forcing functions and their corresponding particular solutions are readily available. ✓
- http://www.efunda.com/math/ode/linearde_undeterminedcoeff.cfm

When forcing function is DC

- The particular solution is a constant

$$\tau \frac{dx(t)}{dt} + x(t) = f(t)$$

$$\tau \frac{dx_p}{dt} + x_p = K'$$

Let $x_p = K'$.

$$\text{Then } 0 + K' = K'$$

i.e. $x_p = K'$ is a solution

$f(t)$ is also the steady-state solution

Complete Solution

$\tau \frac{dx}{dt} + x = K'$ where K' is the steady - state solution (x_{ss})

$x(t) = Ke^{-\frac{t}{\tau}} + K'$ ✓

Applying the initial condition, i.e. $x(t)$ at $t = 0$:

$x(0) = Ke^0 + K' \Rightarrow K = x(0) - K'$

∴ final solution is :

$x(t) = (x(0) - K')e^{-\frac{t}{\tau}} + K' = x(0)e^{-\frac{t}{\tau}} + K'(1 - e^{-\frac{t}{\tau}})$

$x(t) = x(0)e^{-\frac{t}{\tau}} + x_{ss}(1 - e^{-\frac{t}{\tau}})$ ✓

Recap of the solution

$$\tau \frac{dx}{dt} + x = f(t)$$

$$x = x_c + x_p$$

$$\text{S.S. soln: } \frac{dx}{dt} = 0 \Rightarrow x_{ss} = f(t)$$

In our case $f(t)$ is a constant.

$$x_p \text{ is also a constant. } \underline{f(t) = k'}$$

$$\underline{x_p = k'} \rightarrow \tau \frac{dx_p}{dt} + x_p = k'$$

$0 \quad k' = k' \checkmark$

x_c

Homogeneous eqn: $f(t) = 0$

$$\tau \frac{dx}{dt} + x = 0 \Rightarrow \left(\frac{dx}{x} = \int -\frac{1}{\tau} \cdot dt \right)$$
$$\tau \frac{dx}{dt} = -x \rightarrow \ln |x| = -\frac{t}{\tau} + C$$

Recap of the solution

$$x_c = e^{(-t/\tau + c)} = (e^c) e^{-t/\tau} = K e^{-t/\tau}$$

$$x = x_c + x_p = \frac{K e^{-t/\tau} + K'}{\uparrow \text{unknown}}$$

Initial condition: $x(0) = x(t) |_{t=0}$

$$x(0) = K \cdot e^{-0/\tau} + K' = K + K'$$

$$\Rightarrow K = x(0) - K'$$

$$x(t) = \left(x(0) - x_{ss} \right) e^{-t/\tau} + x_{ss} = x(0) \cdot e^{-t/\tau} + x_{ss} (1 - e^{-t/\tau})$$


Nature of the solution

$$\underline{x(t) = x(0)e^{-\frac{t}{\tau}} + x_{ss}(1 - e^{-\frac{t}{\tau}})}$$

τ = Time constant

$n \quad e^{-n} \quad (1 - e^{-n})$

n	e^{-n}	$(1 - e^{-n})$
0	1	0
1	0.367879	<u>0.632121</u>
2	0.135335	0.864665
3	0.049787	0.950213
4	0.018316	0.981684
5	0.006738	0.993262
6	0.002479	0.997521
7	0.000912	0.999088

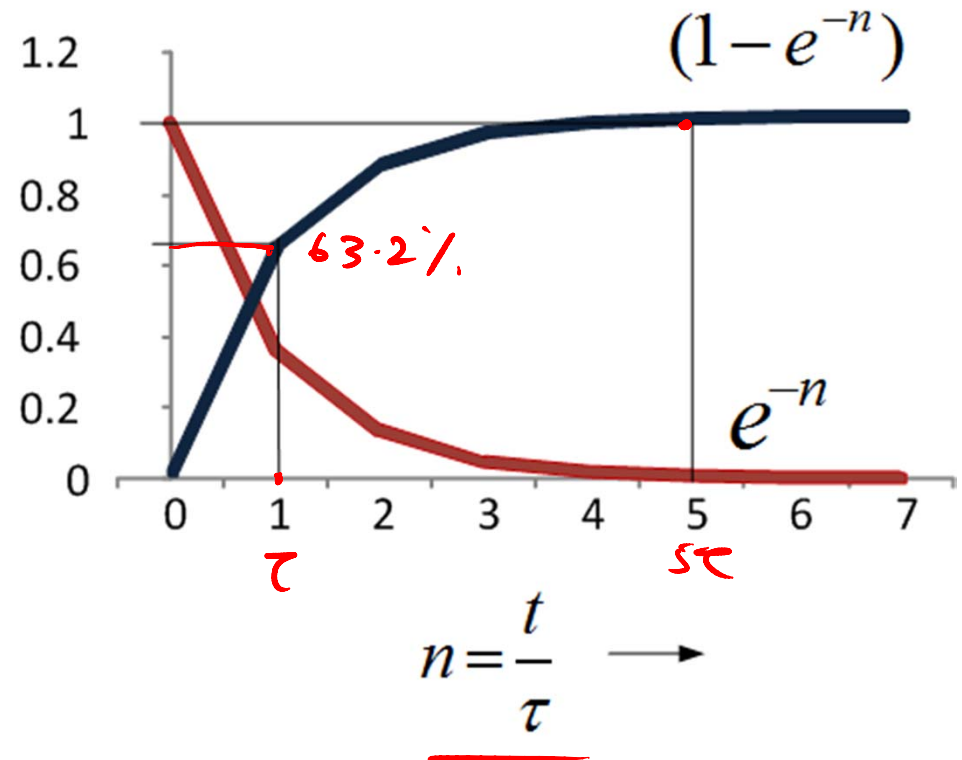

RC and RL comparing to the general form

$$\tau \frac{dx}{dt} + x = K' \text{ where } K' \text{ is the steady-state solution } (x_{ss})$$

$$x(t) = \overline{x(0)} e^{-\frac{t}{\tau}} + \overline{x_{ss}} (1 - e^{-\frac{t}{\tau}})$$

$$RC \frac{dv_c}{dt} + v_c = V_s$$

$$\frac{L}{R} \frac{di_L}{dt} + i_L = \frac{V_s}{R}$$

$$\tau_{RC} = RC$$

$$K' = V_s$$


$$v_c(t) = v_c(0) \cdot e^{-\frac{t}{RC}} + V_s (1 - e^{-t/RC})$$

$$\tau_{LR} = \frac{L}{R}$$

$$K' = \frac{V_s}{R}$$

$$i_L(t) = i_L(0) \cdot e^{-\frac{t}{L/R}} + \frac{V_s}{R} (1 - e^{-t/L/R})$$

Example1

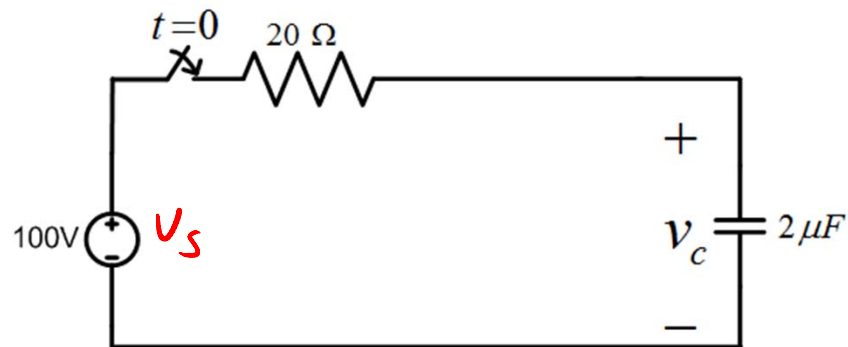

Find $v_c(t)$ after $t > 0$.

$v_c(0) = 0$ initially uncharged


$$v_c(ss) = 100V$$

$$\tau = RC = 20 \times 2 \times 10^{-6} \text{ s}$$

$$= 40 \times 10^{-6} \text{ s}$$

$$v_c(t) = 100 \left(1 - e^{-\frac{t}{40 \times 10^{-6}}} \right) \text{ V}$$

Example 2

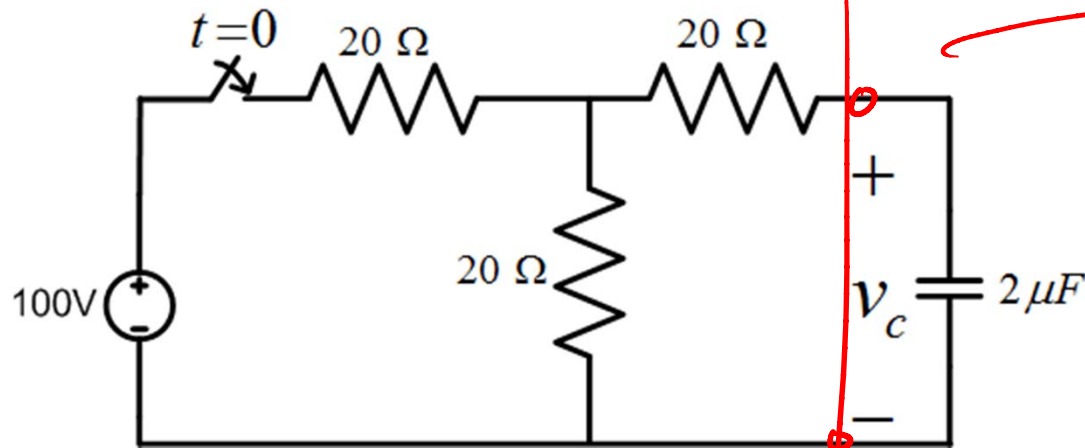


$$v_c(t) = 50 \left(1 - e^{-t/60 \times 10^{-6}} \right) V$$

$v_c(t)$ for $t > 0$.


$$v_c(0) = 0$$

$$V_{c,ss} = 50$$


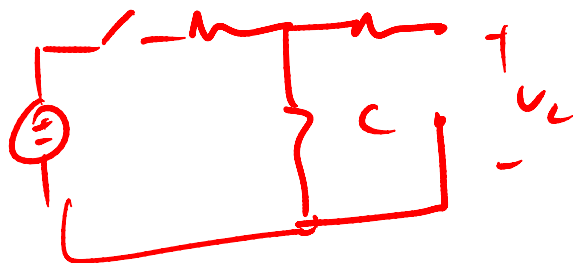
$$\tau = R_{TH} \times C = 30 \times 2 \times 10^{-6} = 60 \mu s$$






$$V_{TH} =$$

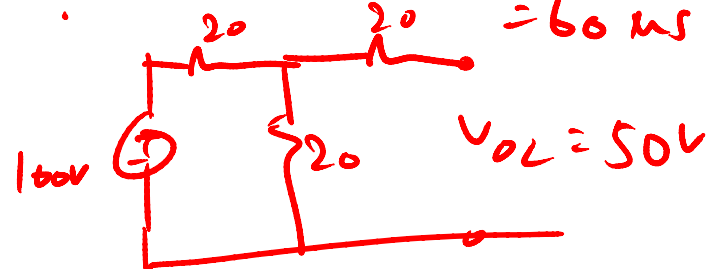

$$R_{TH} =$$

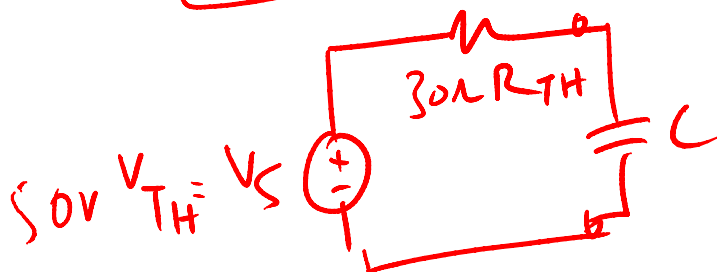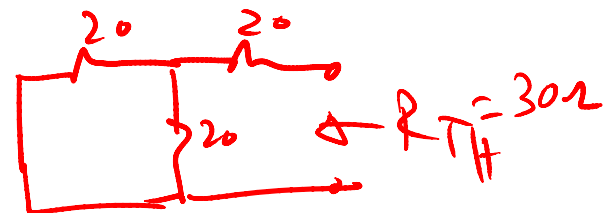

Example 3

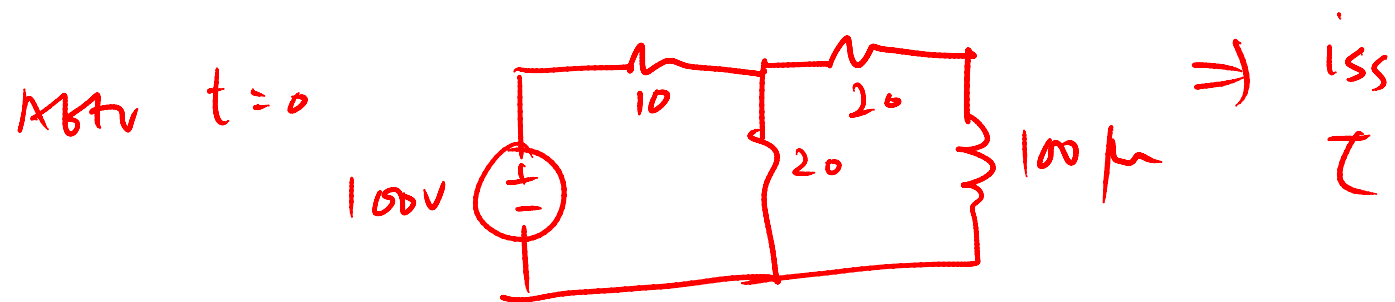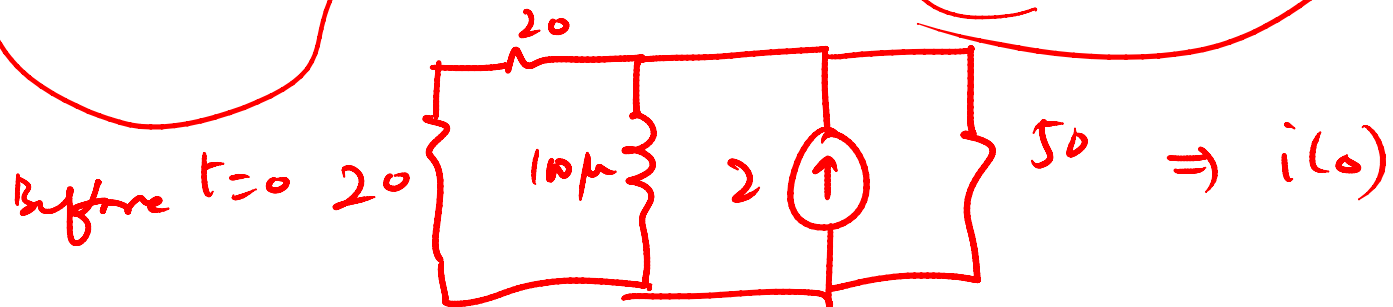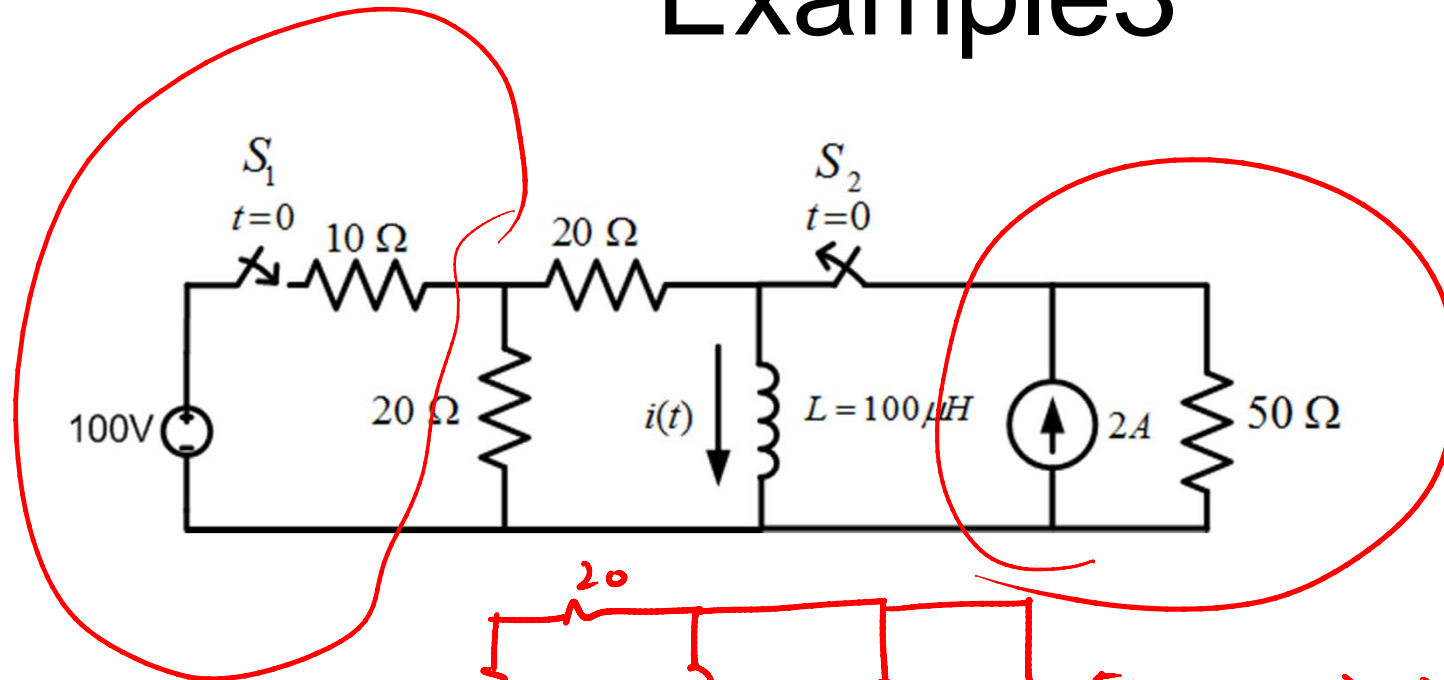

Lab4: Objectives

- To learn about the behavior of capacitors and inductors in DC circuits.
- To learn about the use of the Oscilloscope.
- To learn about the charging / discharging of capacitors.
- To measure the time constants for RC, RL circuits using the oscilloscope.

Lab4: Equipment to be used

- Lab DC power supply
- Digital multi-meter
- Breadboard
- Oscilloscope
- Signal Generator

Oscilloscope

- Basic function
- The probe
- Internal square wave
- Auto-exec
- Vertical scale
- Horizontal scale
- Trigger source and level
- Cursor for measuring signals

Oscilloscope Tutorial on Youtube

http://www.youtube.com/watch?v=qlfo_-d82Co&feature=channel

<http://www.youtube.com/watch?v=hUlgAu3QQWQ&feature=channel>

http://www.youtube.com/watch?v=g_KuGEh0PyA&feature=channel

Signal / Function Generator

- Functions
- Frequency setting
- Main and Aux/TTL output

http://www.youtube.com/watch?v=_pDz6e2ADew&feature=related