

CHAPTER 2

Exercises

- E2.1** (a) R_2 , R_3 , and R_4 are in parallel. Furthermore R_1 is in series with the combination of the other resistors. Thus we have:

$$R_{eq} = R_1 + \frac{1}{1/R_2 + 1/R_3 + 1/R_4} = 3 \Omega$$

- (b) R_3 and R_4 are in parallel. Furthermore, R_2 is in series with the combination of R_3 and R_4 . Finally R_1 is in parallel with the combination of the other resistors. Thus we have:

$$R_{eq} = \frac{1}{1/R_1 + 1/[R_2 + 1/(1/R_3 + 1/R_4)]} = 5 \Omega$$


- (c) R_1 and R_2 are in parallel. Furthermore, R_3 and R_4 are in parallel. Finally, the two parallel combinations are in series.

$$R_{eq} = \frac{1}{1/R_1 + 1/R_2} + \frac{1}{1/R_3 + 1/R_4} = 52.1 \Omega$$

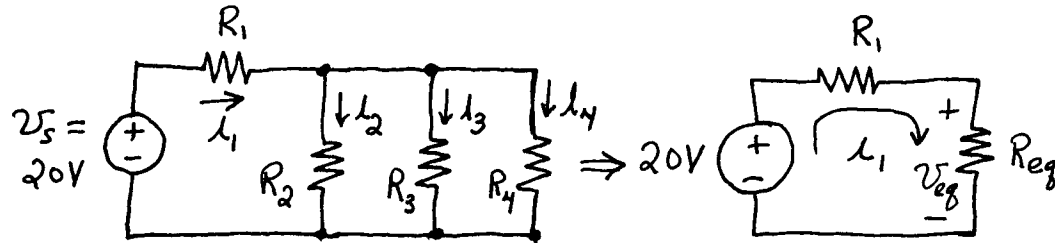- (d) R_1 and R_2 are in series. Furthermore, R_3 is in parallel with the series combination of R_1 and R_2 .

$$R_{eq} = \frac{1}{1/R_3 + 1/(R_1 + R_2)} = 1.5 \text{ k}\Omega$$


- E2.2** (a) First we combine R_2 , R_3 , and R_4 in parallel. Then R_1 is in series with the parallel combination.



$$R_{eq} = \frac{1}{1/R_2 + 1/R_3 + 1/R_4} = 9.231 \Omega \quad i_1 = \frac{20 \text{ V}}{R_1 + R_{eq}} = \frac{20}{10 + 9.231} = 1.04 \text{ A}$$

$$v_{eq} = R_{eq} i_1 = 9.600 \text{ V} \quad i_2 = v_{eq} / R_2 = 0.480 \text{ A} \quad i_3 = v_{eq} / R_3 = 0.320 \text{ A} \\ i_4 = v_{eq} / R_4 = 0.240 \text{ A}$$

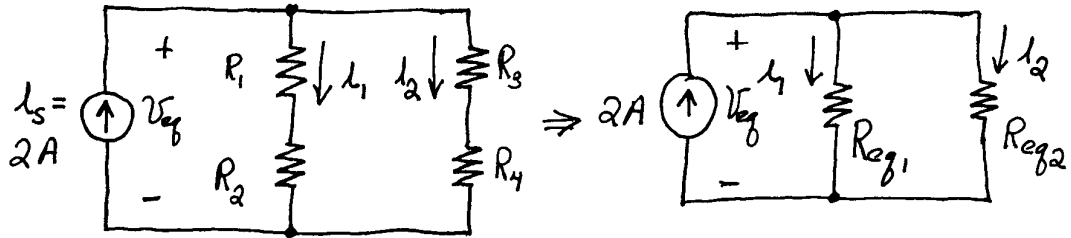
(b) R_1 and R_2 are in series. Furthermore, R_3 and R_4 are in series. Finally, the two series combinations are in parallel.



$$R_{eq1} = R_1 + R_2 = 20 \Omega \quad R_{eq2} = R_3 + R_4 = 20 \Omega \quad R_{eq} = \frac{1}{1/R_{eq1} + 1/R_{eq2}} = 10 \Omega$$

$$v_{eq} = 2 \times R_{eq} = 20 \text{ V} \quad i_1 = v_{eq} / R_{eq1} = 1 \text{ A} \quad i_2 = v_{eq} / R_{eq2} = 1 \text{ A}$$

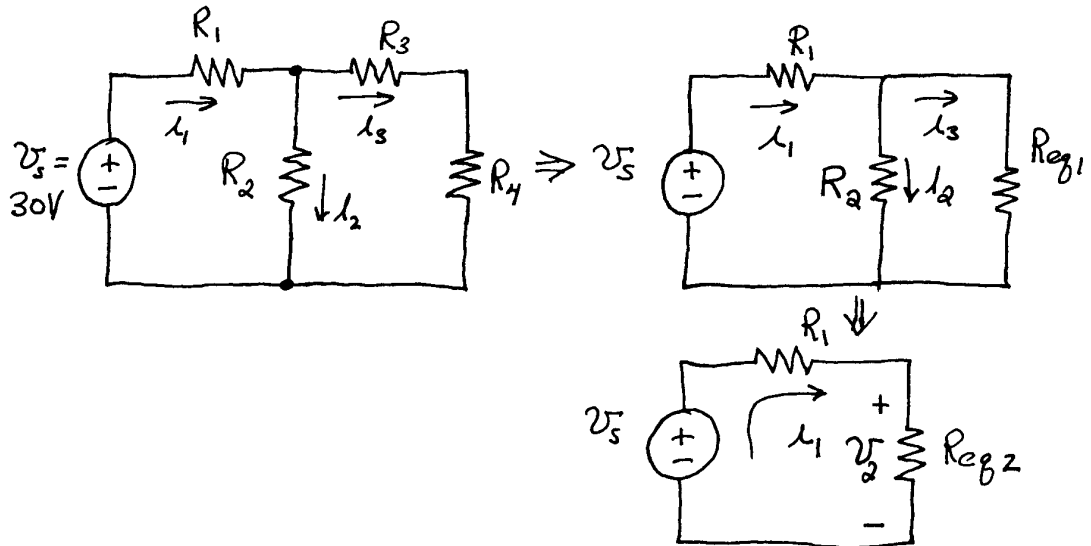(c) R_3 and R_4 are in series. The combination of R_3 and R_4 is in parallel with R_2 . Finally the combination of R_2 , R_3 , and R_4 is in series with R_1 .



$$R_{eq1} = R_3 + R_4 = 40 \Omega \quad R_{eq2} = \frac{1}{1/R_{eq1} + 1/R_2} = 20 \Omega \quad i_1 = \frac{v_s}{R_1 + R_{eq2}} = 1 \text{ A}$$

$$v_2 = i_1 R_{eq2} = 20 \text{ V} \quad i_2 = v_2 / R_2 = 0.5 \text{ A} \quad i_3 = v_2 / R_{eq1} = 0.5 \text{ A}$$

E2.3 (a) $v_1 = v_s \frac{R_1}{R_1 + R_2 + R_3 + R_4} = 10 \text{ V}$. $v_2 = v_s \frac{R_2}{R_1 + R_2 + R_3 + R_4} = 20 \text{ V}$.
Similarly, we find $v_3 = 30 \text{ V}$ and $v_4 = 60 \text{ V}$.

(b) First combine R_2 and R_3 in parallel: $R_{eq} = 1/(1/R_2 + 1/R_3) = 2.917 \Omega$.

Then we have $v_1 = v_s \frac{R_1}{R_1 + R_{eq} + R_4} = 6.05 \text{ V}$. Similarly, we find

$$v_2 = v_s \frac{R_{eq}}{R_1 + R_{eq} + R_4} = 5.88 \text{ V and } v_4 = 8.07 \text{ V}.$$

E2.4 (a) First combine R_1 and R_2 in series: $R_{eq} = R_1 + R_2 = 30 \Omega$. Then we have

$$i_1 = i_s \frac{R_3}{R_3 + R_{eq}} = \frac{15}{15 + 30} = 1 \text{ A and } i_3 = i_s \frac{R_{eq}}{R_3 + R_{eq}} = \frac{30}{15 + 30} = 2 \text{ A}.$$

(b) The current division principle applies to two resistances in parallel. Therefore, to determine i_1 , first combine R_2 and R_3 in parallel: $R_{eq} =$

$$1/(1/R_2 + 1/R_3) = 5 \Omega. \text{ Then we have } i_1 = i_s \frac{R_{eq}}{R_1 + R_{eq}} = \frac{5}{10 + 5} = 1 \text{ A}.$$

Similarly, $i_2 = 1 \text{ A}$ and $i_3 = 1 \text{ A}$.

E2.5 Write KVL for the loop consisting of v_1 , v_y , and v_2 . The result is $-v_1 - v_y + v_2 = 0$ from which we obtain $v_y = v_2 - v_1$. Similarly we obtain $v_z = v_3 - v_1$.

E2.6 Node 1: $\frac{v_1 - v_3}{R_1} + \frac{v_1 - v_2}{R_2} = i_a$ Node 2: $\frac{v_2 - v_1}{R_2} + \frac{v_2}{R_3} + \frac{v_2 - v_3}{R_4} = 0$

Node 3: $\frac{v_3}{R_5} + \frac{v_3 - v_2}{R_4} + \frac{v_3 - v_1}{R_1} + i_b = 0$

E2.7 Following the step-by-step method in the book, we obtain

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} & 0 \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} & -\frac{1}{R_4} \\ 0 & -\frac{1}{R_4} & \frac{1}{R_4} + \frac{1}{R_5} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} -i_s \\ 0 \\ i_s \end{bmatrix}$$

E2.8 Instructions for various calculators vary. The MATLAB solution is given in the book following this exercise.

E2.9 (a) Writing the node equations we obtain:

$$\text{Node 1: } \frac{v_1 - v_3}{20} + \frac{v_1}{5} + \frac{v_1 - v_2}{10} = 0$$

$$\text{Node 2: } \frac{v_2 - v_1}{10} + 10 + \frac{v_2 - v_3}{5} = 0$$

$$\text{Node 3: } \frac{v_3 - v_1}{20} + \frac{v_3}{10} + \frac{v_3 - v_2}{5} = 0$$

(b) Simplifying the equations we obtain:

$$0.35v_1 - 0.10v_2 - 0.05v_3 = 0$$

$$-0.10v_1 + 0.30v_2 - 0.20v_3 = -10$$

$$-0.05v_1 - 0.20v_2 + 0.35v_3 = 0$$

(c) and (d) Solving using Matlab:

```
>>clear
```

```
>>G = [0.35 -0.1 -0.05; -0.10 0.30 -0.20; -0.05 -0.20 0.35];
```

```
>>I = [0; -10; 0];
```

```
>>V = G\I
```

```
V =
```

```
 -27.2727
```

```
 -72.7273
```

```
 -45.4545
```

```
>>Ix = (V(1) - V(3))/20
```

```
Ix =
```

```
 0.9091
```

E2.10 Using determinants we can solve for the unknown voltages as follows:

$$v_1 = \frac{\begin{vmatrix} 6 & -0.2 \\ 1 & 0.5 \end{vmatrix}}{\begin{vmatrix} 0.7 & -0.2 \\ -0.2 & 0.5 \end{vmatrix}} = \frac{3 + 0.2}{0.35 - 0.04} = 10.32 \text{ V}$$

$$v_2 = \frac{\begin{vmatrix} 0.7 & 6 \\ -0.2 & 1 \end{vmatrix}}{\begin{vmatrix} 0.7 & -0.2 \\ -0.2 & 0.5 \end{vmatrix}} = \frac{0.7 + 1.2}{0.35 - 0.04} = 6.129 \text{ V}$$

Many other methods exist for solving linear equations.

E2.11 First write KCL equations at nodes 1 and 2:

$$\text{Node 1: } \frac{v_1 - 10}{2} + \frac{v_1}{5} + \frac{v_1 - v_2}{10} = 0$$

$$\text{Node 2: } \frac{v_2 - 10}{10} + \frac{v_2}{5} + \frac{v_2 - v_1}{10} = 0$$

Then, simplify the equations to obtain:

$$8v_1 - v_2 = 50 \quad \text{and} \quad -v_1 + 4v_2 = 10$$

Solving manually or with a calculator, we find $v_1 = 6.77$ V and $v_2 = 4.19$ V.

The MATLAB session using the symbolic approach is:

```
>> clear
[V1,V2] = solve('(V1-10)/2+(V1)/5+(V1 - V2)/10 = 0' , ...
                '(V2-10)/10 +V2/5 +(V2-V1)/10 = 0')
V1 =
210/31
V2 =
130/31
```

Next, we solve using the numerical approach.

```
>> clear
G = [8 -1; -1 4];
I = [50; 10];
V = G\I
V =
    6.7742
    4.1935
```

E2.12 The equation for the supernode enclosing the 15-V source is:

$$\frac{v_3 - v_2}{R_3} + \frac{v_3 - v_1}{R_1} = \frac{v_1}{R_2} + \frac{v_2}{R_4}$$

This equation can be readily shown to be equivalent to Equation 2.37 in the book. (Keep in mind that $v_3 = -15$ V.)

- E2.13** Write KVL from the reference to node 1 then through the 10-V source to node 2 then back to the reference node:

$$-v_1 + 10 + v_2 = 0$$

Then write KCL equations. First for a supernode enclosing the 10-V source, we have:

$$\frac{v_1}{R_1} + \frac{v_1 - v_3}{R_2} + \frac{v_2 - v_3}{R_3} = 1$$

Node 3:

$$\frac{v_3}{R_4} + \frac{v_3 - v_1}{R_2} + \frac{v_3 - v_2}{R_3} = 0$$

Reference node:


$$\frac{v_1}{R_1} + \frac{v_3}{R_4} = 1$$

An independent set consists of the KVL equation and any two of the KCL equations.

- E2.14** (a) Select the reference node at the left-hand end of the voltage source as shown at right.

Then write a KCL equation at node 1.
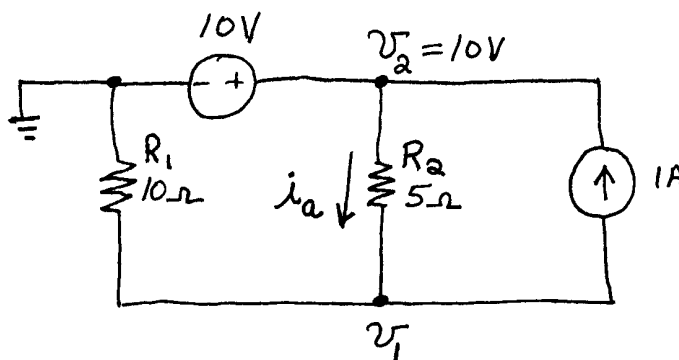
$$\frac{v_1}{R_1} + \frac{v_1 - 10}{R_2} + 1 = 0$$




Substituting values for the resistances and solving, we find $v_1 = 3.33$ V.

Then we have $i_a = \frac{10 - v_1}{R_2} = 1.333$ A.

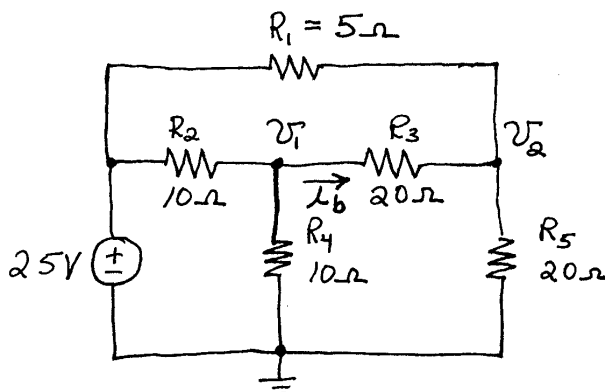- (b) Select the reference node and assign node voltages as shown.

Then write KCL equations at nodes 1 and 2.




$$\frac{v_1 - 25}{R_2} + \frac{v_1}{R_4} + \frac{v_1 - v_2}{R_3} = 0$$

$$\frac{v_2 - 25}{R_1} + \frac{v_2 - v_1}{R_3} + \frac{v_2}{R_5} = 0$$

Substituting values for the resistances and solving, we find $v_1 = 13.79$ V and $v_2 = 18.97$ V. Then we have $i_b = \frac{v_1 - v_2}{R_3} = -0.259$ A.

- E2.15** (a) Select the reference node and node voltage as shown. Then write a KCL equation at node 1, resulting in

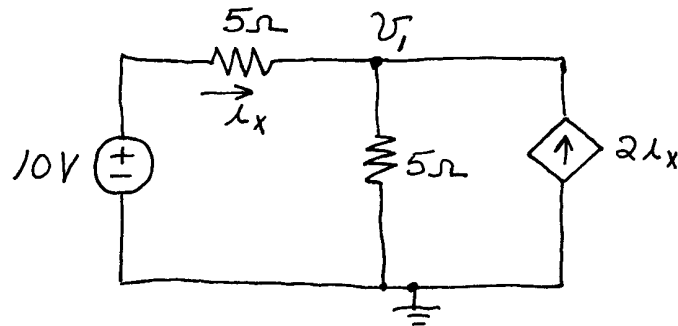
$$\frac{v_1}{5} + \frac{v_1 - 10}{5} - 2i_x = 0$$



Then use $i_x = (10 - v_1)/5$ to substitute and solve. We find $v_1 = 7.5$ V.

Then we have $i_x = \frac{10 - v_1}{5} = 0.5$ A.

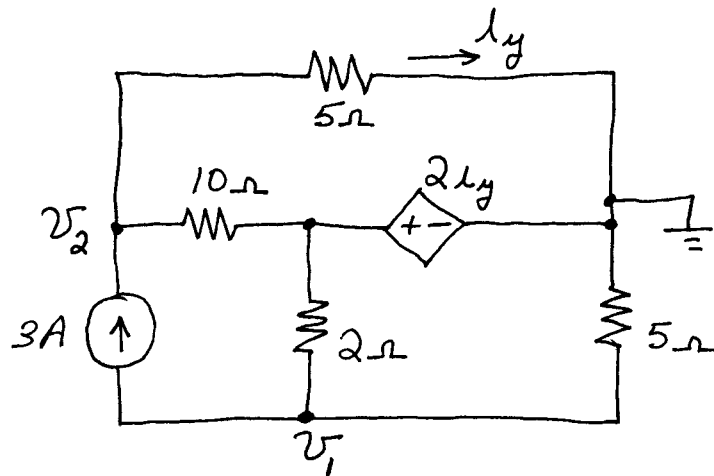- (b) Choose the reference node and node voltages shown:



Then write KCL equations at nodes 1 and 2:

$$\frac{v_1}{5} + \frac{v_1 - 2i_y}{2} + 3 = 0 \quad \frac{v_2}{5} + \frac{v_2 - 2i_y}{10} = 3$$

Finally use $i_y = v_2 / 5$ to substitute and solve. This yields $v_2 = 11.54 \text{ V}$ and $i_y = 2.31 \text{ A}$.

E2.16 >> clear

```
>> [V1 V2 V3] = solve('V3/R4 + (V3 - V2)/R3 + (V3 - V1)/R1 = 0', ...
    'V1/R2 + V3/R4 = Is', ...
    'V1 = (1/2)*(V3 - V1) + V2', 'V1', 'V2', 'V3');
>> pretty(V1), pretty(V2), pretty(V3)
```

$$\frac{R_2 I_s (2 R_3 R_1 + 3 R_4 R_1 + 2 R_4 R_3)}{2 R_3 R_1 + 3 R_4 R_1 + 3 R_1 R_2 + 2 R_4 R_3 + 2 R_3 R_2}$$

$$\frac{R_2 I_s (3 R_3 R_1 + 3 R_4 R_1 + 2 R_4 R_3)}{2 R_3 R_1 + 3 R_4 R_1 + 3 R_1 R_2 + 2 R_4 R_3 + 2 R_3 R_2}$$

$$\frac{I_s R_2 R_4 (3 R_1 + 2 R_3)}{2 R_3 R_1 + 3 R_4 R_1 + 3 R_1 R_2 + 2 R_4 R_3 + 2 R_3 R_2}$$

E2.17 Refer to Figure 2.33b in the book. (a) Two mesh currents flow through R_2 : i_1 flows downward and i_4 flows upward. Thus the current flowing in R_2 referenced upward is $i_4 - i_1$. (b) Similarly, mesh current i_1 flows to the left through R_4 and mesh current i_2 flows to the right, so the total current referenced to the right is $i_2 - i_1$. (c) Mesh current i_3 flows downward through R_8 and mesh current i_4 flows upward, so the total current referenced downward is $i_3 - i_4$. (d) Finally, the total current referenced upward through R_8 is $i_4 - i_3$.


E2.18 Refer to Figure 2.33b in the book. Following each mesh current in turn, we have

$$\begin{aligned} R_1 i_1 + R_2 (i_1 - i_4) + R_4 (i_1 - i_2) - v_A &= 0 \\ R_5 i_2 + R_4 (i_2 - i_1) + R_6 (i_2 - i_3) &= 0 \\ R_7 i_3 + R_6 (i_3 - i_2) + R_8 (i_3 - i_4) &= 0 \\ R_3 i_4 + R_2 (i_4 - i_1) + R_8 (i_4 - i_3) &= 0 \end{aligned}$$

In matrix form, these equations become

$$\begin{bmatrix} (R_1 + R_2 + R_4) & -R_4 & 0 & -R_2 \\ -R_4 & (R_4 + R_5 + R_6) & -R_6 & 0 \\ 0 & -R_6 & (R_6 + R_7 + R_8) & -R_8 \\ -R_2 & 0 & -R_8 & (R_2 + R_3 + R_8) \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} v_A \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

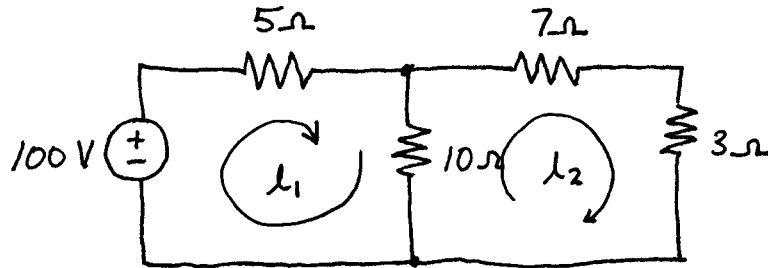E2.19 We choose the mesh currents as shown:




Then, the mesh equations are:

$$5i_1 + 10(i_1 - i_2) = 100 \quad \text{and} \quad 10(i_2 - i_1) + 7i_2 + 3i_2 = 0$$

Simplifying and solving these equations, we find that $i_1 = 10 \text{ A}$ and $i_2 = 5 \text{ A}$. The net current flowing downward through the $10\text{-}\Omega$ resistance is $i_1 - i_2 = 5 \text{ A}$.

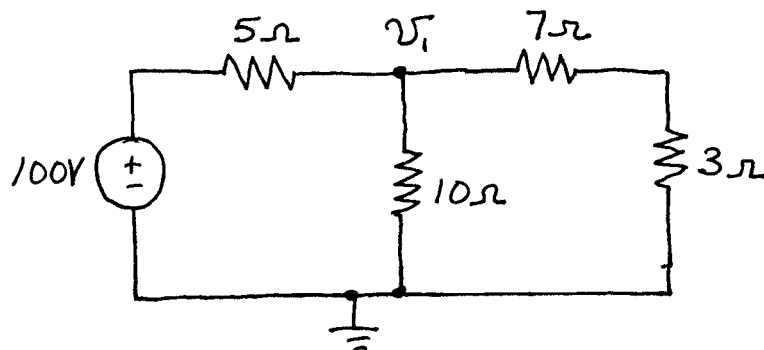
To solve by node voltages, we select the reference node and node voltage shown. (We do not need to assign a node voltage to the connection between the $7\text{-}\Omega$ resistance and the $3\text{-}\Omega$ resistance because we can treat the series combination as a single $10\text{-}\Omega$ resistance.)



The node equation is $(v_1 - 10)/5 + v_1/10 + v_1/10 = 0$. Solving we find that $v_1 = 50$ V. Thus we again find that the current through the $10\text{-}\Omega$ resistance is $i = v_1/10 = 5$ A.

Combining resistances in series and parallel, we find that the resistance "seen" by the voltage source is $10\text{ }\Omega$. Thus the current through the source and $5\text{-}\Omega$ resistance is $(100\text{ V})/(10\text{ }\Omega) = 10$ A. This current splits equally between the $10\text{-}\Omega$ resistance and the series combination of $7\text{ }\Omega$ and $3\text{ }\Omega$.

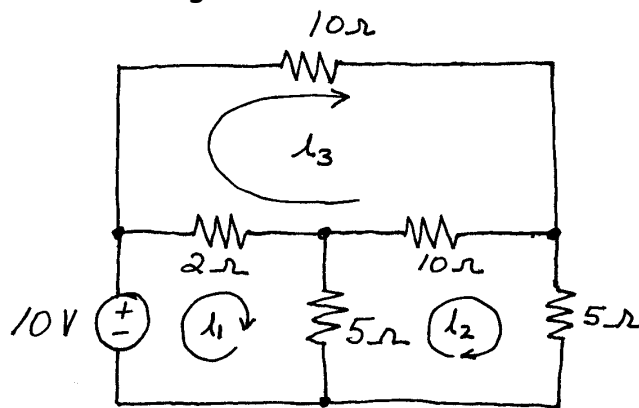E2.20 First, we assign the mesh currents as shown.



Then we write KVL equations following each mesh current:

$$\begin{aligned} 2(i_1 - i_3) + 5(i_1 - i_2) &= 10 \\ 5i_2 + 5(i_2 - i_1) + 10(i_2 - i_3) &= 0 \\ 10i_3 + 10(i_3 - i_2) + 2(i_3 - i_1) &= 0 \end{aligned}$$

Simplifying and solving, we find that $i_1 = 2.194$ A, $i_2 = 0.839$ A, and $i_3 = 0.581$ A. Thus the current in the $2\text{-}\Omega$ resistance referenced to the right is $i_1 - i_3 = 2.194 - 0.581 = 1.613$ A.

E2.21 Following the step-by-step process, we obtain

$$\begin{bmatrix} (R_2 + R_3) & -R_3 & -R_2 \\ -R_3 & (R_3 + R_4) & 0 \\ -R_2 & 0 & (R_1 + R_2) \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} v_A \\ -v_B \\ v_B \end{bmatrix}$$

E2.22 Refer to Figure 2.39 in the book. In terms of the mesh currents, the current directed to the right in the 5-A current source is i_1 , however by the definition of the current source, the current is 5 A directed to the left. Thus, we conclude that $i_1 = -5$ A. Then we write a KVL equation following i_2 , which results in $10(i_2 - i_1) + 5i_2 = 100$.

E2.23 Refer to Figure 2.40 in the book. First, for the current source, we have


$$i_2 - i_1 = 1$$

Then, we write a KVL equation going around the perimeter of the entire circuit:

$$5i_1 + 10i_2 + 20 - 10 = 0$$


Simplifying and solving these equations we obtain $i_1 = -4/3$ A and $i_2 = -1/3$ A.

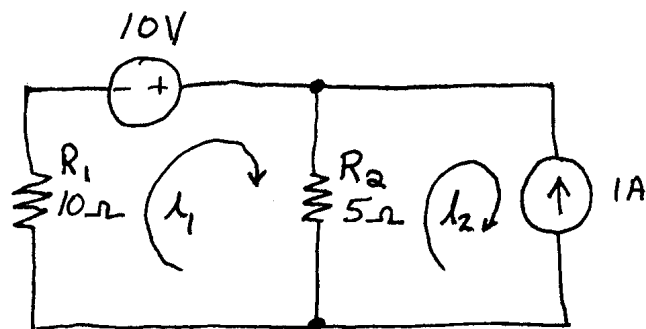E2.24 (a) As usual, we select the mesh currents flowing clockwise around the meshes as shown. Then for the current source, we have $i_2 = -1$ A. This is because we defined the mesh



current i_2 as the current referenced downward through the current source. However, we know that the current through this source is 1 A flowing upward. Next we write a KVL equation around mesh 1: $10i_1 - 10 + 5(i_1 - i_2) = 0$. Solving, we find that $i_1 = 1/3$ A. Referring to Figure 2.30a in the book we see that the value of the current i_a referenced downward through the 5Ω resistance is to be found. In terms of the mesh currents, we have $i_a = i_1 - i_2 = 4/3$ A.

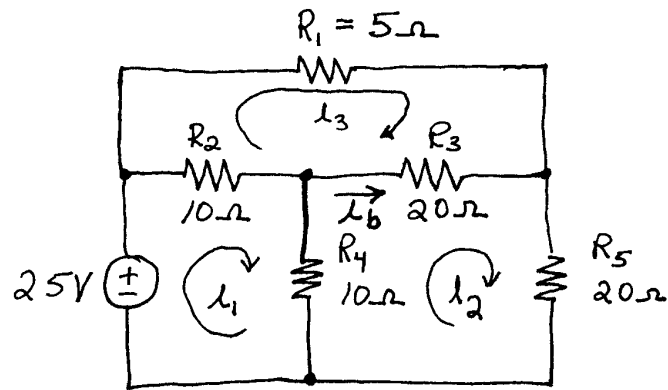(b) As usual, we select the mesh currents flowing clockwise around the meshes as shown. Then we write a KVL equation for each mesh.



$$-25 + 10(i_1 - i_3) + 10(i_1 - i_2) = 0$$

$$10(i_2 - i_1) + 20(i_2 - i_3) + 20i_2 = 0$$

$$10(i_3 - i_1) + 5i_3 + 20(i_3 - i_2) = 0$$

Simplifying and solving, we find $i_1 = 2.3276$ A, $i_2 = 0.9483$ A, and $i_3 = 1.2069$ A. Finally, we have $i_b = i_2 - i_3 = -0.2586$ A.

E2.25

(a) KVL mesh 1:


$$-10 + 5i_1 + 5(i_1 - i_2) = 0$$

For the current source:

$$i_2 = -2i_x$$

However, i_x and i_1 are the same current, so we also have $i_1 = i_x$.

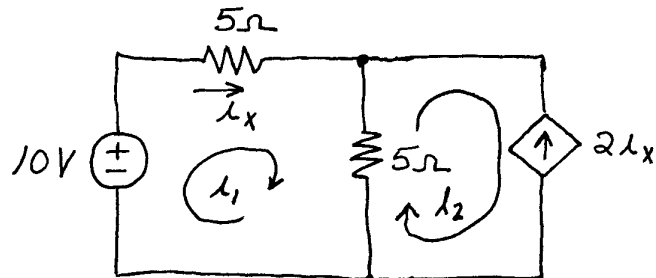Simplifying and solving, we find $i_x = i_1 = 0.5$ A.




(b) First for the current source, we have: $i_1 = 3$ A

Writing KVL around meshes 2 and 3, we have:

$$2(i_2 - i_1) + 2i_y + 5i_2 = 0$$

$$10(i_3 - i_1) + 5i_3 - 2i_y = 0$$

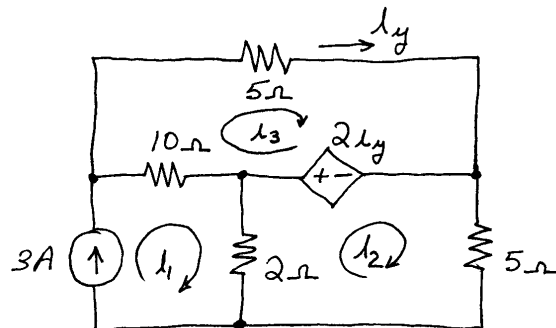


However i_3 and i_y are the same current: $i_y = i_3$. Simplifying and solving, we find that $i_3 = i_y = 2.31$ A.

- E2.26** Under open-circuit conditions, 5 A circulates clockwise through the current source and the 10- Ω resistance. The voltage across the 10- Ω resistance is 50 V. No current flows through the 40- Ω resistance so the open circuit voltage is $V_f = 50$ V.

With the output shorted, the 5 A divides between the two resistances in parallel. The short-circuit current is the current through the 40- Ω resistance, which is $i_{sc} = 5 \frac{10}{10 + 40} = 1$ A. Then, the Thévenin resistance is $R_f = v_{oc} / i_{sc} = 50 \Omega$.

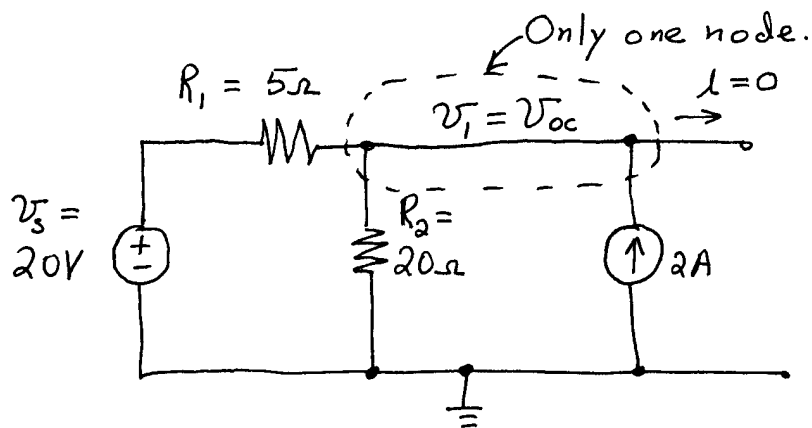- E2.27** Choose the reference node at the bottom of the circuit as shown:






Notice that the node voltage is the open-circuit voltage. Then write a KCL equation:

$$\frac{v_{oc} - 20}{5} + \frac{v_{oc}}{20} = 2$$

Solving we find that $v_{oc} = 24$ V which agrees with the value found in Example 2.17.

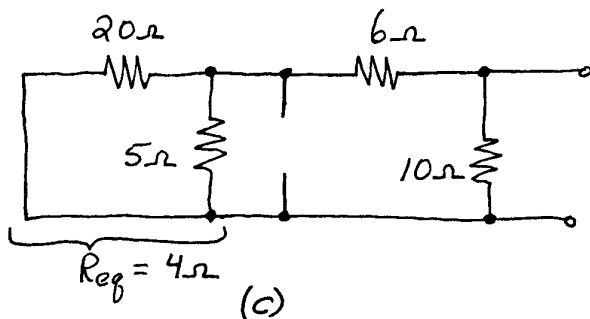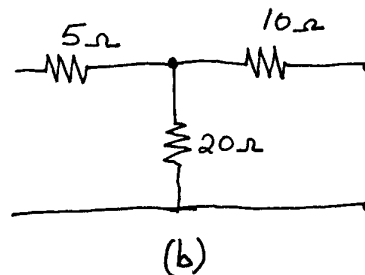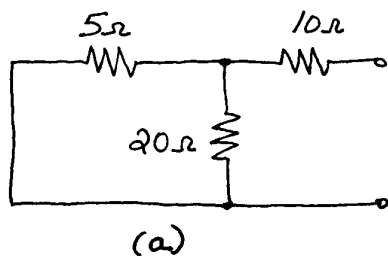- E2.28** To zero the sources, the voltage sources become short circuits and the current sources become open circuits. The resulting circuits are :




$$(a) R_T = 10 + \frac{1}{1/5 + 1/20} = 14 \Omega$$

$$(b) R_T = 10 + 20 = 30 \Omega$$


$$(c) R_T = \frac{1}{\frac{1}{10} + \frac{1}{6 + \frac{1}{(1/5 + 1/20)}}} = 5 \Omega$$

E2.29 (a) Zero sources to determine Thévenin resistance. Thus
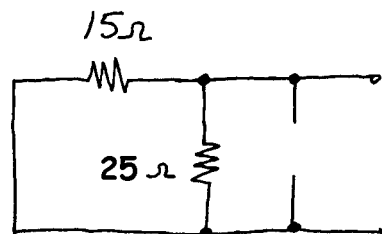
$$R_T = \frac{1}{1/15 + 1/25} = 9.375 \Omega.$$




Then find short-circuit current:

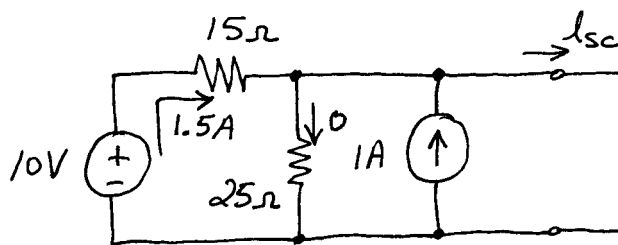

$$I_n = i_{sc} = 10/15 + 1 = 1.67 \text{ A}$$

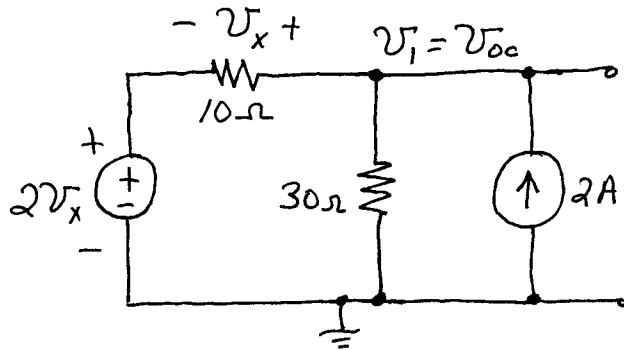
(b) We cannot find the Thévenin resistance by zeroing the sources, because we have a controlled source. Thus, we find the open-circuit voltage and the short-circuit current.



$$\frac{v_{oc} - 2v_x}{10} + \frac{v_{oc}}{30} = 2 \quad v_{oc} = 3v_x$$

Solving, we find $V_T = v_{oc} = 30 \text{ V}$.


Now, we find the short-circuit current:

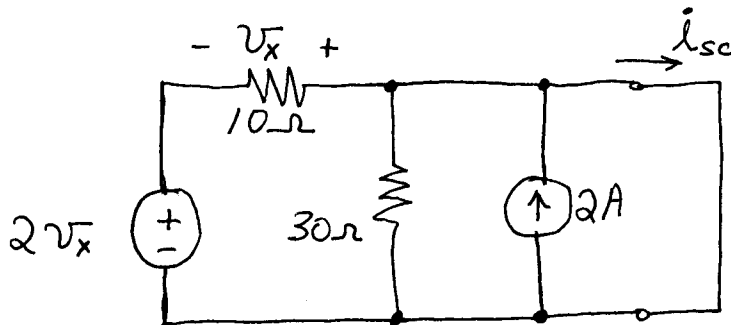

$$2v_x + v_x = 0 \Rightarrow v_x = 0$$

Therefore $i_{sc} = 2 \text{ A}$. Then we have $R_T = v_{oc} / i_{sc} = 15 \Omega$.

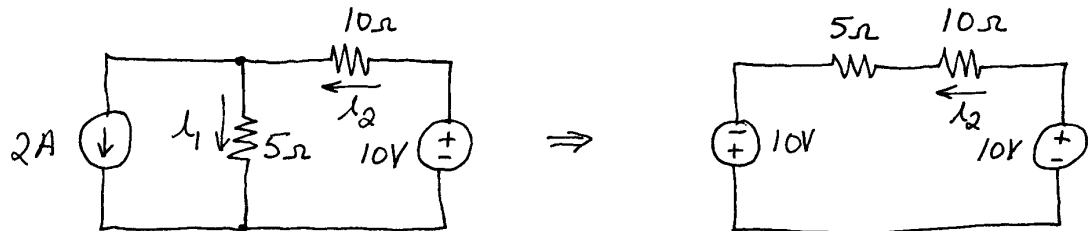
E2.30 First, we transform the 2-A source and the 5- Ω resistance into a voltage source and a series resistance:



Then we have $i_2 = \frac{10+10}{15} = 1.333 \text{ A}$.

From the original circuit, we have $i_1 = i_2 - 2$, from which we find $i_1 = -0.667 \text{ A}$.

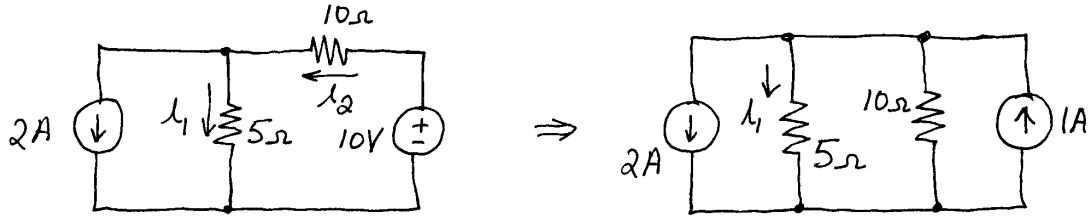The other approach is to start from the original circuit and transform the $10\text{-}\Omega$ resistance and the 10-V voltage source into a current source and parallel resistance:



Then we combine the resistances in parallel. $R_{eq} = \frac{1}{1/5 + 1/10} = 3.333 \Omega$.


The current flowing upward through this resistance is 1 A . Thus the voltage across R_{eq} referenced positive at the bottom is 3.333 V and $i_1 = -3.333/5 = -0.667 \text{ A}$. Then from the original circuit we have $i_2 = 2 + i_1 = 1.333 \text{ A}$, as before.

E2.31 Refer to Figure 2.62b. We have $i_1 = 15/15 = 1 \text{ A}$.

Refer to Figure 2.62c. Using the current division principle, we have

$i_2 = -2 \times \frac{5}{5+10} = -0.667 \text{ A}$. (The minus sign is because of the reference direction of i_2 .) Finally, by superposition we have $i_T = i_1 + i_2 = 0.333 \text{ A}$.

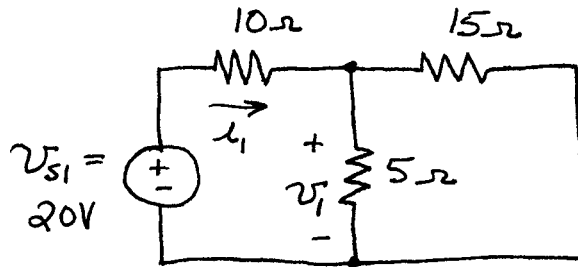E2.32 With only the first source active we have:




Then we combine resistances in series and parallel:

$$R_{eq} = 10 + \frac{1}{1/5 + 1/15} = 13.75 \Omega$$

Thus, $i_1 = 20/13.75 = 1.455 \text{ A}$, and $v_1 = 3.75i_1 = 5.45 \text{ V}$.

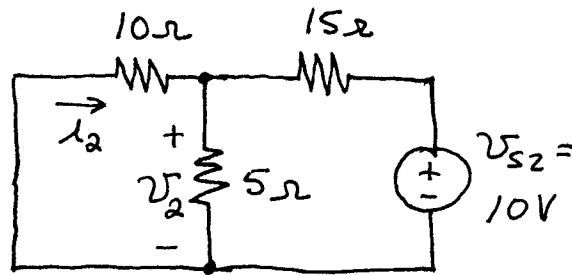With only the second source active, we have:



Then we combine resistances in series and parallel:

$$R_{eq2} = 15 + \frac{1}{1/5 + 1/10} = 18.33 \Omega$$

Thus, $i_s = 10 / 18.33 = 0.546 \text{ A}$, and $v_2 = 3.33 i_s = 1.818 \text{ V}$. Then, we have

$$i_2 = (-v_2) / 10 = -0.1818 \text{ A}$$

Finally we have $v_T = v_1 + v_2 = 5.45 + 1.818 = 7.27 \text{ V}$ and

$$i_T = i_1 + i_2 = 1.455 - 0.1818 = 1.27 \text{ A}.$$



Answers for Selected Problems

P2.1* (a) $R_{eq} = 20 \Omega$ (b) $R_{eq} = 23 \Omega$

P2.2* $R_x = 5 \Omega$.

P2.3* $R_{ab} = 10 \Omega$

P2.4*

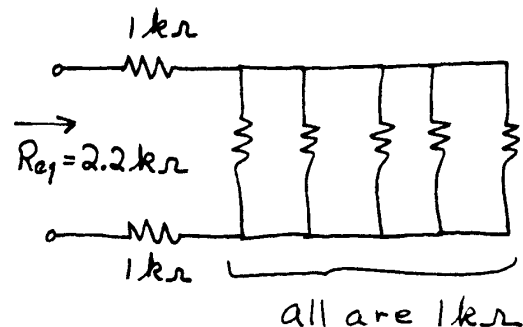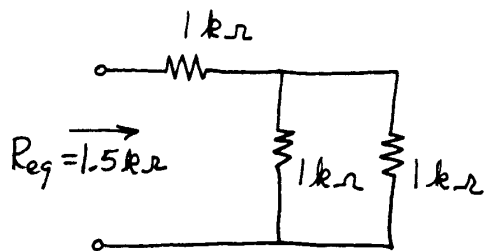

P2.5* $R_{ab} = 9.6 \, \Omega$

P2.23* $i_1 = 1 \, A$ $i_2 = 0.5 \, A$

P2.24* $v_1 = 3 \, V$ $v_2 = 0.5 \, V$

P2.25* $v = 140 \, V$; $i = 1 \, A$

P2.34* $i_1 = 1.5 \, A$ $i_2 = 0.5 \, A$
 $P_{4A} = 30 \, W$ delivering
 $P_{2A} = 15 \, W$ absorbing
 $P_{5\Omega} = 11.25 \, W$ absorbing
 $P_{15\Omega} = 3.75 \, W$ absorbing

P2.35* $i_1 = 2.5 \, A$ $i_2 = 0.8333 \, A$

P2.36* $v_1 = 5 \, V$ $v_2 = 7 \, V$ $v_3 = 13 \, V$

P2.37* $i_1 = 1 \, A$ $i_2 = 2 \, A$

P2.38* $v = 3.333 \, V$

P2.43* $R_g = 25 \, m\Omega$

P2.48* $v_1 = 14.29 \, V$ $v_2 = 11.43 \, V$ $i_1 = 0.2857 \, A$

P2.49* $v_1 = 6.667 \, V$ $v_2 = -3.333 \, V$ $i_s = -3.333 \, A$

P2.56* $v_1 = 6 \, V$ $v_2 = 4 \, V$ $i_x = 0.4 \, A$



P2.57* $v_1 = 5.405 \, V$ $v_2 = 7.297 \, V$

P2.65* $i_1 = 2.364 \, A$ $i_2 = 1.818 \, A$ $P = 4.471 \, W$

P2.66* $v_2 = 0.500 \, V$ $P = 6 \, W$

P2.67* $i_1 = 0.2857 \text{ A}$

P2.80*

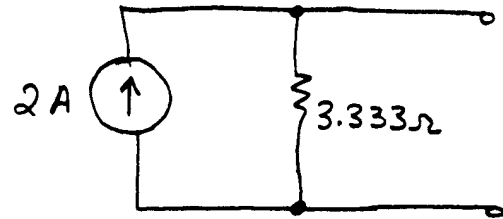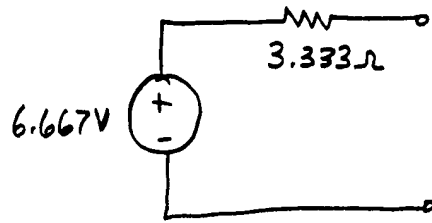

P2.81* $R_x = 50 \Omega$

P2.91* $R_x = 0$ $P_{\max} = 80 \text{ W}$

P2.94* $i_v = 2 \text{ A}$ $i_c = 2 \text{ A}$ $i = i_v + i_c = 4 \text{ A}$

P2.95* $i_s = -3.333 \text{ A}$

P2.103* $R_3 = 5932 \Omega$ $i_{\text{detector}} = 31.65 \times 10^{-9} \text{ A}$

Practice Test

T2.1 (a) 6, (b) 10, (c) 2, (d) 7, (e) 10 or 13 (perhaps 13 is the better answer), (f) 1 or 4 (perhaps 4 is the better answer), (g) 11, (h) 3, (i) 8, (j) 15, (k) 17, (l) 14.

T2.2 The equivalent resistance seen by the voltage source is:

$$R_{eq} = R_1 + \frac{1}{1/R_2 + 1/R_3 + 1/R_4} = 16 \Omega$$

$$i_s = \frac{V_s}{R_{eq}} = 6 \text{ A}$$

Then, using the current division principle, we have

$$i_4 = \frac{G_4}{G_2 + G_3 + G_4} i_s = \frac{1/60}{1/48 + 1/16 + 1/60} 6 = 1 \text{ A}$$

T2.3 Writing KCL equations at each node gives

$$\frac{v_1}{4} + \frac{v_1 - v_2}{5} + \frac{v_1 - v_3}{2} = 0$$

$$\frac{v_2 - v_1}{5} + \frac{v_2}{10} = 2$$

$$\frac{v_3}{1} + \frac{v_3 - v_1}{2} = -2$$

In standard form, we have:

$$0.95v_1 - 0.20v_2 - 0.50v_3 = 0$$

$$-0.20v_1 + 0.30v_2 = 2$$

$$-0.50v_1 + 1.50v_3 = -2$$

In matrix form, we have

$$\mathbf{GV} = \mathbf{I}$$

$$\begin{bmatrix} 0.95 & -0.20 & -0.50 \\ -0.20 & 0.30 & 0 \\ -0.50 & 0 & 1.50 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 2 \\ -2 \end{bmatrix}$$

The MATLAB commands needed to obtain the column vector of the node voltages are

$$G = [0.95 \ -0.20 \ -0.50; \ -0.20 \ 0.30 \ 0; \ -0.50 \ 0 \ 1.50]$$

$$I = [0; \ 2; \ -2]$$

$$V = G \backslash I \quad \% \text{ As an alternative we could use } V = \text{inv}(G) * I$$

Actually, because the circuit contains only resistances and independent current sources, we could have used the short-cut method to obtain the \mathbf{G} and \mathbf{I} matrices.

T2.4 We can write the following equations:

$$\text{KVL mesh 1: } R_1 i_1 - V_s + R_3 (i_1 - i_3) + R_2 (i_1 - i_2) = 0$$

KVL for the supermesh obtained by combining meshes 2 and 3:

$$R_4 i_2 + R_2 (i_2 - i_1) + R_3 (i_3 - i_1) + R_5 i_3 = 0$$


KVL around the periphery of the circuit:

$$R_1 i_1 - V_s + R_4 i_2 + R_5 i_3 = 0$$


$$\text{Current source: } i_2 - i_3 = I_s$$

A set of equations for solving the network must include the current source equation plus two of the mesh equations. The three mesh equations are dependent and will not provide a solution by themselves.

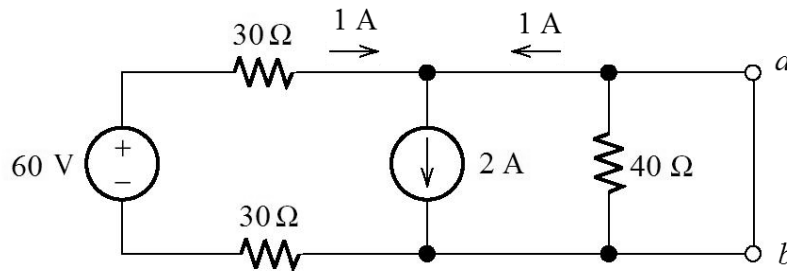T2.5 Under short-circuit conditions, the circuit becomes



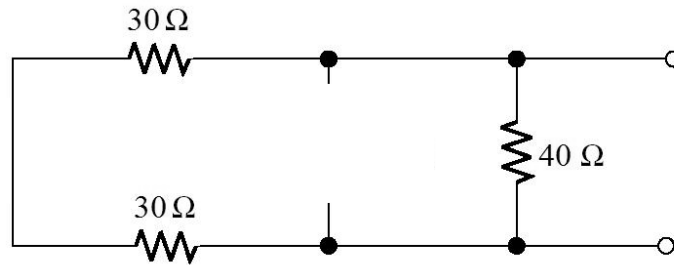
Thus, the short-circuit current is 1 A flowing out of b and into a .
Zeroing the sources, we have



Thus, the Thévenin resistance is


$$R_t = \frac{1}{1/40 + 1/(30 + 30)} = 24 \Omega$$

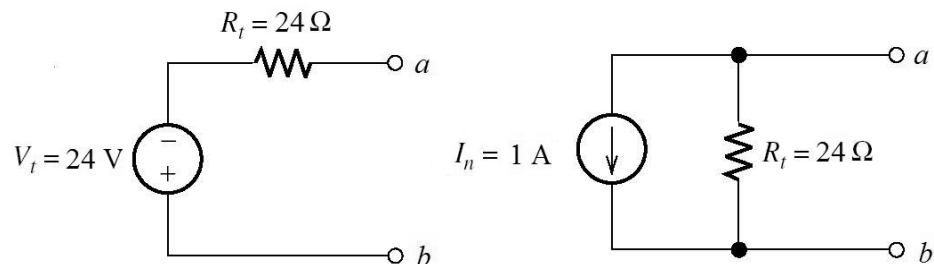
and the Thévenin voltage is $V_t = I_{sc} R_t = 24 \text{ V}$. The equivalent circuits are:




Because the short-circuit current flows out of terminal b , we have oriented the voltage polarity positive toward b and pointed the current source reference toward b .

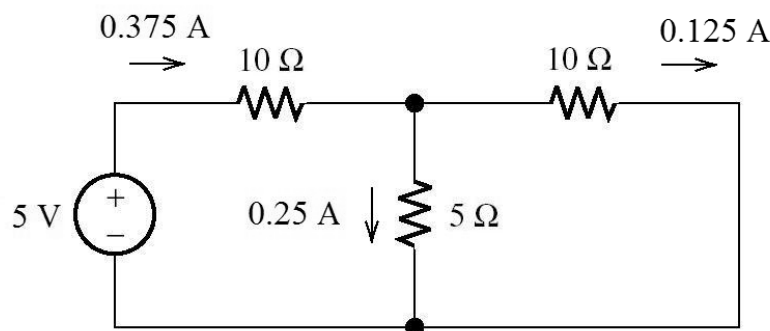T2.6 With one source active at a time, we have



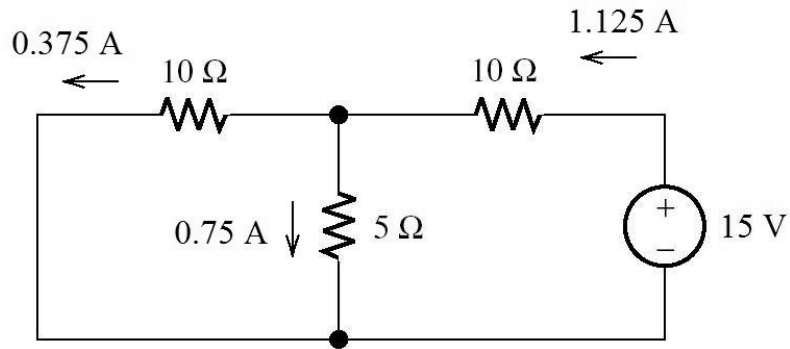

Then, with both sources active, we have

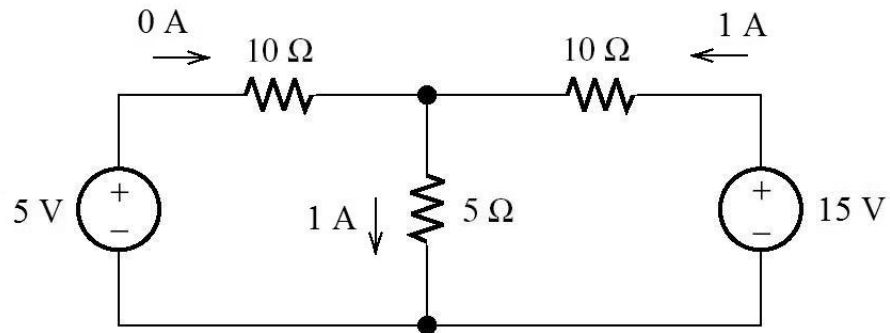

We see that the 5-V source produces 25% of the total current through the 5- Ω resistance. However, the power produced by the 5-V source with both sources active is zero. Thus, the 5-V source produces 0% of the power delivered to the 5- Ω resistance. Strange, but true! Because power is a nonlinear function of current (i.e., $P = Ri^2$), the superposition principle does not apply to power.