

CG1108 Sem 2 AY2010/11

**Part2
Lecture 5**



^{DC}
Steady-state



DC Transients

- Learning objectives:
 - Understand the meaning of transients. ✓
 - Write differential equations for circuits containing inductors and capacitors.
 - Solving differential equations to find the time value of voltages and currents
 - Use of Oscilloscope and Signal generator

Transients

- The time-varying voltages and currents resulting from the adding or removing voltage and current source to circuits containing energy storage elements, are called **transients.** ✓
- Voltage and current in such circuits are represented by **First-order differential equations.**

First-order circuits with DC supply

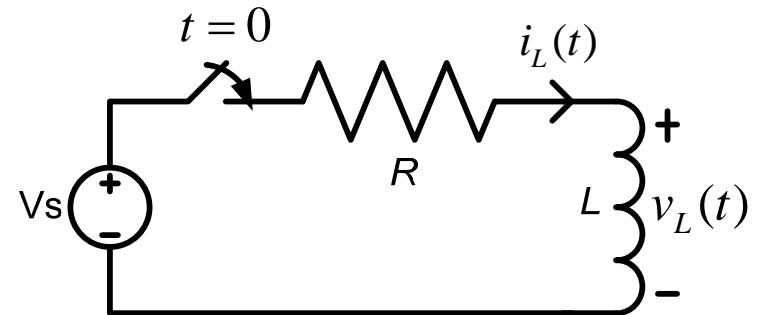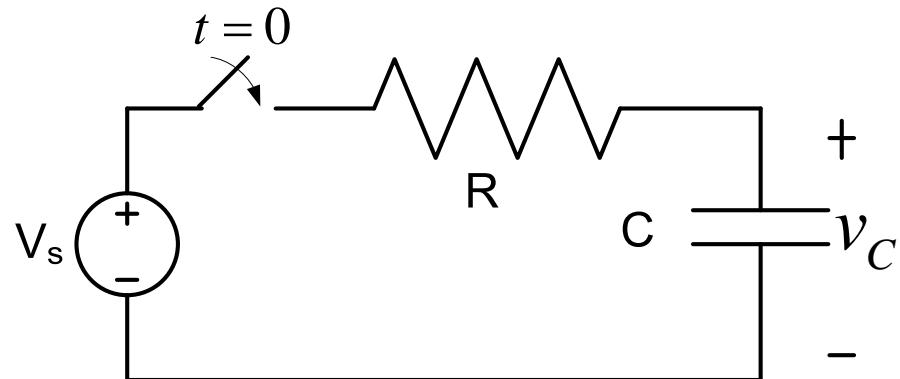

$$\cancel{RC \frac{dv_c}{dt} + v_c = V_s} \quad \checkmark$$

$$x = v_c$$

$$\tau = RC$$

$$K' = V_s$$

$$v_c(s) = V_s$$

$$\cancel{-\frac{\tau}{dt} \frac{dx}{dt} + x = K'} \quad \uparrow$$

$$\frac{dx}{dt} = 0$$

$$\cancel{\frac{L}{R} \frac{di_L}{dt} + i_L = \frac{V_s}{R}}$$

$$x = i_L$$

$$\tau = \frac{L}{R}$$


$$K' = \frac{V_s}{R}$$

$$i_L(s) = \frac{R}{R} \frac{V_s}{R}$$

Solution of Differential eqn

$$\tau \frac{dx}{dt} + x(t) = K'$$

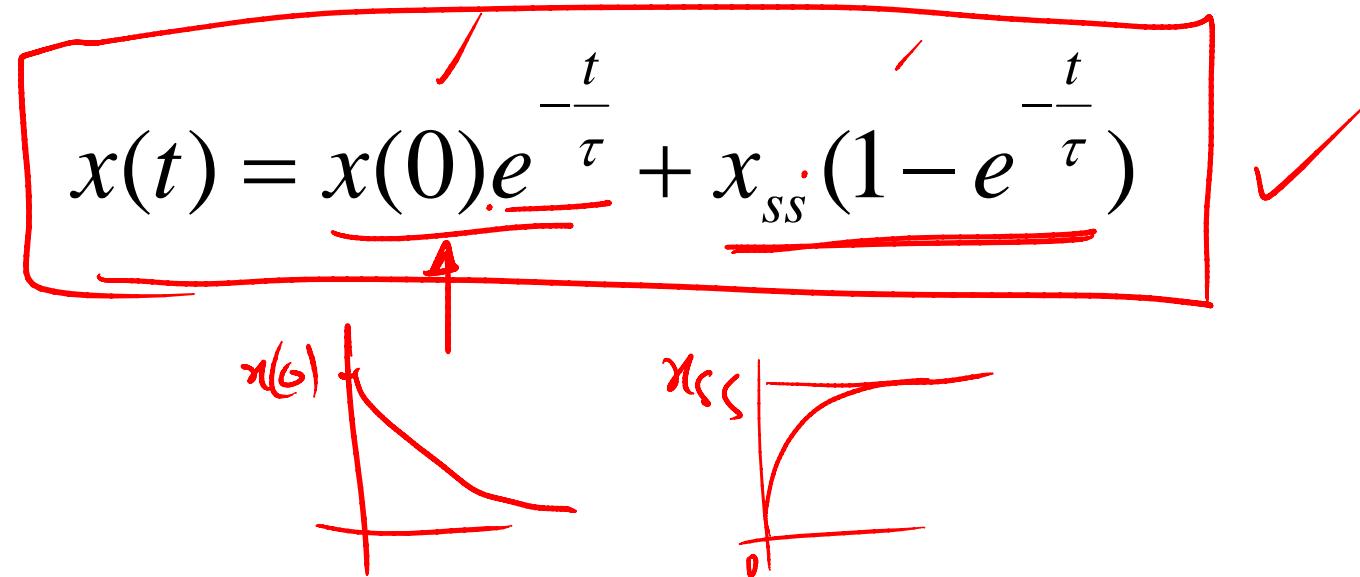For DC circuits, $\frac{dx(t)}{dt} = 0, x_{ss} = K'$




Nature of the solution

$$x(t) = x(0)e^{-\frac{t}{\tau}} + x_{ss}(1 - e^{-\frac{t}{\tau}})$$

τ = Time constant

n	e^{-n}	$(1 - e^{-n})$
0	1	0
1	0.367879	0.632121
2	0.135335	0.864665
3	0.049787	0.950213
4	0.018316	0.981684
5	0.006738	0.993262
6	0.002479	0.997521
7	0.000912	0.999088

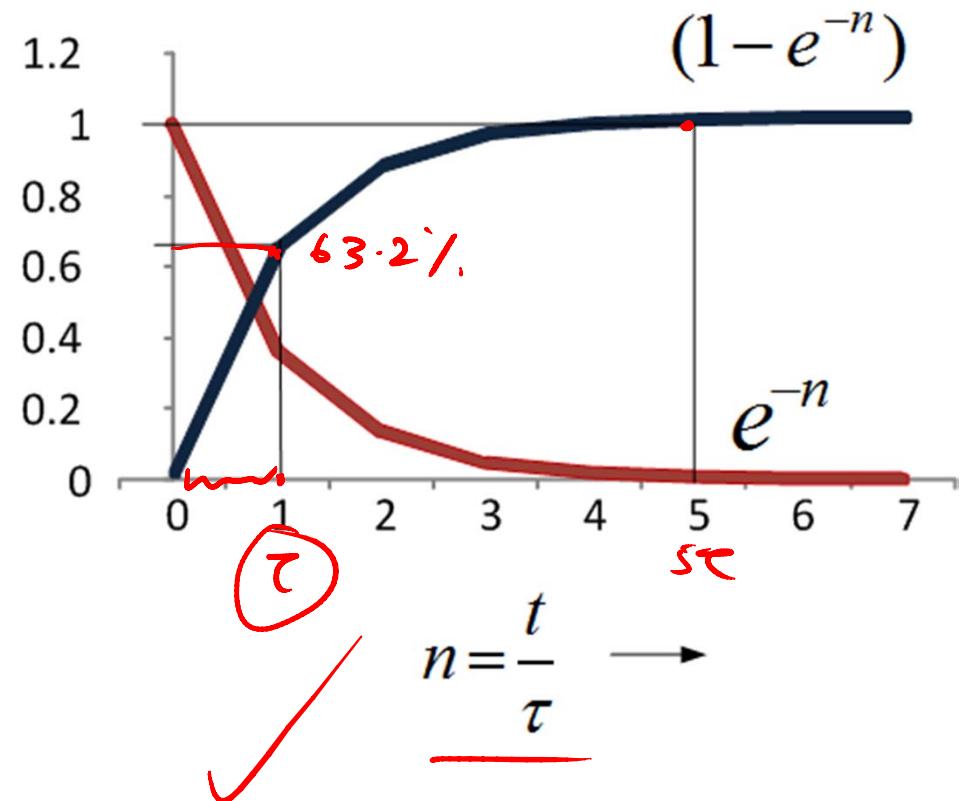

RC and RL comparing to the general form

$\tau \frac{dx}{dt} + x = K'$ where K' is the steady - state solution (x_{ss})

$$x(t) = x(0)e^{-\frac{t}{\tau}} + x_{ss}(1 - e^{-\frac{t}{\tau}})$$


$$RC \frac{dv_c}{dt} + v_c = V_s$$

$$v_c(t) = v_c(0) \cdot e^{-\frac{t}{RC}} + V_s \left(1 - e^{-\frac{t}{RC}}\right)$$

$$\frac{L}{R} \frac{di_L}{dt} + i_L = \frac{V_s}{R}$$

$$i_L(t) = i_L(0) \cdot e^{-\frac{t}{L/R}} + \frac{V_s}{R} \left(1 - e^{-\frac{t}{L/R}}\right).$$

Example2

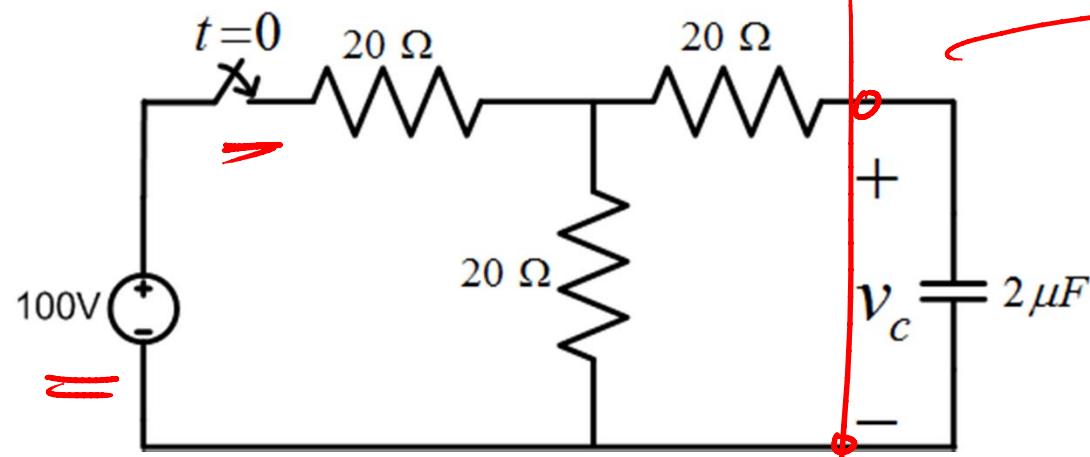


$$v_c(t) = 50 \left(1 - e^{-\frac{t}{60 \times 10^6}} \right) V$$

$v_c(t)$ for $t > 0$.



$$v_c(0) = 0$$

$$\therefore v_{c,ss} = 50$$

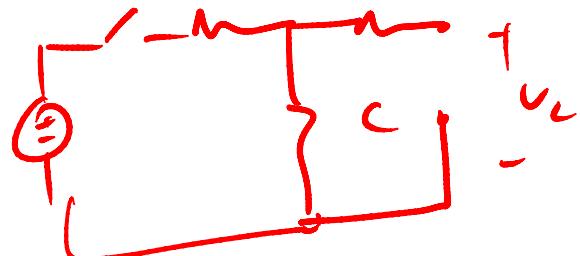
$$\therefore \tau = R_{TH} \times C = 30 \times 2 \times 10^6 = 60 \text{ ms}$$






$$V_{TH} =$$

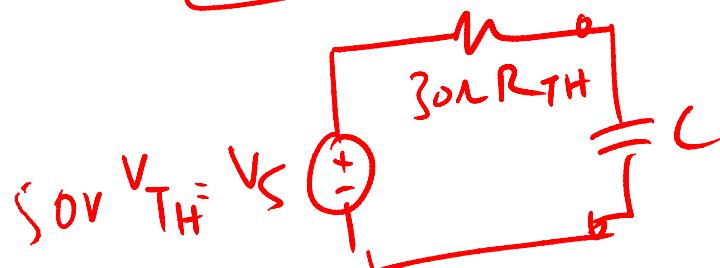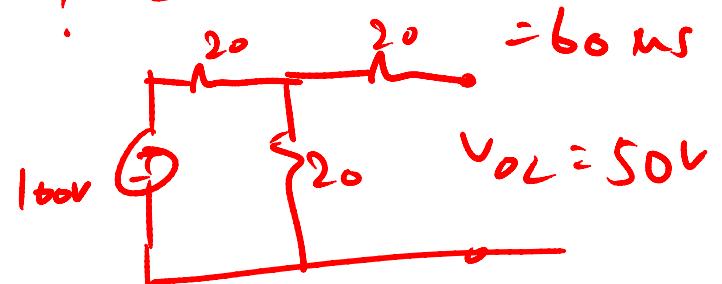

$$R_{TH} =$$

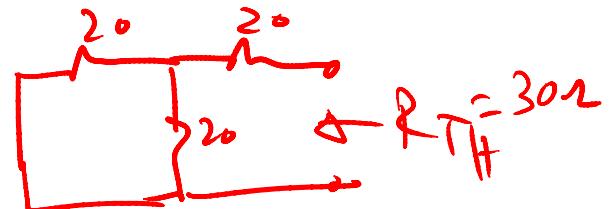

Example3

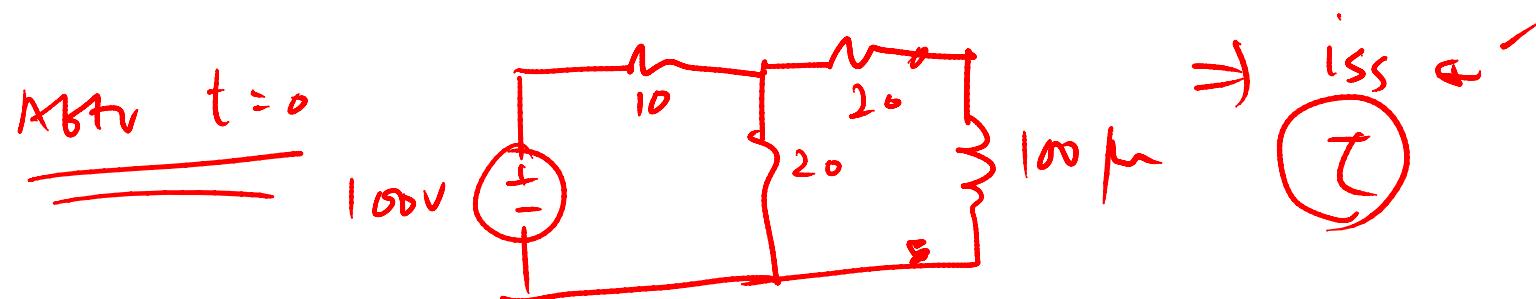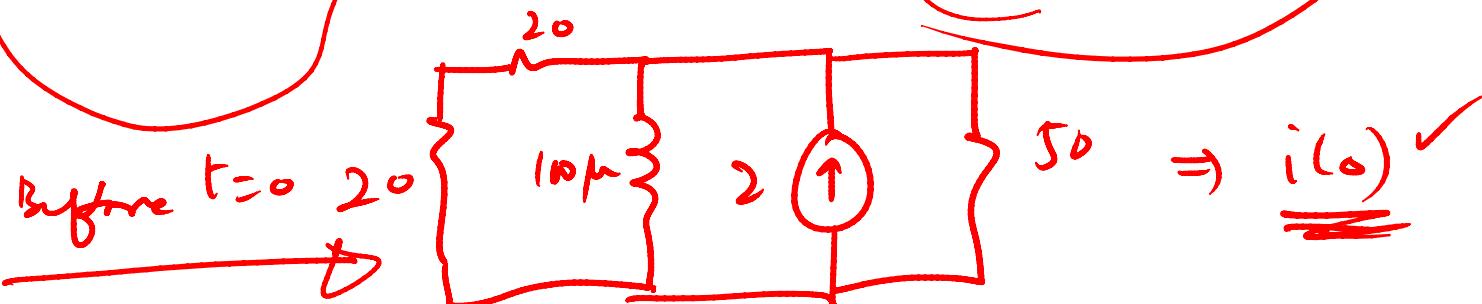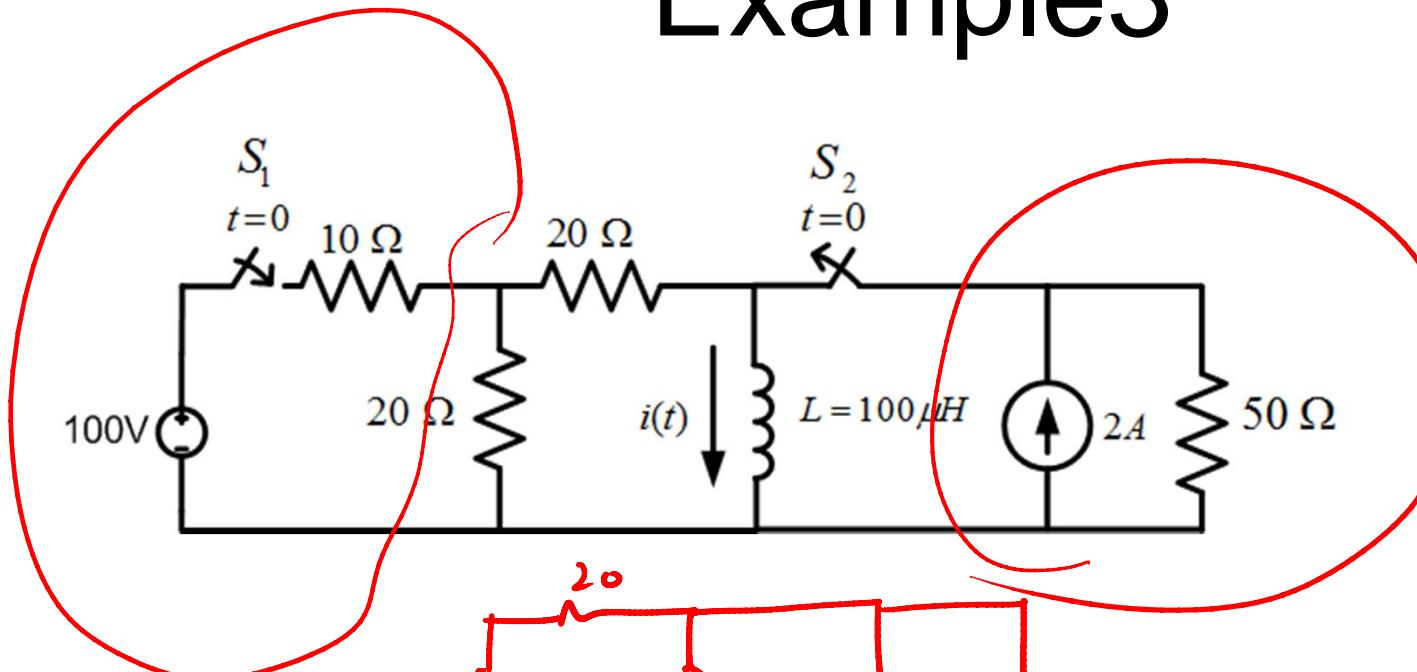

Summary of DC transients

- ① Understand behaviour of Capacitor and Inductor
in DC steady state.

Cap \rightarrow open circuit

Ind \rightarrow short circuit

- ② Thvenin equivalent

- ③ Apply the transient formula

$$x(t) = x(0) e^{-t/\tau} + x_{ss} (1 - e^{-t/\tau})$$




Lab4: Objectives


- To learn about the behavior of capacitors and inductors in DC circuits.
- To learn about the use of the Oscilloscope.
- To measure the time constants for RC, RL circuits using the oscilloscope.

Oscilloscope

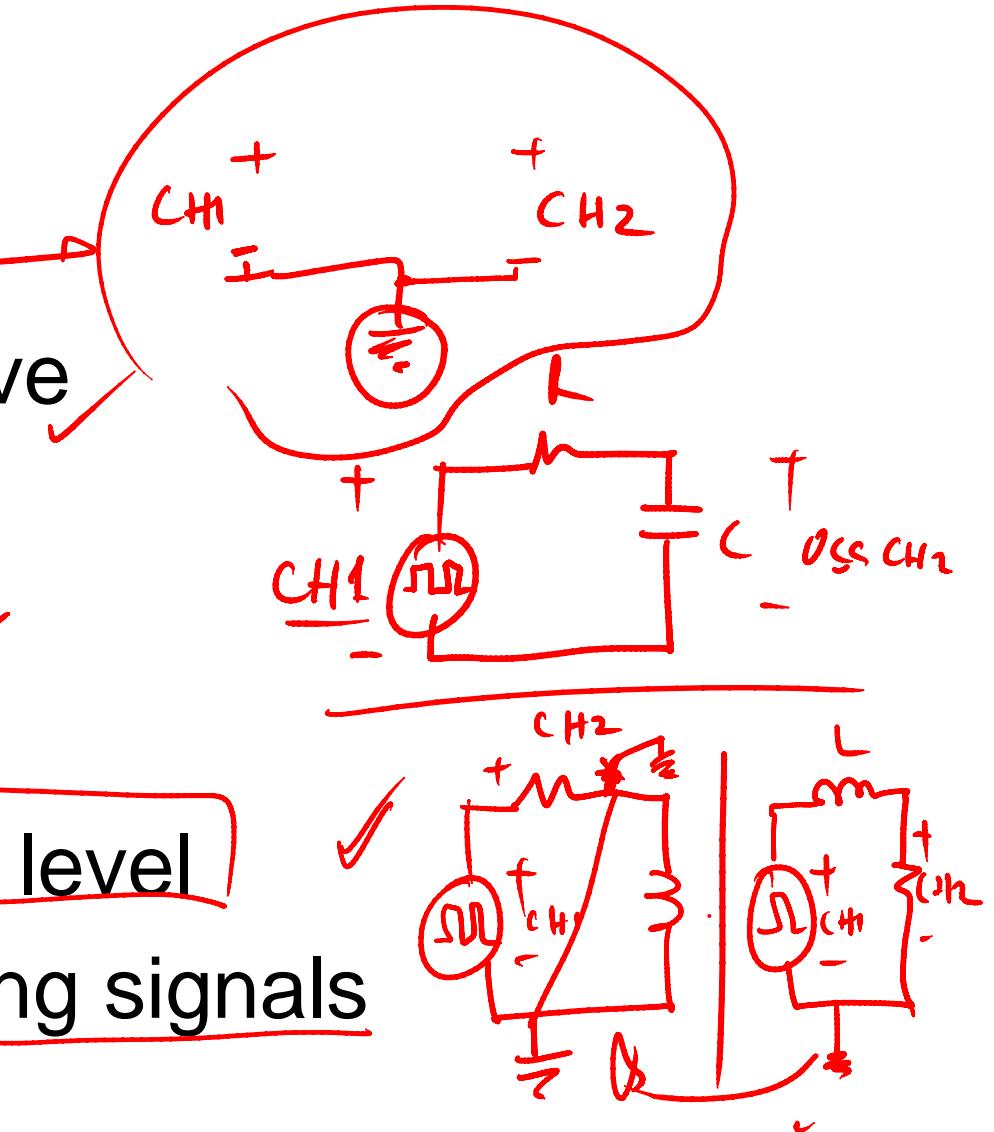- Basic function
- The probe
- Internal square wave
- Auto-setup ✓
- Vertical scale ✓
- Horizontal scale ✓
- Trigger source and level
- Cursor for measuring signals



Observations in Lab4

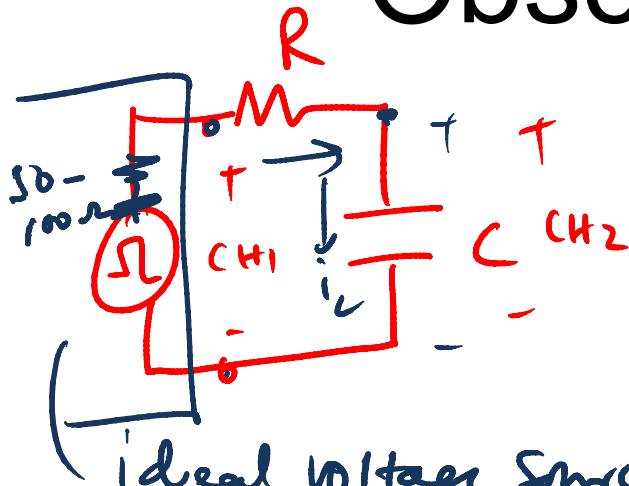


ideal Voltage Source

$$i_C(0^+) = \frac{5 - V_C^0}{R_S + R}$$

$$i_C(T/2) = \frac{5 - V_C(T/2)}{R_S + R}$$


$$= 0 .$$

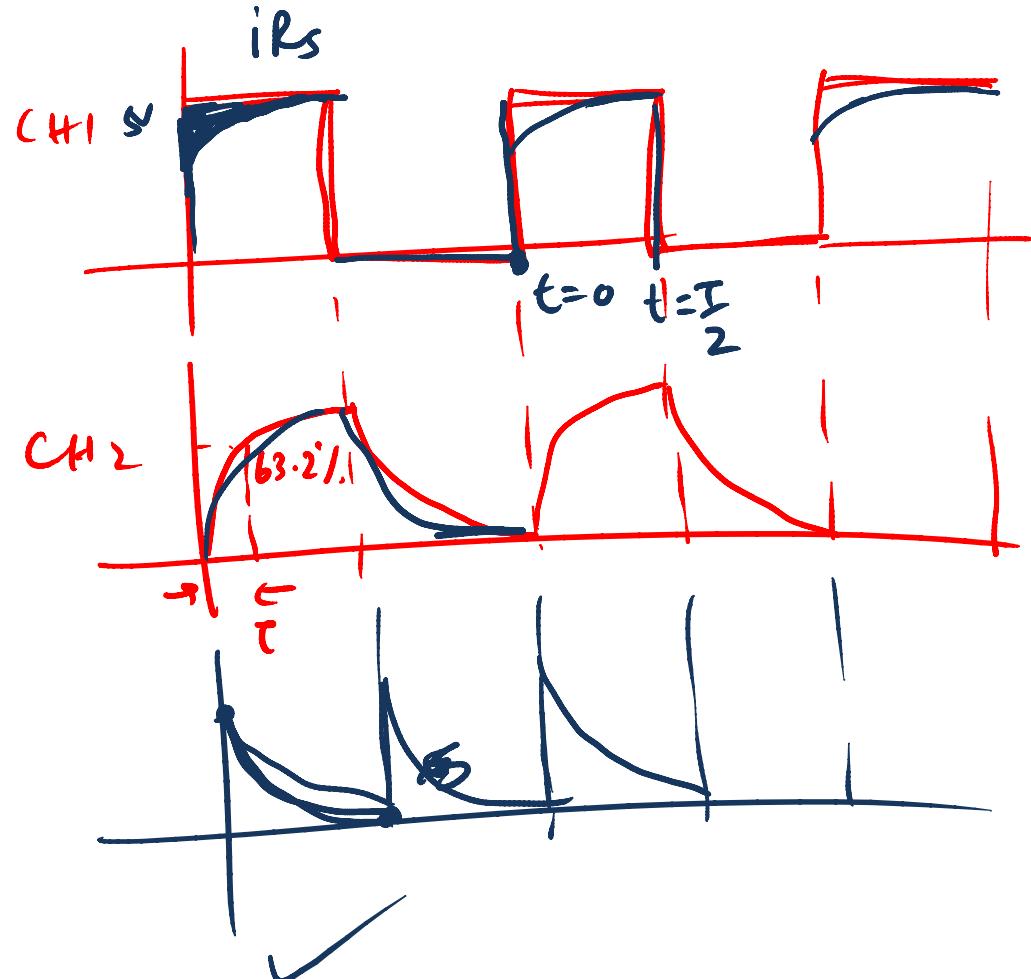


CG1108 AY2010/11 Sem2

Lecture 6

Learning objectives

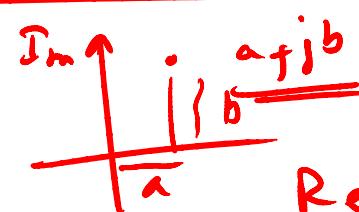- Time-varying sources ✓
- RMS (Root Mean Square) value for A.C.
- Sinusoids : $\sin(\omega t + \theta)$, $\cos(\omega t + \theta)$ ✓
- Complex algebra $|+j2|$ 
- Phasor
- Impedances
- AC ckt analysis with phasors and impedances ✓


Time dependent sources

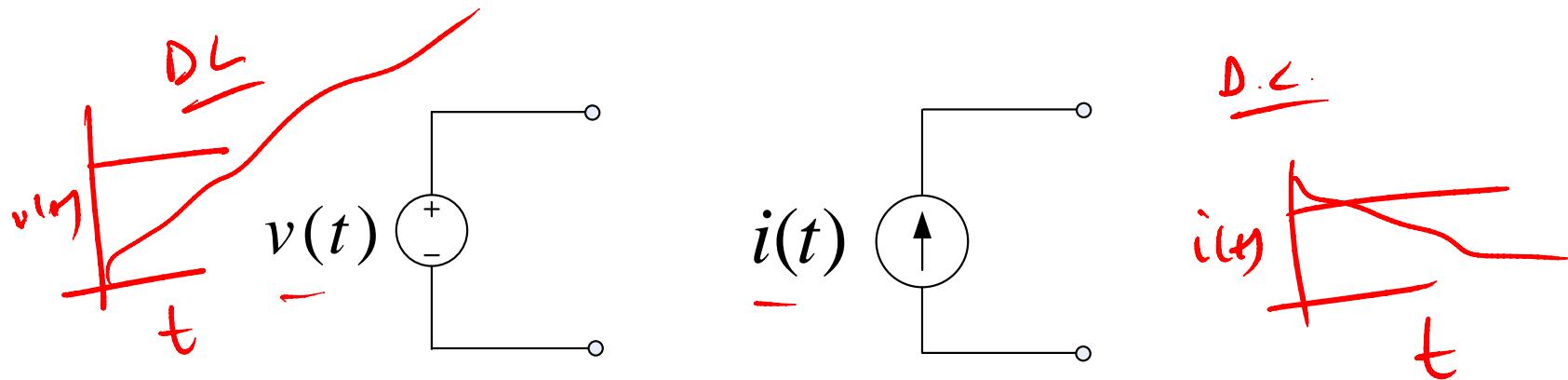


- Periodic functions

$$\underline{x(t) = x(t + nT), \quad n = 1, 2, 3, \dots}$$


T = Time period

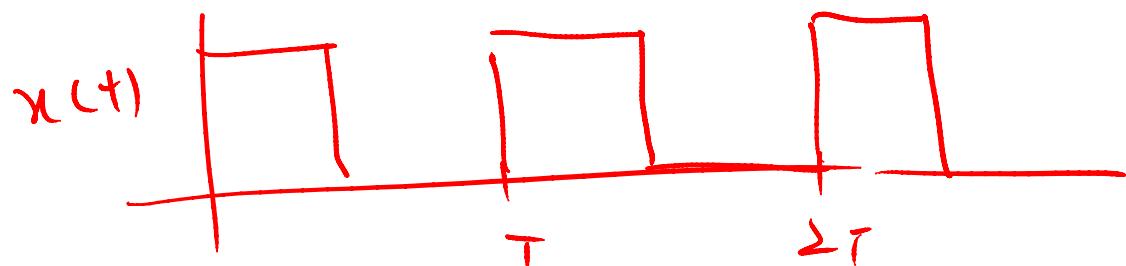


Common periodic signals

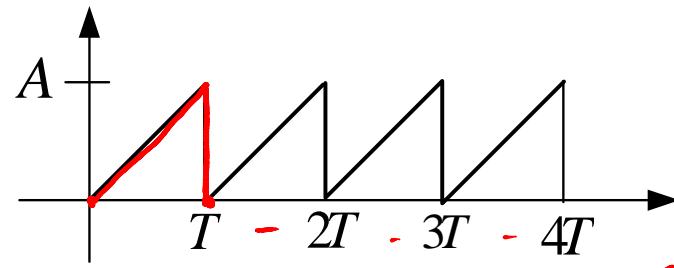


Sawtooth wave ✓

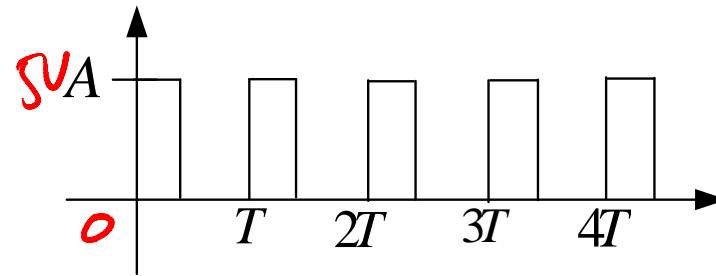

Pulse train (TTL) ✓

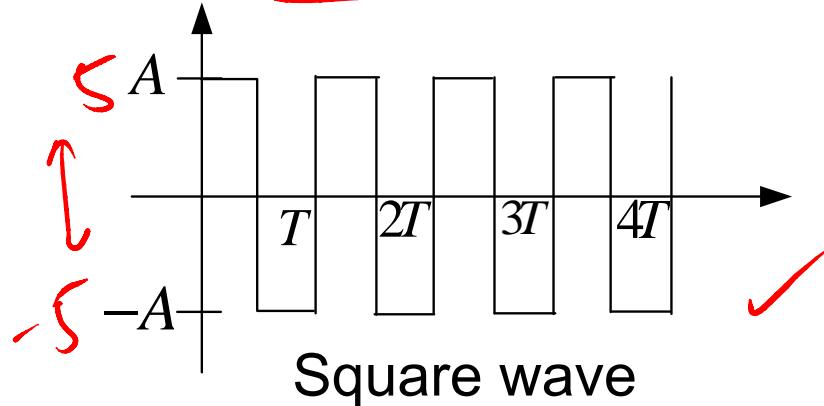

Square wave ✓

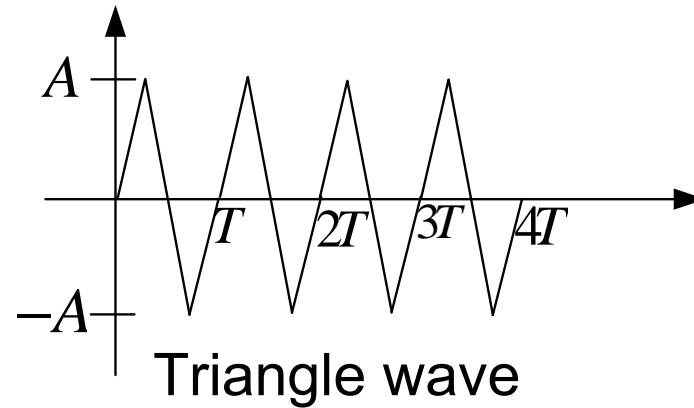

Triangle wave ✓✓

Periodic signals

- The time period of the signal is defined as the time taken to complete one cycle
- The frequency of the periodic signal is the number of cycles completed in one second. The units of frequency are hertz (Hz).
- Angular frequency (radians per second) , as one period in time corresponds to radian.

$$\omega = 2\pi f$$

Root-mean-square (RMS) values

$$p(t) = \frac{v^2(t)}{R}$$

$$E_T = \int_0^T p(t) dt = \int_0^T \frac{v^2(t)}{R} dt$$


$$P_{avg} = \frac{E_T}{T} = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{T} \int_0^T \frac{v^2(t)}{R} dt = \frac{\left(\frac{1}{T} \int_0^T v^2(t) dt \right)}{R}$$

average power =


$$= \frac{1}{T} \int_0^T p(t) dt$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$P_{avg} = \frac{V_{rms}^2}{R}$$

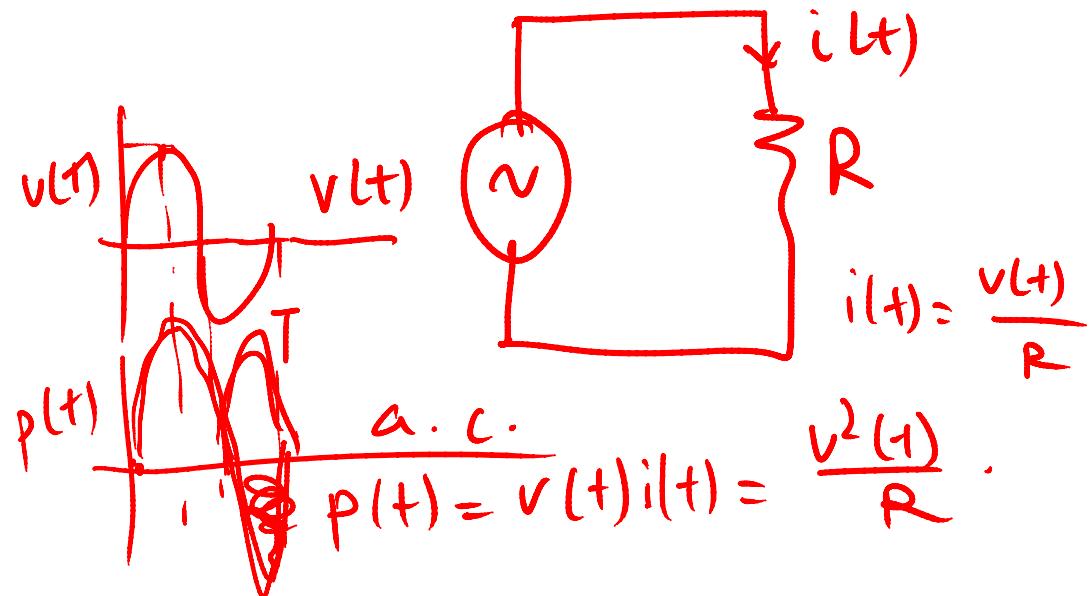

Sinusoidal signals

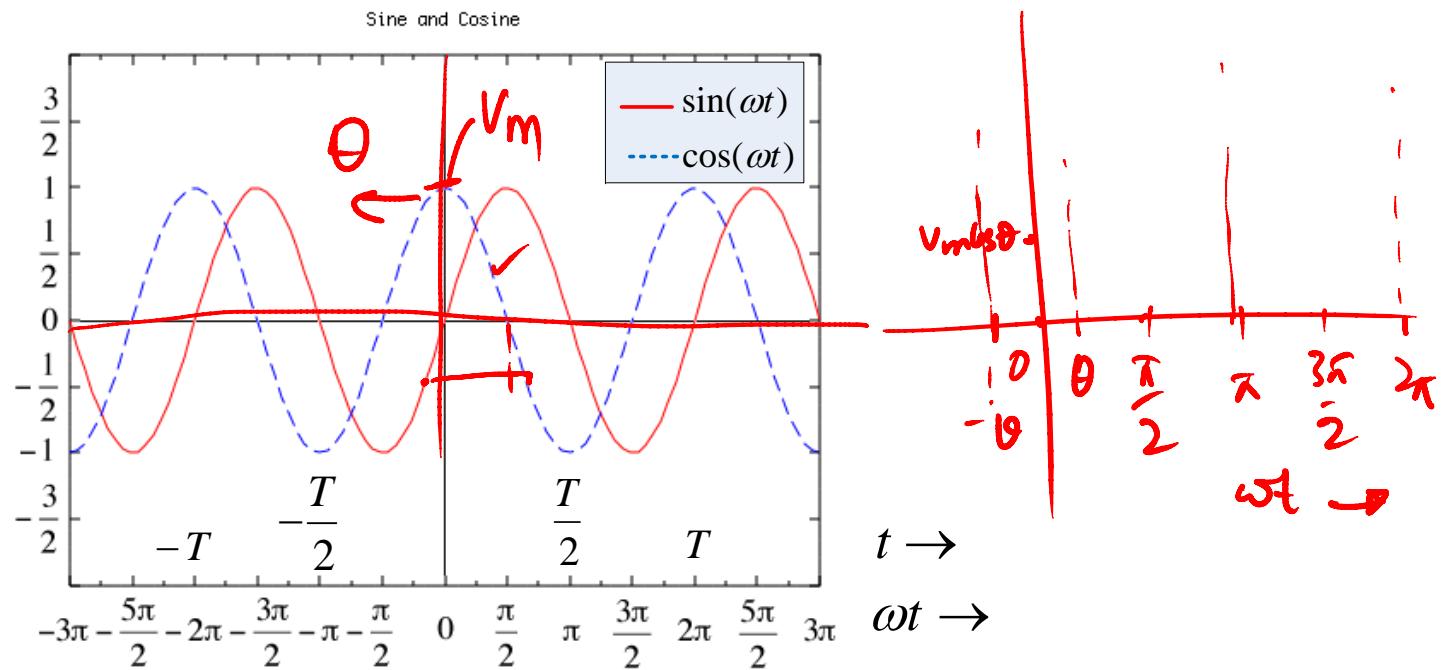

$$v(t) = V_m \cos(\omega t + \theta)$$

V_m is the peak value of the voltage

$$V_m = V_m \cos(\omega t + \theta)$$

θ is the phase angle

$$\omega t + \theta = 0$$

$\omega t = -\theta$, ω = angular freq

At $t = 0$

$$v(t) = V_m \cos \theta$$


RMS for a sinusoid

$$\begin{aligned} V_{rms} &= \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} = \sqrt{\frac{1}{T} \int_0^T V_m^2 \cos^2(\omega t + \theta) dt} \\ &= \sqrt{\frac{1}{T} \frac{V_m^2}{2} \int_0^T (1 + \cos 2(\omega t + \theta)) dt} = \sqrt{\frac{V_m^2}{2}} = \frac{V_m}{\sqrt{2}} \quad \checkmark \end{aligned}$$

- For example when we say the PUB supply in Singapore is 230V, we mean that the RMS value of the PUB supply is 230V and its peak value would be

$$V_m = \sqrt{2} V_{rms} = 230 \times \sqrt{2} = 230 \times 1.414 = \underline{\underline{325V}}$$

Circuits with sinusoidal sources

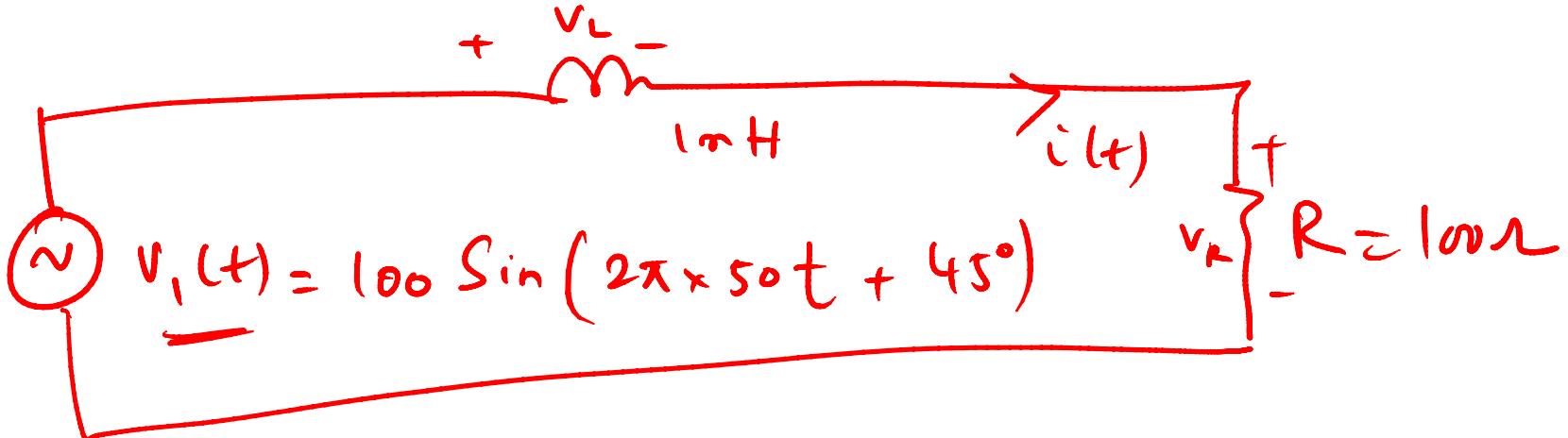

$$v_L = L \frac{di}{dt}$$

$$v_1(t) = v_L(t) + v_R(t)$$

$$L \frac{di(t)}{dt} + iR = v_1(t)$$

Solve diff eqn


with sinusoidal forcing

func?

$f(t)$
Forcing
fn

Complex number

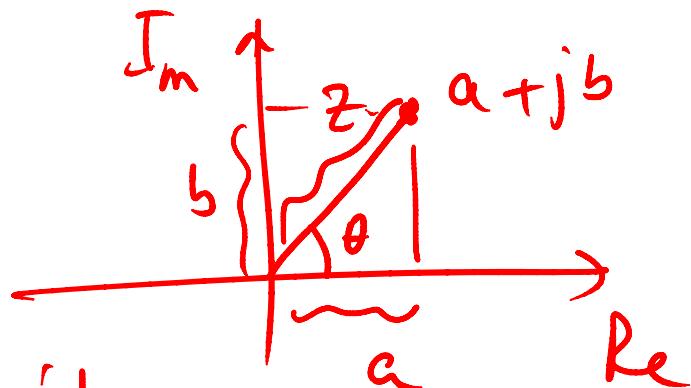- Complex plane
 - Real axis
 - Imaginary axis
- Rectangular form
- Polar form
 - Magnitude
 - Angle
- Complex algebra



$$: \underline{a+jb}$$

$$z = \sqrt{a^2 + b^2} \quad \theta = \tan^{-1}\left(\frac{b}{a}\right)$$

$$A = 1+j2$$

$$B = 0.5 + j1$$

$$A - B = \underline{(1-0.5)} + j(2-1) = 0.5 + j(-1)$$

$$A * B = (1+j2)(0.5+j1) =$$

Complex algebra

- Addition/Subtraction

- Done in rectangular form

$$A = a_1 + j b_1$$
$$\theta = z_1 \angle \theta_1$$

- Multiplication/Division

- Done in polar form

$$B = a_2 + j b_2$$
$$= z_2 \angle \theta_2$$

$$A * B = z_1 \cdot z_2 \angle \underline{\theta_1 + \theta_2}$$

$$A \div B = (z_1 \div z_2), \underline{\theta_1 - \theta_2}$$

Rect \rightarrow Polar

Phasor

- Sinusoidal voltages and currents can be represented as vectors in a complex plane. *Complex Number*
- These are called Phasors and are very useful in steady-state analysis of sinusoidal voltages and currents.
- Phasor is just a definition. This gives rise to mathematical convenience. It has no physical significance.

Phasor Definition


- For a sinusoidal voltage of

$$v_1(t) = \overset{\circ}{V}_1 \cos(\overset{\circ}{\omega}t + \overset{\circ}{\theta})$$

- we define the phasor as: $\overset{\circ}{V}_1 = \overset{\downarrow}{V}_1 \angle \overset{\downarrow}{\theta}_1$

- Thus, phasor of a sinusoid is a complex number having a magnitude equal to the peak value and having the same phase angle as the sinusoid.

Euler's identity

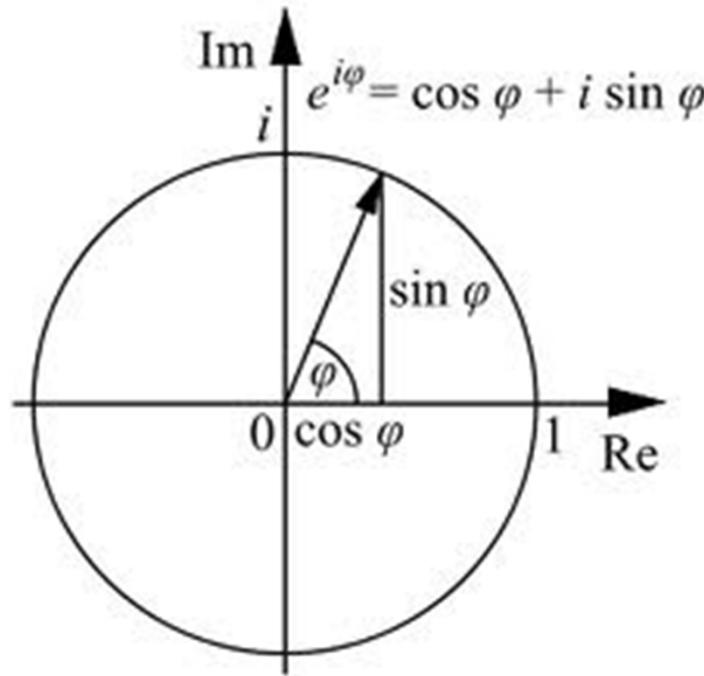

$$e^{j\alpha} = \cos \alpha + j \sin \alpha$$

$$\cos \alpha = \operatorname{Re}(e^{j\alpha})$$

$$\cos(\omega t + \theta) = \operatorname{Re}(e^{j(\omega t + \theta)})$$

$$V_m \cos(\omega t + \theta) = \operatorname{Re}(V_m e^{j(\omega t + \theta)})$$


$$V_m e^{j(\omega t + \theta)} = V_m e^{j\theta} \times e^{j\omega t}$$

Phasor as a rotating vector

- represents a vector in the complex plane whose magnitude is A and whose angle with the real axis is θ . The angle changes with time or in other words the vector keeps rotating at the angular speed of ω rad/sec. and its angle at $t=0$ was ϕ_0 .
- The projection of the vector along the real axis will be the original sinusoidal function
- The phasor can be thought of as a snap shot of the rotating vector at $t=0$.

Phasor Diagram
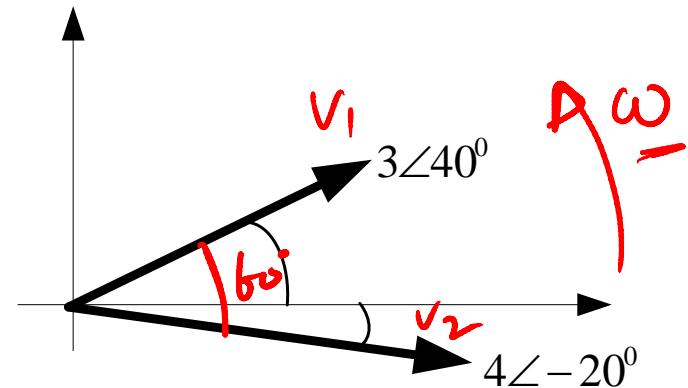
$$v_1(t) = \underline{3 \cos(\omega t + 40^\circ)} \rightarrow \underline{\underline{3 \angle 40^\circ}}$$
$$\underline{v_2(t) = 4 \cos(\omega t - 20^\circ)} \rightarrow \underline{\underline{4 \angle -20^\circ}}$$




- Leading / lagging**

v_1 leads v_2 by $(40 - (-20)) = 60^\circ$

v_2 lags v_1 by 60° .

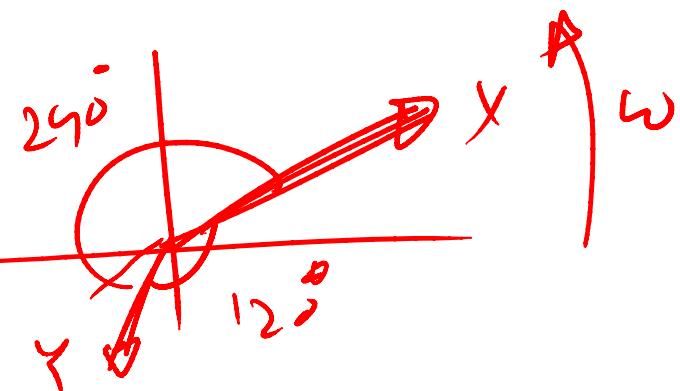y is lagging x by 120°
 y is leading x by 240°




Impedances

- Also known as complex resistance,
frequency-dependent resistance.
- With understanding of impedances for the circuit elements like resistance, inductance and capacitance, the sinusoidal steady-state analysis will be same as analysis of purely resistive circuits under DC supply.

Inductance
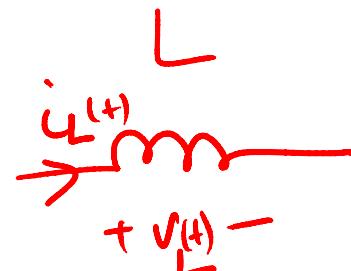
$$i_L(t) = I_m \sin(\omega t + \theta) = I_m \cos(\omega t + \theta - 90^\circ)$$



$$\checkmark v_L(t) = L \frac{di_L(t)}{dt} = L\omega I_m \cos(\omega t + \theta) \quad \checkmark$$

$$\underline{I_L} = \underline{(I_m) \angle \theta - 90^\circ}$$

$$I_L = I_m \angle \theta - 90^\circ, \quad V_L = L\omega I_m \angle \theta$$

$$\underline{V_L} = \underline{\omega L I_m} \angle \theta = \underline{\omega L \angle 90^\circ} \times \underline{I_m \angle \theta - 90^\circ} = Z_L \times I_L$$

$$\underline{Z_L} = \underline{\omega L \angle 90^\circ} = j\omega L \quad : \quad \text{Impedance of an inductor.}$$

$$\text{Ohm's law} = V = \underline{R} \cdot \underline{I}$$

↓
Complex
resistance
Freq. dependent
impedance

Capacitance

$$V_c = Z_c I_c$$

$$Z_c = -j \frac{1}{\omega C} = \frac{1}{j\omega C} = \frac{1}{\omega C} \angle -90^\circ$$

$$- \sin \theta = \cos(\theta + \frac{\pi}{2})$$

$$V_c(t) \rightarrow V_C = V_m \angle \theta$$

$$i_c(t) \rightarrow I_c = C \omega V_m \angle \theta + \frac{\pi}{2} = C \omega \left(\frac{\pi}{2} \cdot V_m \right) \angle \theta$$

$$\frac{1}{Z_c} = C \omega \angle \frac{\pi}{2}$$

$$Z_c = \frac{1}{C \omega} \angle -\frac{\pi}{2}$$

$$i_c = C \frac{dV_c}{dt}$$

A circuit diagram showing a capacitor symbol (two parallel lines) connected to a battery with voltage \$V_c\$.

$$V_c(t) = V_m \cos(\omega t + \theta)$$

$$i_c = C \cdot V_m \cdot \omega (-i) \cdot \sin(\omega t + \theta)$$


$$= C V_m \omega \cos(\omega t + \theta + \frac{\pi}{2})$$

Resistance


$$V_R = RI_R$$

$$\mathcal{Z}_R = R$$


Impedances for R, L and C

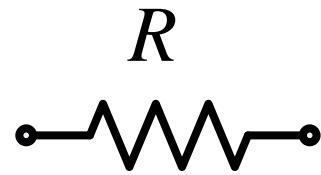


$$Z_R = R$$

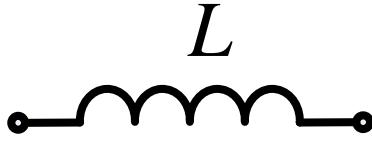


$$Z_L = j\omega L$$

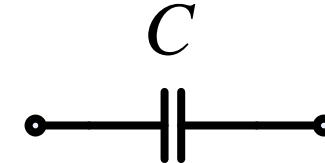


$$Z_C = \frac{1}{j\omega C}$$

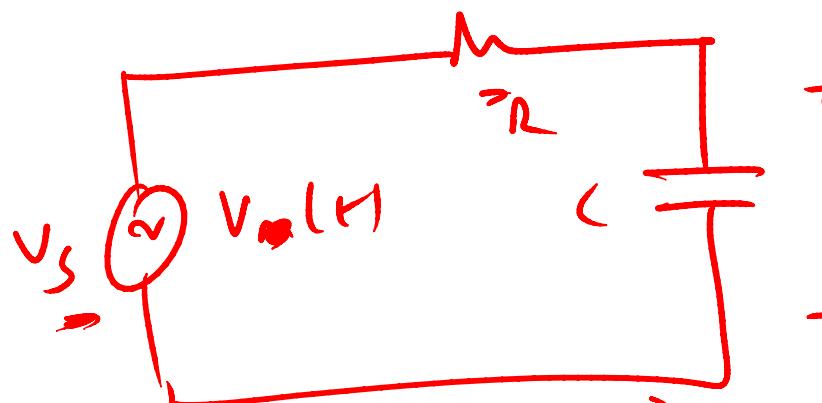
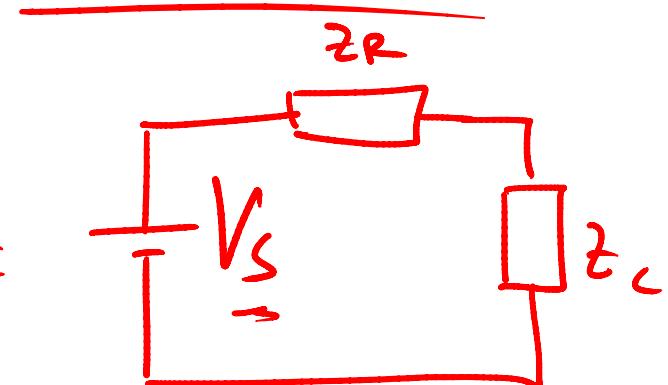
$$V_C = V_S \cdot \frac{Z_C}{Z_R + Z_C}$$



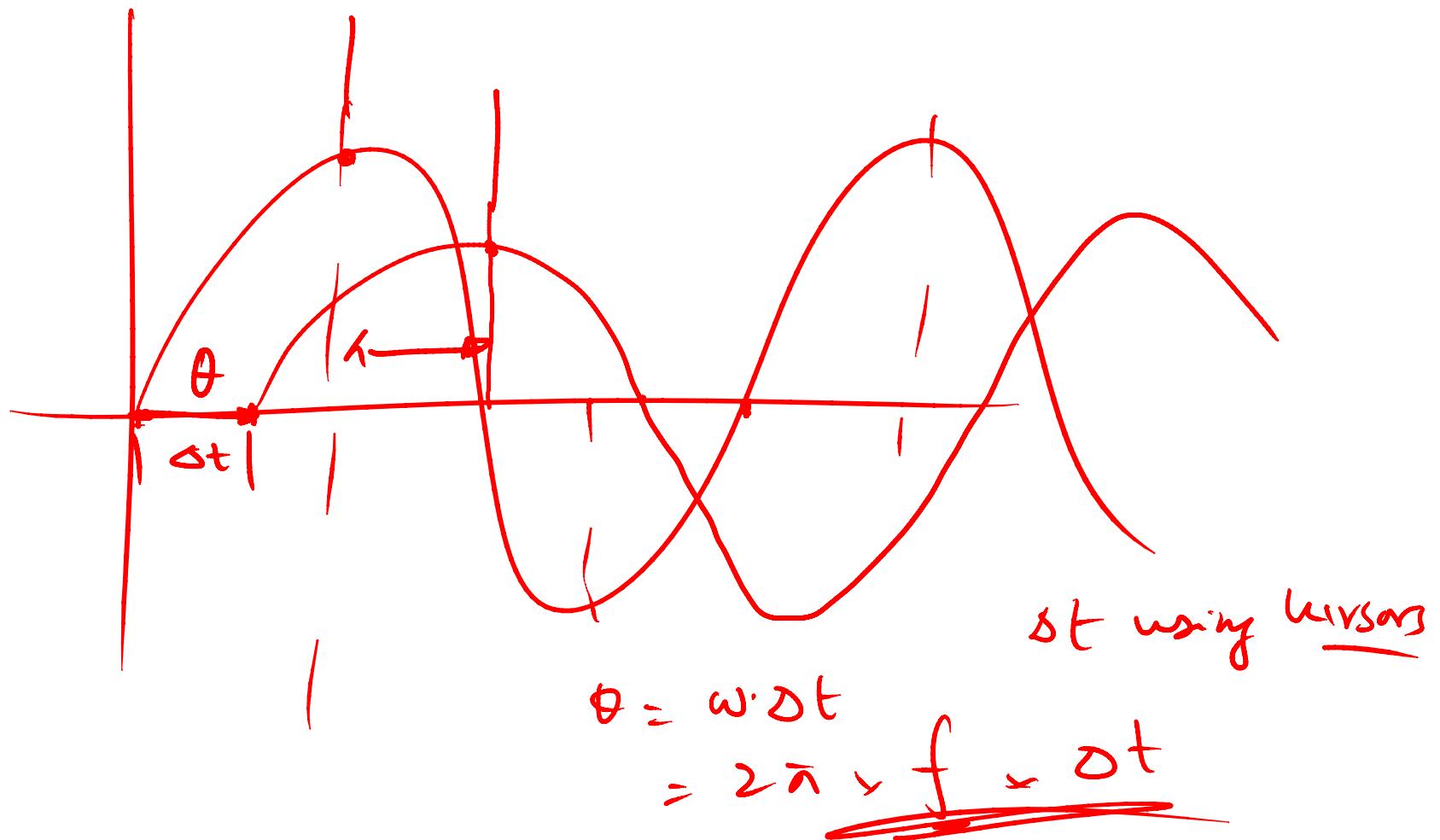Circuit Analysis with phasors and Complex Impedances





Step-by-step procedures for steady-state analysis of circuits with sinusoidal sources:

- All sources must have the same frequency.
- Replace the time descriptions of the voltage and current sources with the corresponding phasors.
- Replace the inductance with its impedance and capacitance with its impedance of . Resistances have the same impedance as their resistance.

Step-by-step procedures for steady-state analysis of circuits with sinusoidal sources:





- Analyze the circuits as before with DC sources and resistances only.
- Convert the final results in phasor to time-domain form

Example

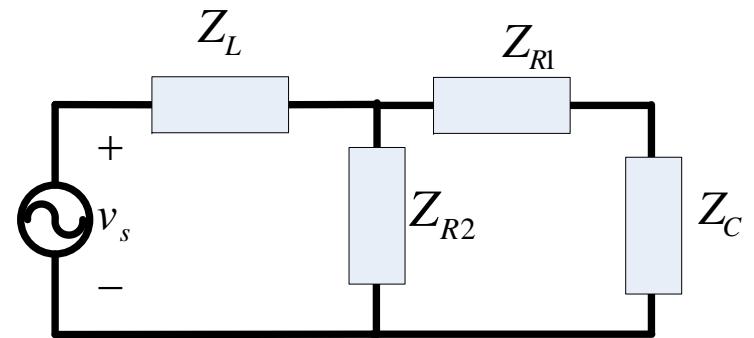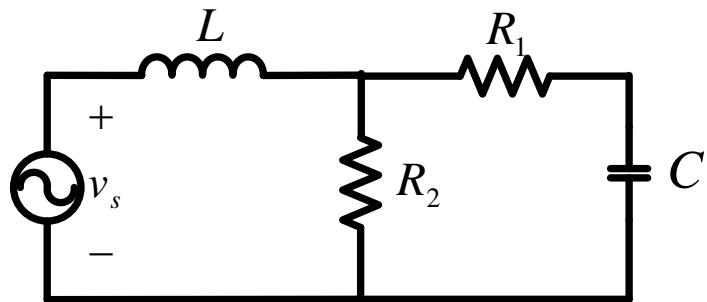


Lab5 Studying AC signals

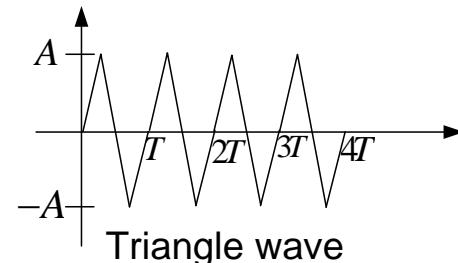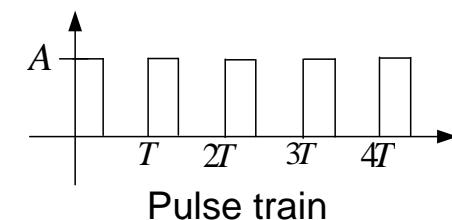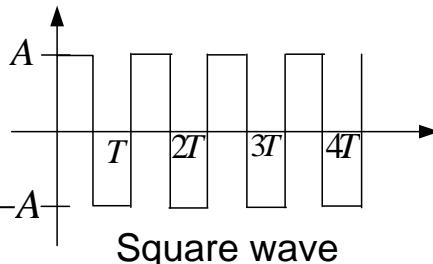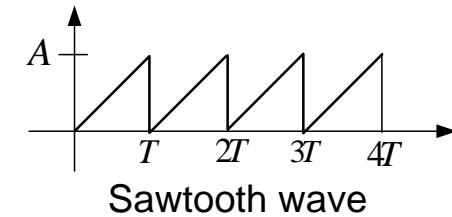- Observing various types of ac signals using signal generator and oscilloscope.
- Measuring RMS of the signals with same peak-to-peak.



Measuring Phase difference

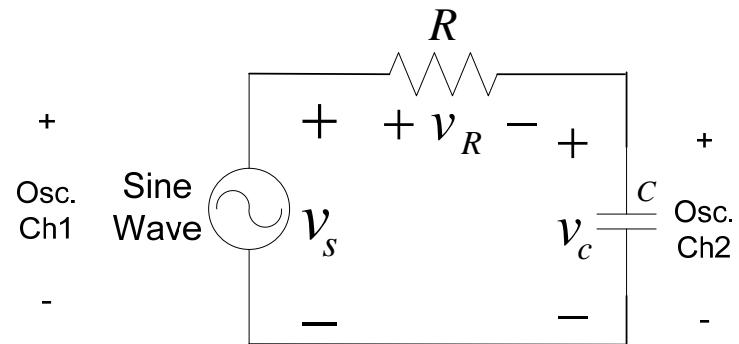

Measuring Phase difference

