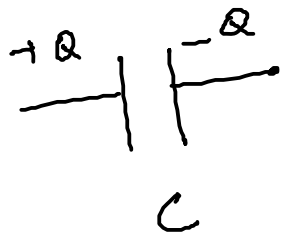


1. A voltage of 50V appears across a 10 μ F capacitor.
 - a) Determine the magnitude of net charge stored on each plate and total net charge on both the plates.
 - b) Calculate the energy stored in the capacitor.
 - c) If the capacitor is discharged by a steady current of 100 μ A. How long does it take to discharge the capacitor to 0V?

Solution:



$$Q = CV$$

$$C = 10 \mu\text{F}, V = 50$$

$$Q = 10 \times 10^{-6} \times 50 \\ = 5 \times 10^{-4} \text{ C.}$$

- a) The net charge stored on each plate is 5×10^{-4} coulomb. One plate has positive charge and the other plate has negative charge.

The net charge on both the plates equals zero.

(b) Energy stored on the capacitor $= \frac{1}{2} CV^2$


$$= \frac{1}{2} \times 10 \times 10^{-6} \times 50^2 = 12.5 \text{ mJ.}$$

(c) If discharge rate $\frac{dQ}{dt} = -100 \times 10^{-6} \text{ A}$


To discharge to 0V i.e. $Q_{\text{final}} = C \cdot V = 0$

$$\text{Time taken} = \frac{Q_{\text{final}} - Q_{\text{initial}}}{dQ/dt} = \frac{0 - 5 \times 10^{-4}}{-100 \times 10^{-6}} = 5 \text{ sec.}$$

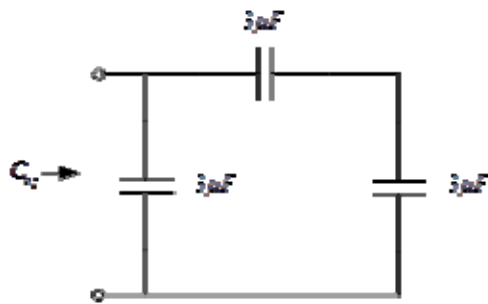2. Find the equivalent capacitance for each of the circuits shown in the figure.





(a)

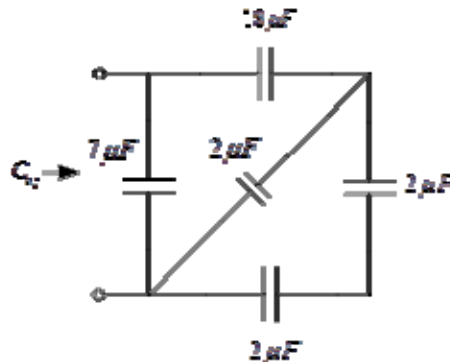

(b)

Solution:
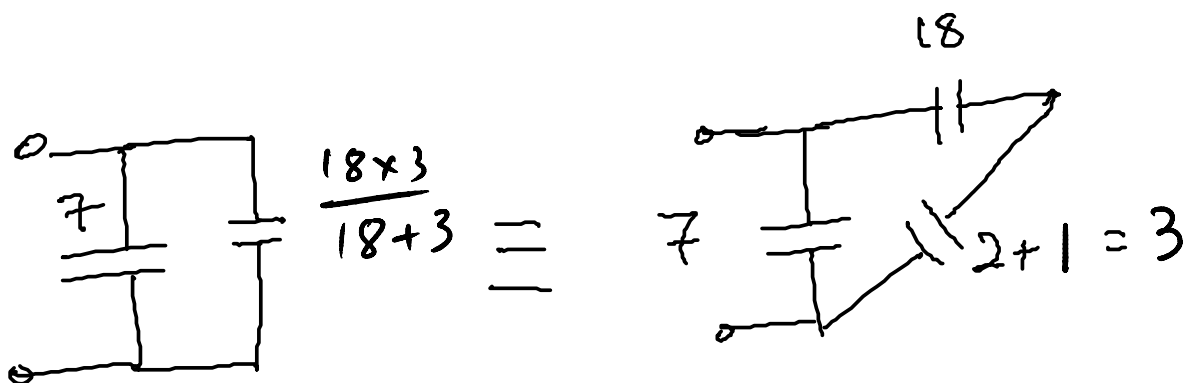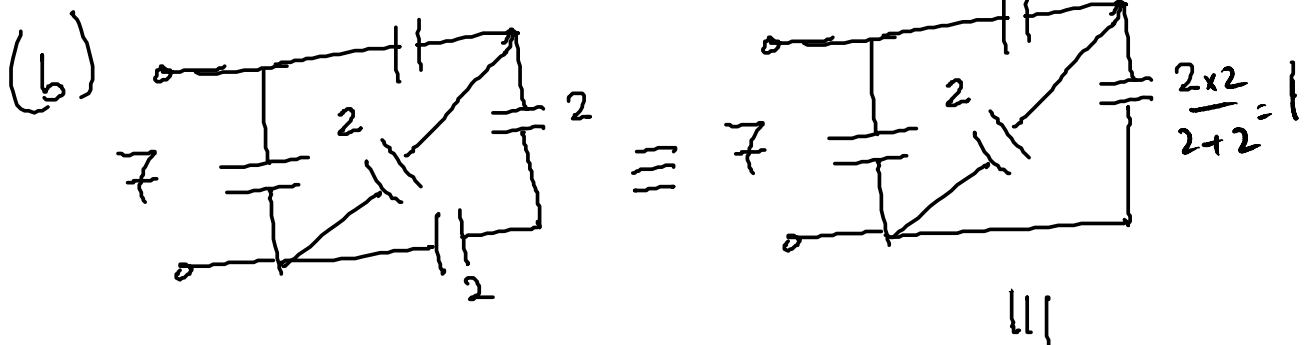
$$(a) \quad C_{eq} = \frac{3 \times 3}{3 + 3} + 3 = \frac{3 \times 3}{3 + 3} = 3 + \frac{3}{2} = 4.5 \mu F$$



$$C_{eq} = 7 + \frac{54}{21} = 9.57 \mu F$$

3. A constant voltage of 30V is applied to a 60 mH inductance. The current in the inductor was zero at $t=0$.
- At what time does the current reach 2A?
 - What is energy stored in the inductor when the current is 2A?

Solution :

For inductor $V = L \frac{di}{dt}$

sf $V = 30V$, $L = 60 \times 10^{-3} H$

Then $\frac{di}{dt} = \frac{V}{L} = \frac{30}{60 \times 10^{-3}} = 0.5 \times 10^3 A/sec$

a) Given $i_L = 0$ at $t = 0$.

Time taken for i_L to reach 2A =

$$= \frac{2}{di/dt} = \frac{2}{0.5 \times 10^3}$$


$$= 4 \text{ ms.}$$

b) Energy stored in the inductor = $\frac{1}{2} L i^2$


$$= \frac{1}{2} \times 60 \times 10^{-3} \times 2^2$$

$$= 120 \times 10^{-3} J = 120 \text{ mJ.}$$

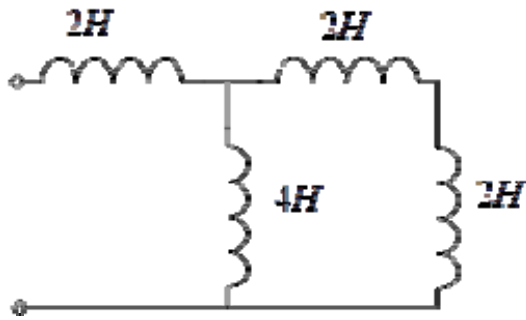
4. Find the equivalent inductance of the circuit below.




Solution :

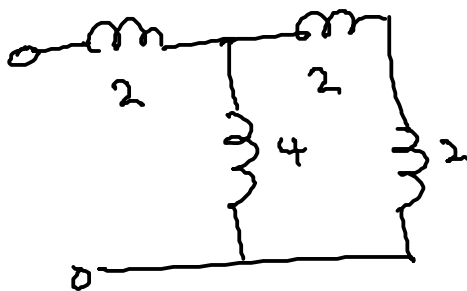


\equiv

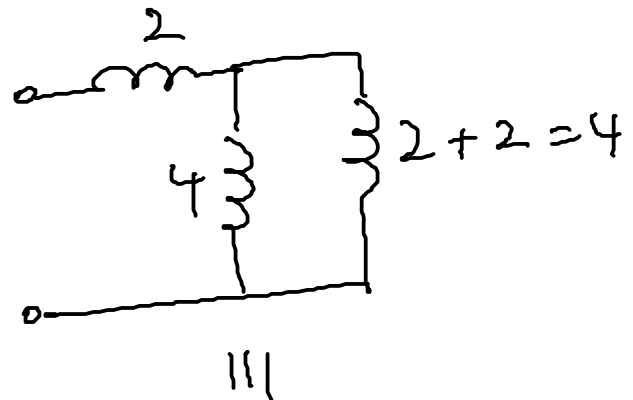

\equiv

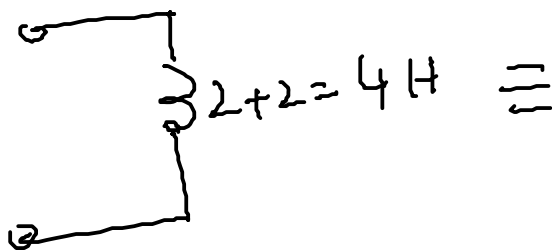


\equiv

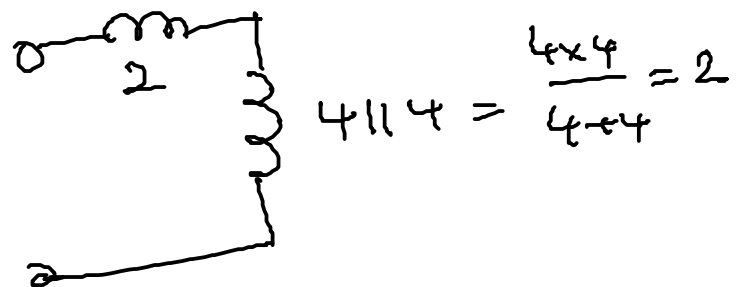

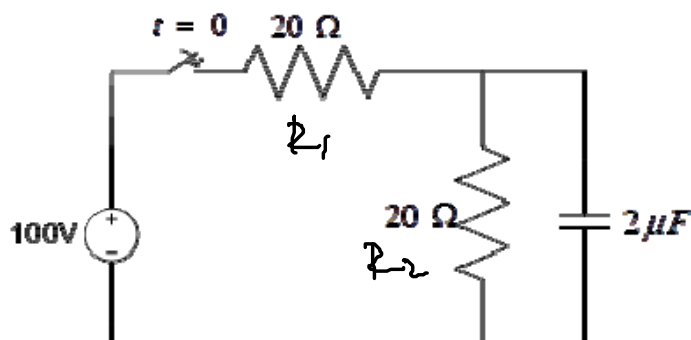5. If the switch in the circuit is closed at $t=0$,
- Determine the current flowing through the resistors and the capacitor when $t=0^+$ (immediately after the switch is closed).
 - What will be the current flow under steady state condition?
 - Determine the voltage across the capacitor under steady state condition.
 - Find an expression for the capacitor voltage as a function of time $t>0$.

Assume that the capacitor is initially uncharged.



Solution

(i) As capacitor voltage can not change instantaneously $V_C(0^-) = V_C(0^+)$

$V_C(0^-)$ can be obtained by the DC analysis before switch was closed.


As can be seen $V_C(0^-) = 0$ before the switch was closed.

$V_C(0^+)$ i.e. capacitor voltage immediately after switch is closed will be zero.

$$\therefore \text{current in } R_2 = \frac{V_C(0^+)}{20} = 0 \text{ A.}$$

$$\therefore \text{current in } R_1 = \frac{100 - V_C(0^+)}{20} = 5 \text{ A.} = i_C(0^+).$$

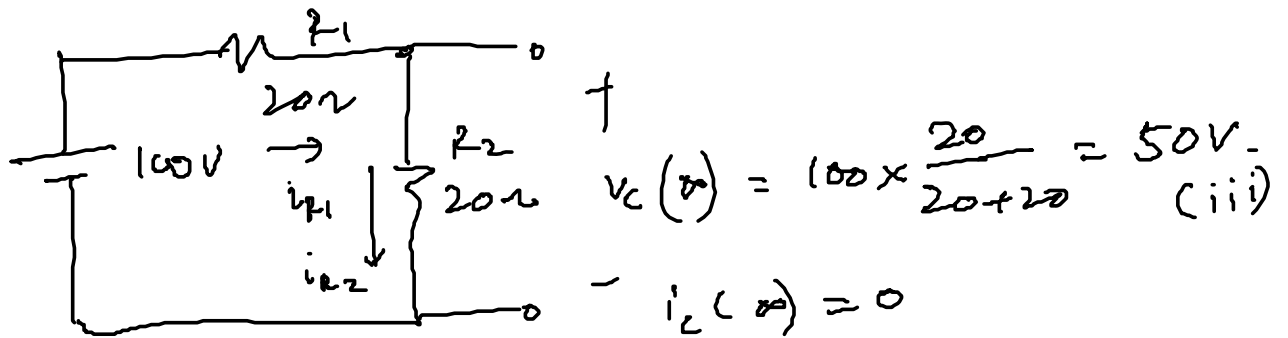(ii) At steady-state, the capacitor will be open circuited.




$$i_{R1} = i_{R2} = \frac{100}{20+20} = 2.5 A$$

(iii) $V_C(\infty) = 100 \times \frac{20}{20+20} = 50V$

(iv) To find the capacitor voltage as a function of time t i.e. $V_C(t)$ at $t=0^+$, we shall put it in the standard form

i.e.

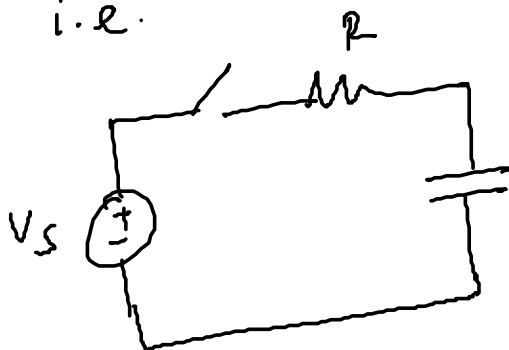

where V_S is the Thevenin's voltage and R is the Thevenin's resistance with C as the Load.

$$V_S = V_T = 50V$$

$$R = R_T = 20 \parallel 20 = 10 \Omega$$

$$\tau = R \times C = 10 \times 2 \times 10^{-6} = 20 \times 10^{-6} \text{ s}.$$


$$v_C(0^+) = v_C(0^-) = 0 \text{ V}$$

$$v_C(\infty) = V_S = 50 \text{ V}$$

$$\begin{aligned} v_C(t) &= v_C(0) \cdot e^{-t/\tau} + v_C(\infty) \cdot (1 - e^{-t/\tau}) \\ &= 50 \left(1 - e^{-t/20 \times 10^{-6}} \right) \text{ V.} \end{aligned}$$


Please note that we use the Thevenin equivalent to put it in the general form.
then we can use the general solution.

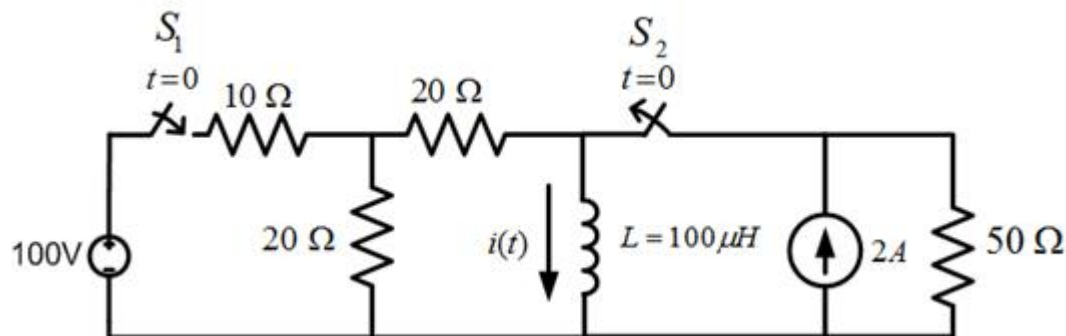6. For the circuit given below, switch S_2 was closed for a long time before $t=0$. At $t=0$, the switch S_1 is closed and S_2 is opened.
- Find the inductor current $i(t)$ at $t=0^+$.
 - Find the time constant for $t \geq 0$.
 - Find an expression for $i(t)$, and sketch the function.
 - Find $i(t)$ for each of the following values of t zero, the time constant, twice the time constant, five times the time constant and ten times the time constant.



Solution

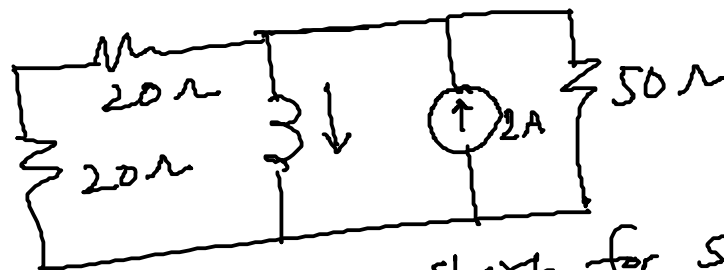
- ① To find inductor current $t = 0^+$.
 $i_L(0^+) = i_L(0^-)$ as inductor current
 can not change instantaneously.
 Before $t=0$, with S_1 open and S_2 closed,
 the circuit is:




As inductor acts as a short for steady state,
 the inductor current = 2A.

$$i_L(0^+) = i_L(0^-) = 2 \text{ A}.$$

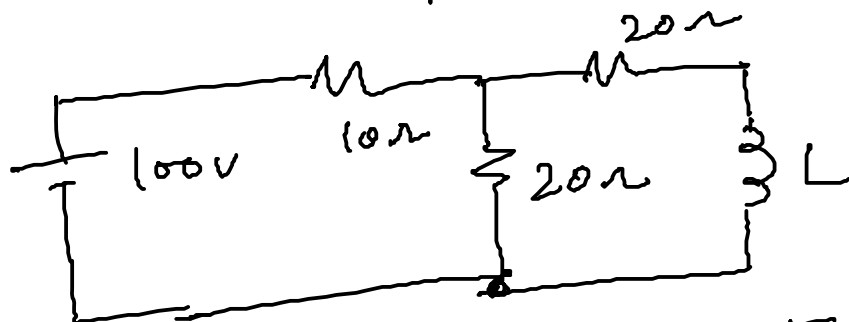After $t=0$, when S_1 is closed and S_2 is opened, the circuit becomes:



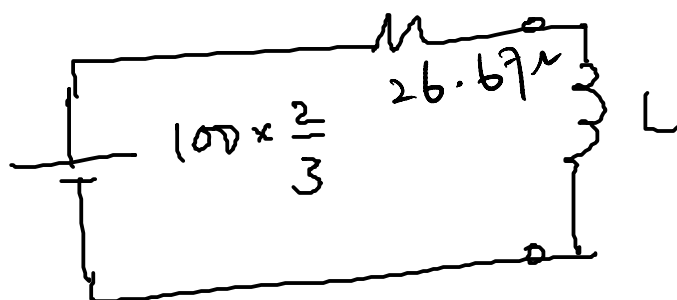Thevenin equivalent of the circuit will be



which is in the standard form.

$$\tau = \frac{L}{R} = \frac{100 \times 10^{-6}}{26.67} = 3.75 \mu\text{s}.$$

$$i_L(0^+) = 2 \text{ A}$$

$$i_L(\infty) = \frac{100 \times 0.5}{20} = 2.5 \text{ A}$$

as L acts as a short circuit in steady-state

$$i_L(t) = i_L(0) \cdot e^{-t/\tau} + i_L(\infty) \cdot (1 - e^{-t/\tau})$$

$$= 2 e^{-t/3.75 \times 10^{-6}} + 2.5 (1 - e^{-t/3.75 \times 10^{-6}}) \text{ A}.$$

$$(d) \text{ At } t = \tau, \quad i_L = 2 \times e^{-1} + 2.5 (1 - e^{-1}) \\ = 2.316 \text{ A}$$

$$\text{At } t = 2\tau, \quad i_L = 2 \times e^{-2} + 2.5 (1 - e^{-2}) \\ = 2.432 \text{ A}$$

$$\text{At } t = 5\tau, \quad i_L = 2 \times e^{-5} + 2.5 (1 - e^{-5}) \\ = 2.497 \text{ A}$$

$$\text{At } t = 10\tau, \quad i_L = 2 \times e^{-10} + \text{Change } 3.33 \text{ to } 2.5 (1 - e^{-10}) \\ = 2.4998 \text{ A}$$

