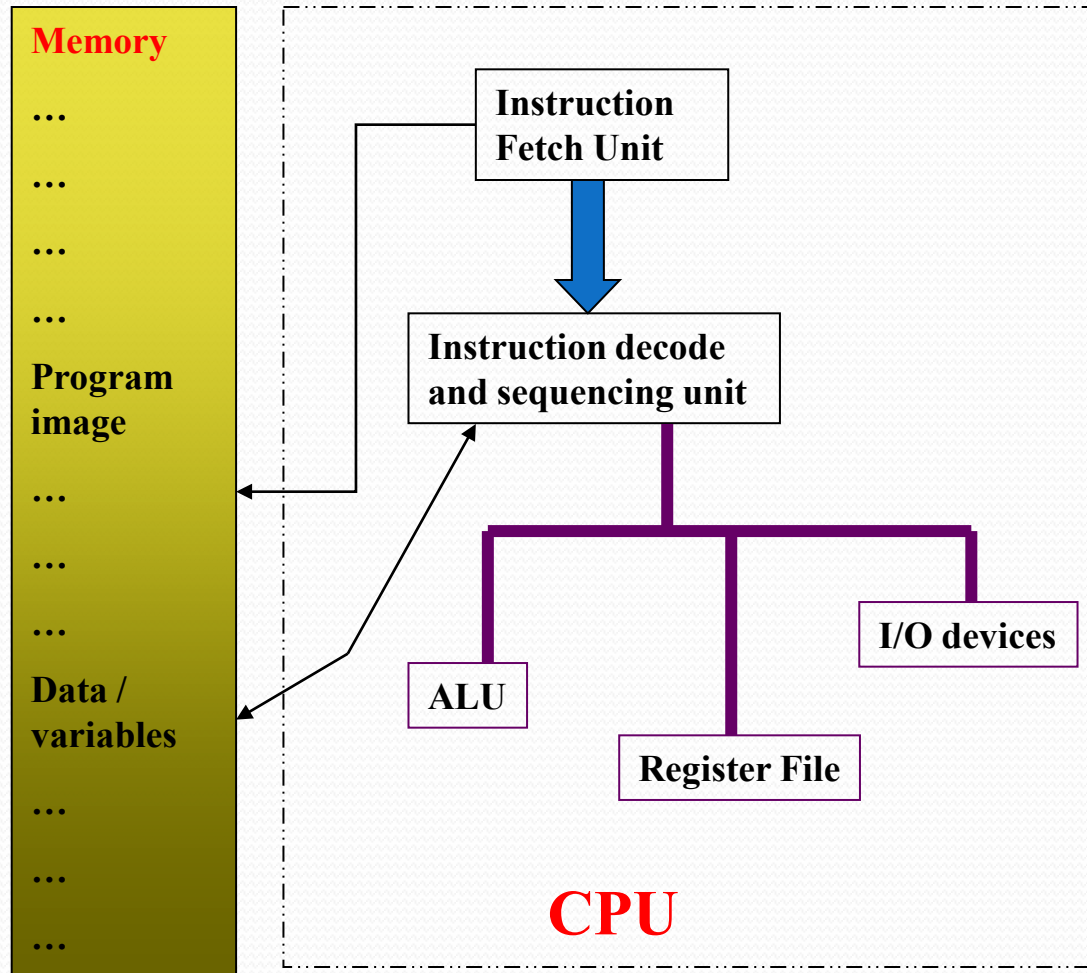




Design of a Microprocessor

The uP3207 processor

Operation of a Simple Microprocessor



- Program to be executed is stored in memory
- Instruction Fetch Unit of CPU will fetch an instruction at a time from memory
- Instruction is sent to the decoding and sequencing unit (DSU)
- The DSC is a state machine that creates the sequence of actions to execute the instruction
 - The sequence acts on objects such the ALU, registers and I/O devices
- Once done control is reverted to the Instruction Fetch Unit to fetch the next instruction.



The uP3207 processor


Our First Central Processing Unit

- What to design?
 - Requirement analysis on intended application
 - Not to be addressed in this course. Assume this is done.
- Features
 - 16 bit data width processor
 - 4K words addressable memory
 - Stack for temporary variable storage
 - Single word instructions
 - Single operands architecture
 - Support direct and indirect addressing
 - Support multiple interrupts from input and output devices
 - Low cost
 - Complete functionalities

uP3207 Microprocessor

Memory interface
4K words of 16 bit
memory, with separate
read/write control

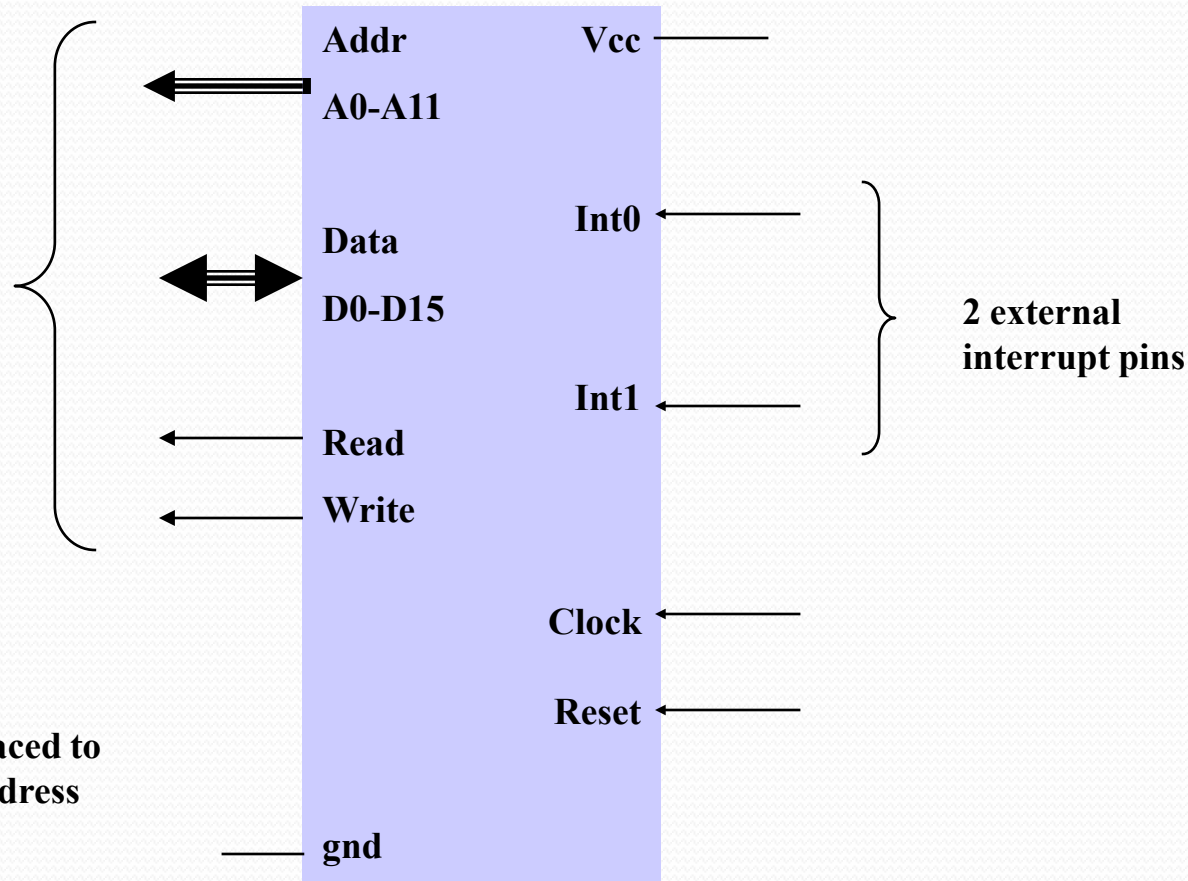
I/O devices will be interfaced to
the uP on the memory address
space.



ISA: Registers and memory overview


- PC: program counter
 - Holds address of the next instruction
- SP: stack pointer
- BP: base pointer
- AC: accumulator
 - main processor register
- XR: operand register
 - For holding the operand of arithmetic/logic operations
- Flags
 - S=AC negative
 - Z=AC zero
 - C=carry flag set
 - Y=DR=0

Programmer's View

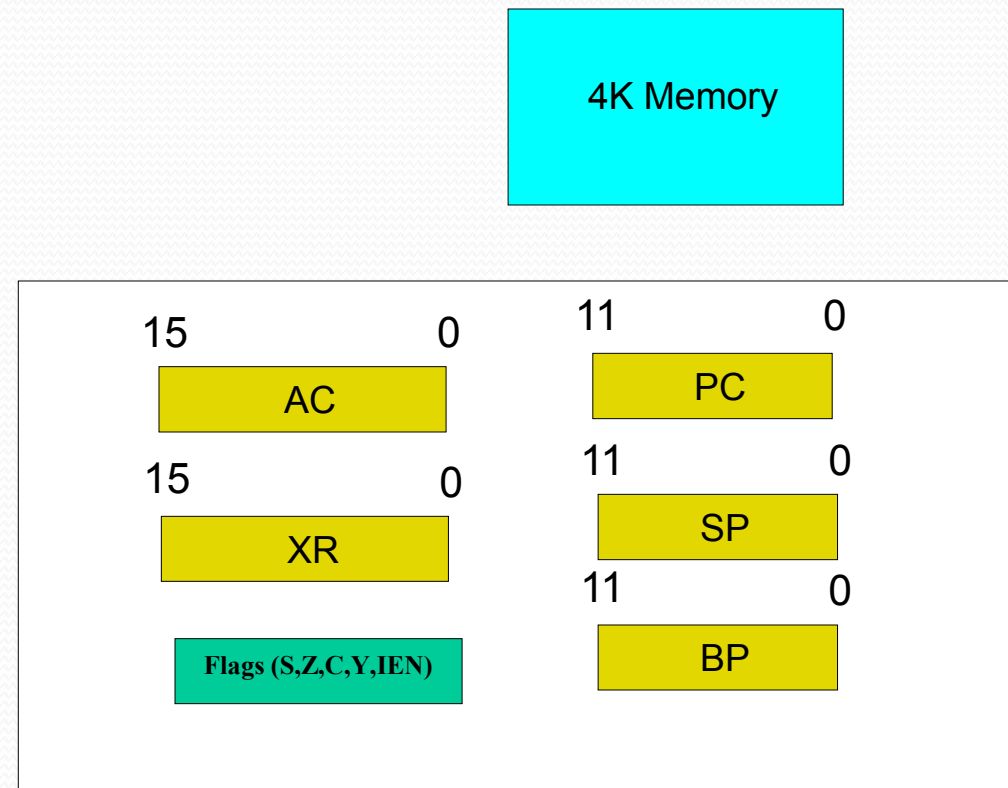


ISA: instructions

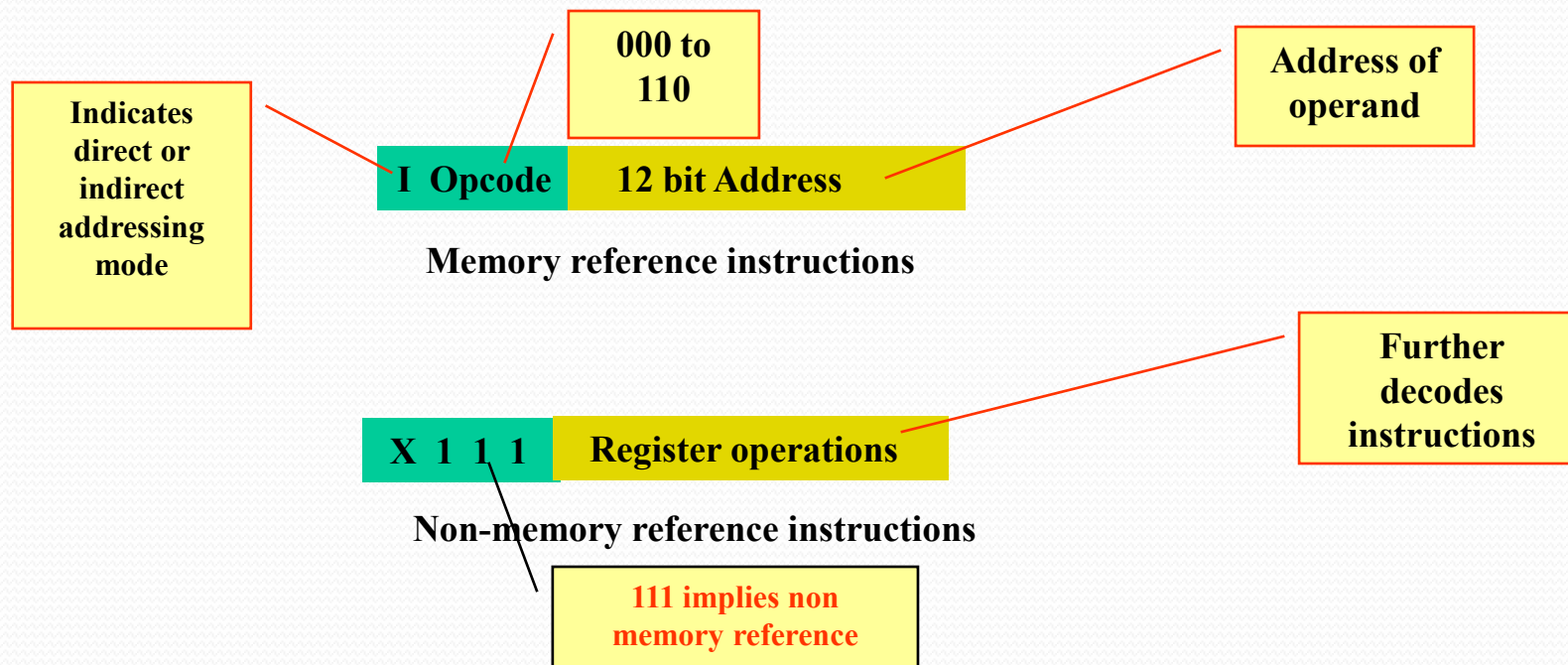- Memory reference group
 - Bits 12-14 not all ones => memory access and Bits 0-11 are addresses
 - I=1 implies indirect addressing
 - I=0 implies direct addressing
 - total of 7 memory instructions (from 000 to 110)
- Non-memory reference group
 - Bit 12-14 are ones, ops are internal => no need for address. Therefore the Bits 0-11 are used to indicate other instructions




Addressing modes

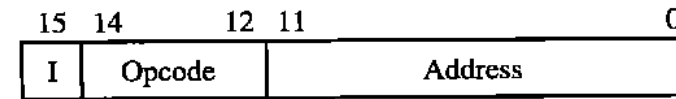
- direct
 - bits 0 - 11 is the address of the operand
- indirect
 - bits 0 - 11 is the address in which we obtain the address of the operand
 - bit 15 can be used to indicate the addressing mode
 - BP indirect
- Immediate (not directly supported)
 - data is placed at a designated location in memory. It can then be loaded using direct or indirect addressing method.



(a) Instruction format

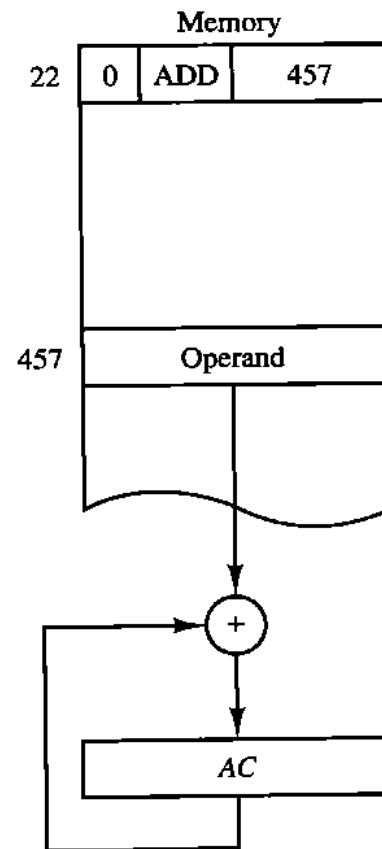

(b) Direct address

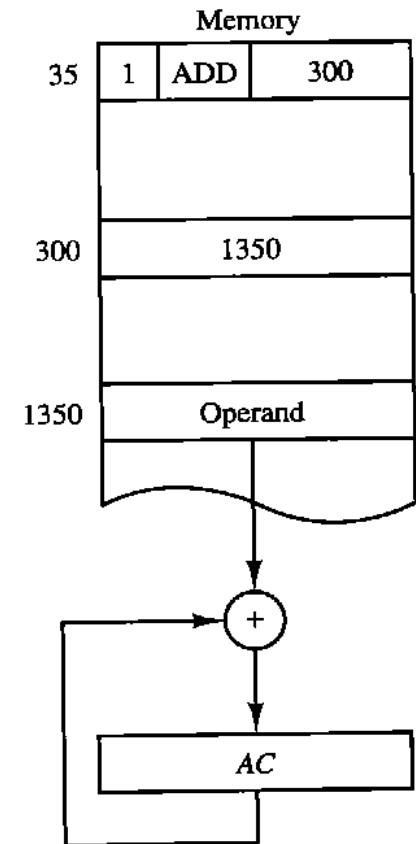

(c) Indirect address

Definition of Instructions:

Memory reference instructions

	Hexadecimal code		
Symbol	I = 0	I = 1	Description
LDB	0xxx	8xxx	Load memory word to BP
LDX	1xxx	9xxx	Load memory word to XR
LDA	2xxx	Axxx	Load memory word to AC
STA	3xxx	Bxxx	Store content of AC in memory
BUN	4xxx	Cxxx	Branch unconditionally
CALL	5xxx	Dxxx	Push PC onto stack and branch unconditionally
DSZ	6xxx	Exxx	Decrement and skip if zero

Register reference instructions

arithmetic

logic

Shift

Bit manipulation

Subroutine
/stack

Conditional
branch

INC	7010	Increment AC
DEC	7011	Decrement AC
ADD	7012	AC=AC+XR
ADC	7013	AC=AC+XR+C
SUB	7014	AC=AC-XR
SBB	7015	AC=AC-XR+1
AND	7016	AC=AC and XR
OR	7017	AC=AC or XR
XOR	7020	AC=AC xor XR
SHR	7021	Shift AC right
SHL	7022	Shift AC left
CLAC	7023	Clear AC
CMAC	7024	Complement AC
CLC	7025	Clear C
CMC	7026	Complement C
STC	7027	Set C
AC2SP	7040	Move content of AC to SP
SP2BP	7041	Move content of SP to BP
LDABP	7042	Load AC indirect through BP
IRET	7043	Restore address from stack onto PC and ION
RET	7044	Restore address from stack onto PC
POP	7045	Pop word from the stack onto AC
PUSH	7046	Push AC onto the stack
SZAC	7047	Skip next instruction if AC zero
SNAC	7080	Skip next instruction if AC negative
SPAC	7081	Skip next instruction if AC positive
SSC	7082	Skip next instruction if C is set
SCC	7083	Skip next instruction if C is clear
ION	7084	Interrupt on
IOF	7085	Interrupt off

Instruction set completeness

- Arithmetic
 - add, adc, sub, sbb, inc, dec
 - Instructions like multiple can be synthesized in software
- Logical
 - and, or, not, xor
 - AND and NOT gives NAND => all logic operations can be performed
- Shift instructions
 - shr, shl
- Instructions for moving information to from memory and processor registers
 - lda, sta
- Program control instructions together with instructions that check status condition.
 - bun, call, dsz. 4 skip instructions
- Input and output instructions.
 - I/O devices are memory mapped



Design of the CPU

The bus


The state generator

Actions in each state for each instruction

Common bus concept for transfer of memory content

- Using digital multiplexer


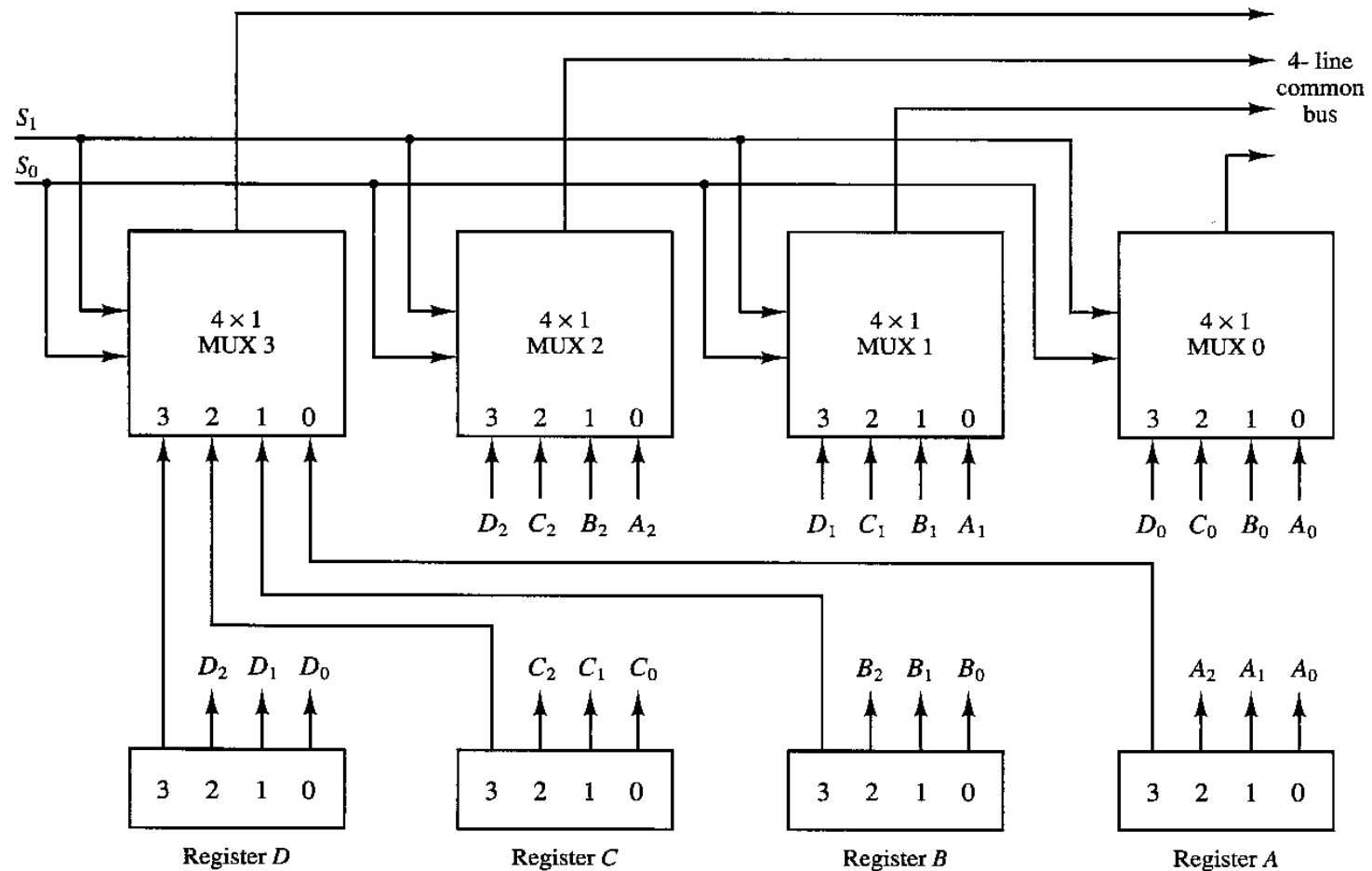
- intuitive but not normally used in uP design
- instead we have tri-state buffer
 - beside 0 and 1, there is a third high impedance state
- allows many devices to be electrically tied together as long as only one device asserts a 0 or 1 at any one time





Construction of a bus system: another perspective

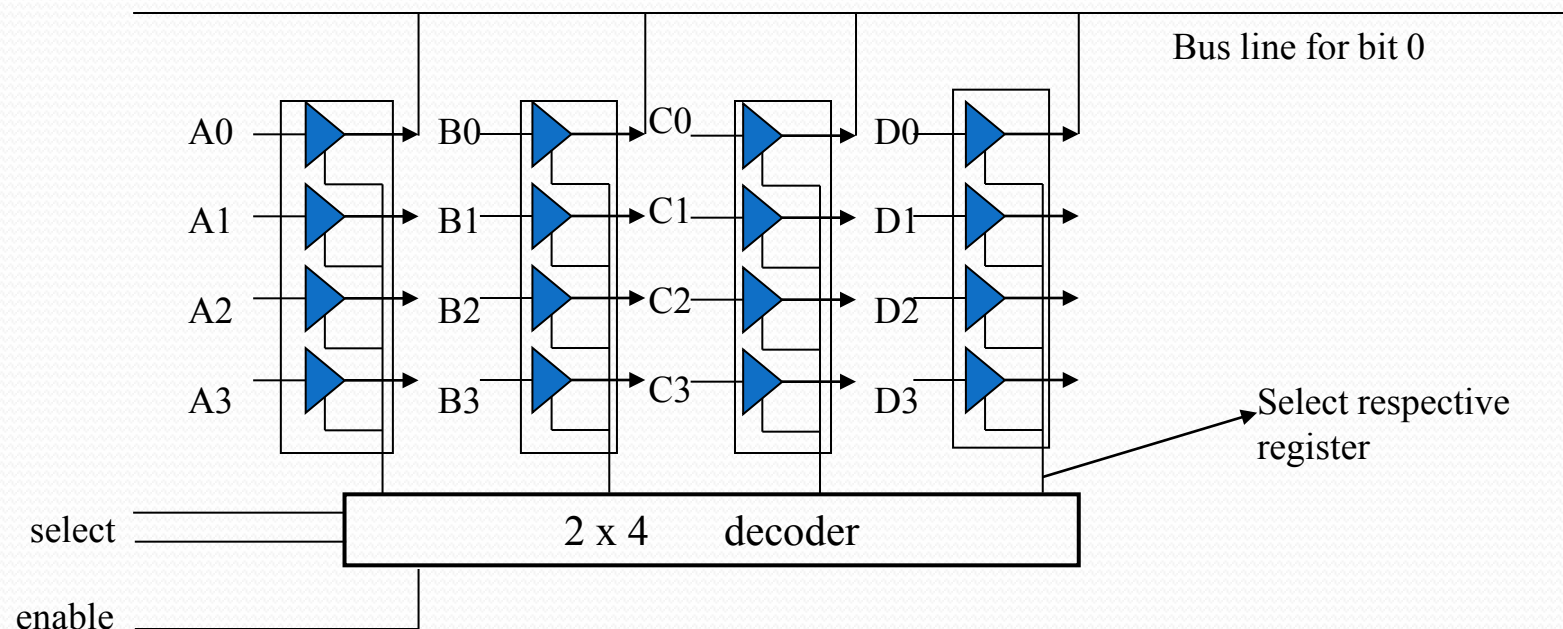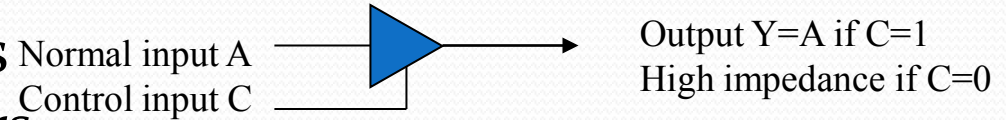- Bus line with three states buffers
 - outputs requires tri-states buffers
 - inputs connected directly to inputs of registers
 - enable to load values
 - check fanout requirement




ISA: Registers and memory overview

- PC: program counter
 - Holds address of the next instruction
- AR: address register
 - holds address for selecting memory
- SP: stack pointer
- BP: base pointer
- IR: instruction register
 - holds the instruction code for decoding
- TR: temporary register
- DR: data register
 - holds memory operand
- AC: accumulator
 - main processor register
- XR: operand register
 - For holding the operand of arithmetic/logic operations
- Flags
 - S=AC negative
 - Z=AC zero
 - C=carry flag set
 - Y=DR=0


What are the objects in the system?

What are available to the programmer?

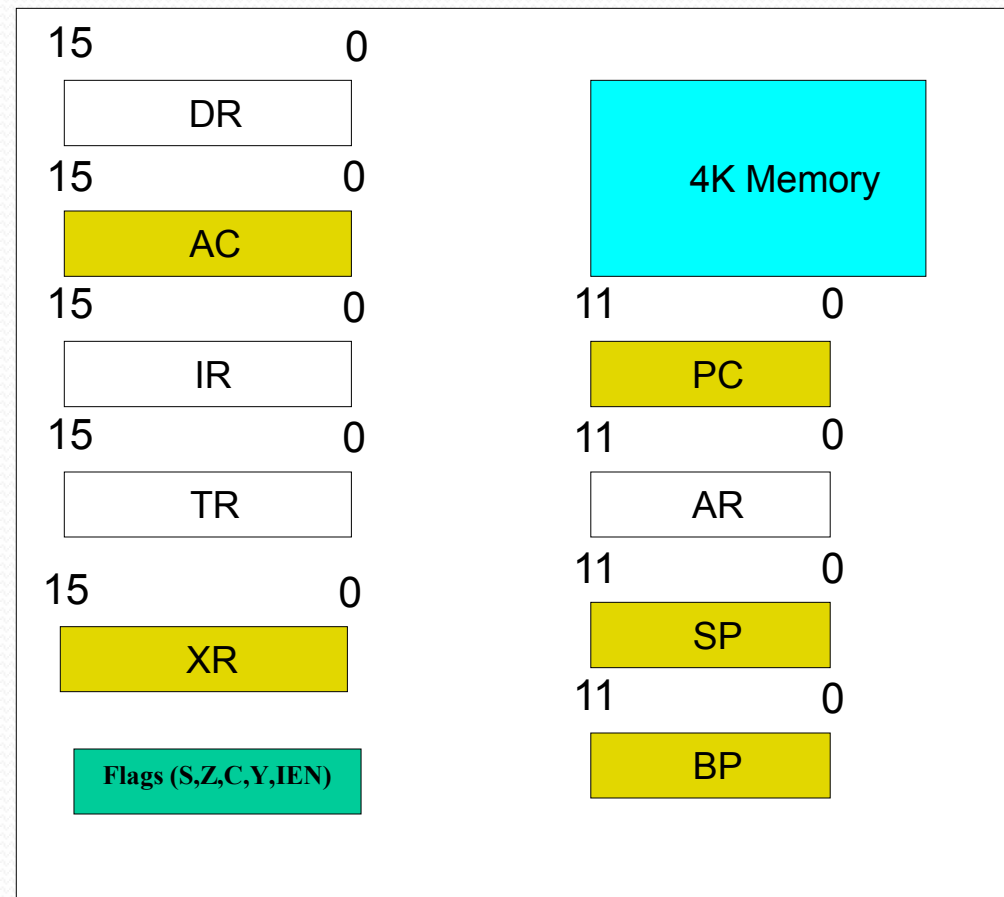


Common bus system of uP4202

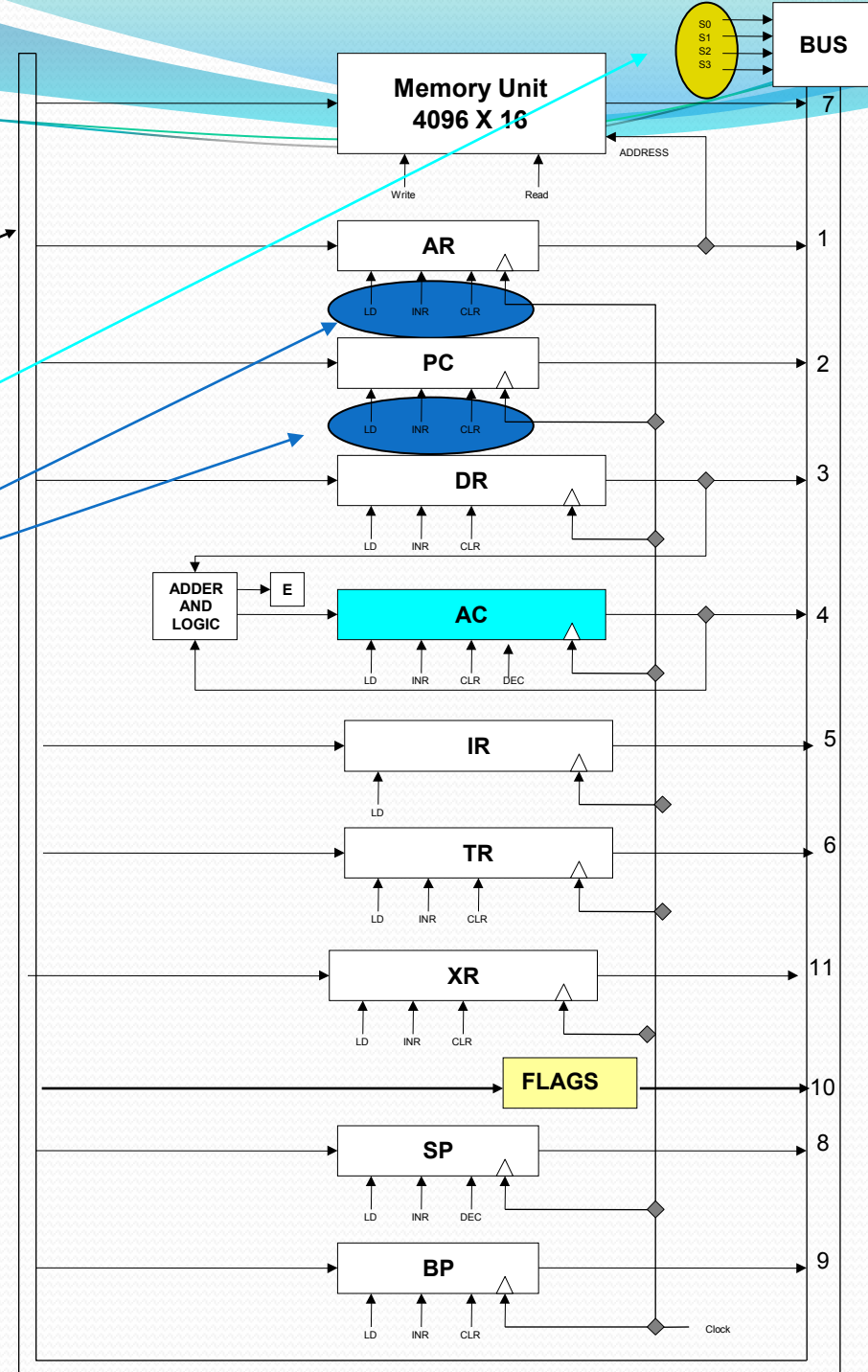- 11 items
 - internal bus to control the movement of data among them
 - 4 bit control lines to determine who drives bus
 - LD line to load specific register
 - the specific word location in the 4K memory is selected by AR
- Control
 - We need to generate So-S₃, LD, INR, CLR to control the movement of data around at the appropriate time.




Timing and control

 
- Creation of sequencing control in the decoding of instructions



State generator

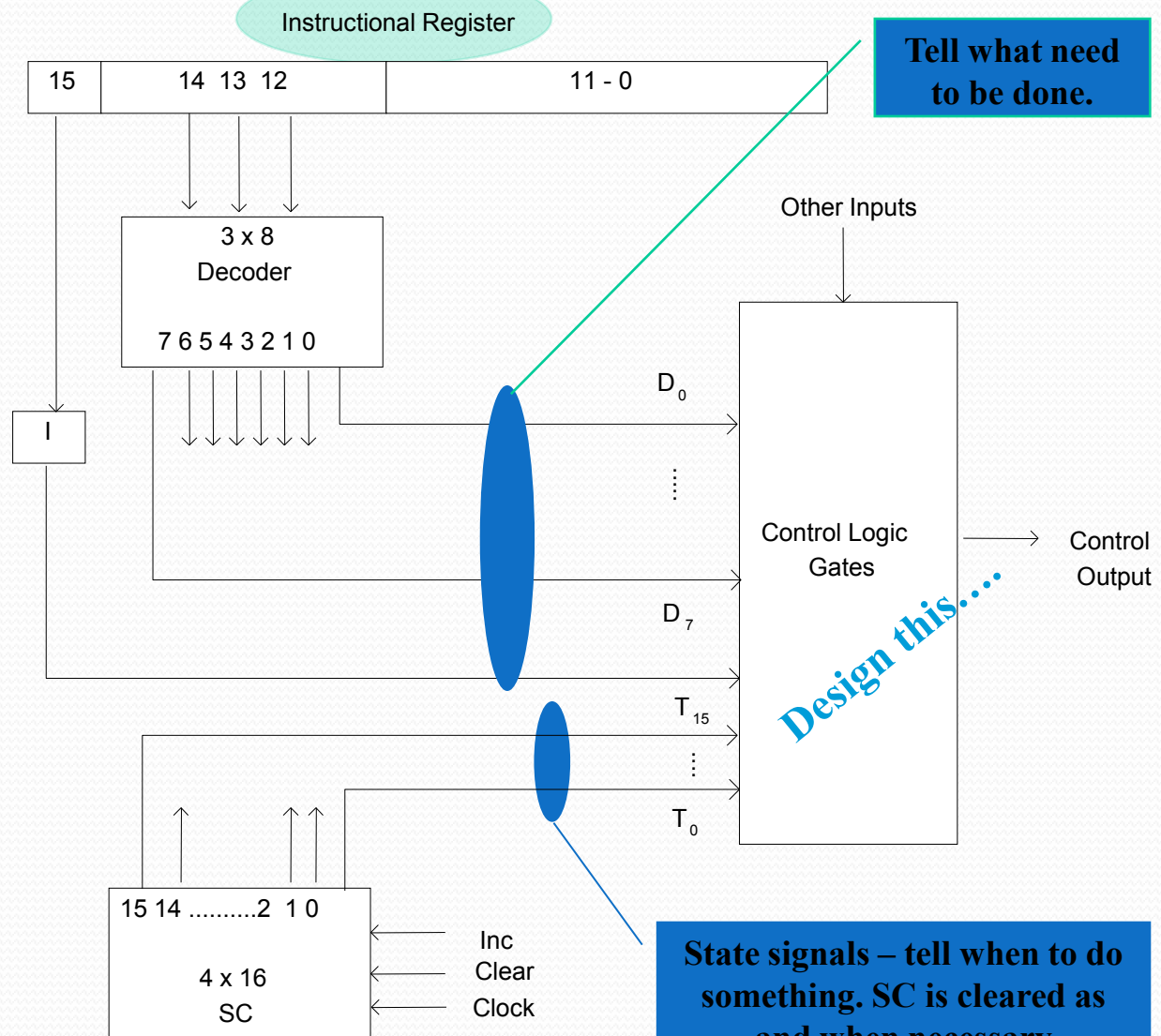

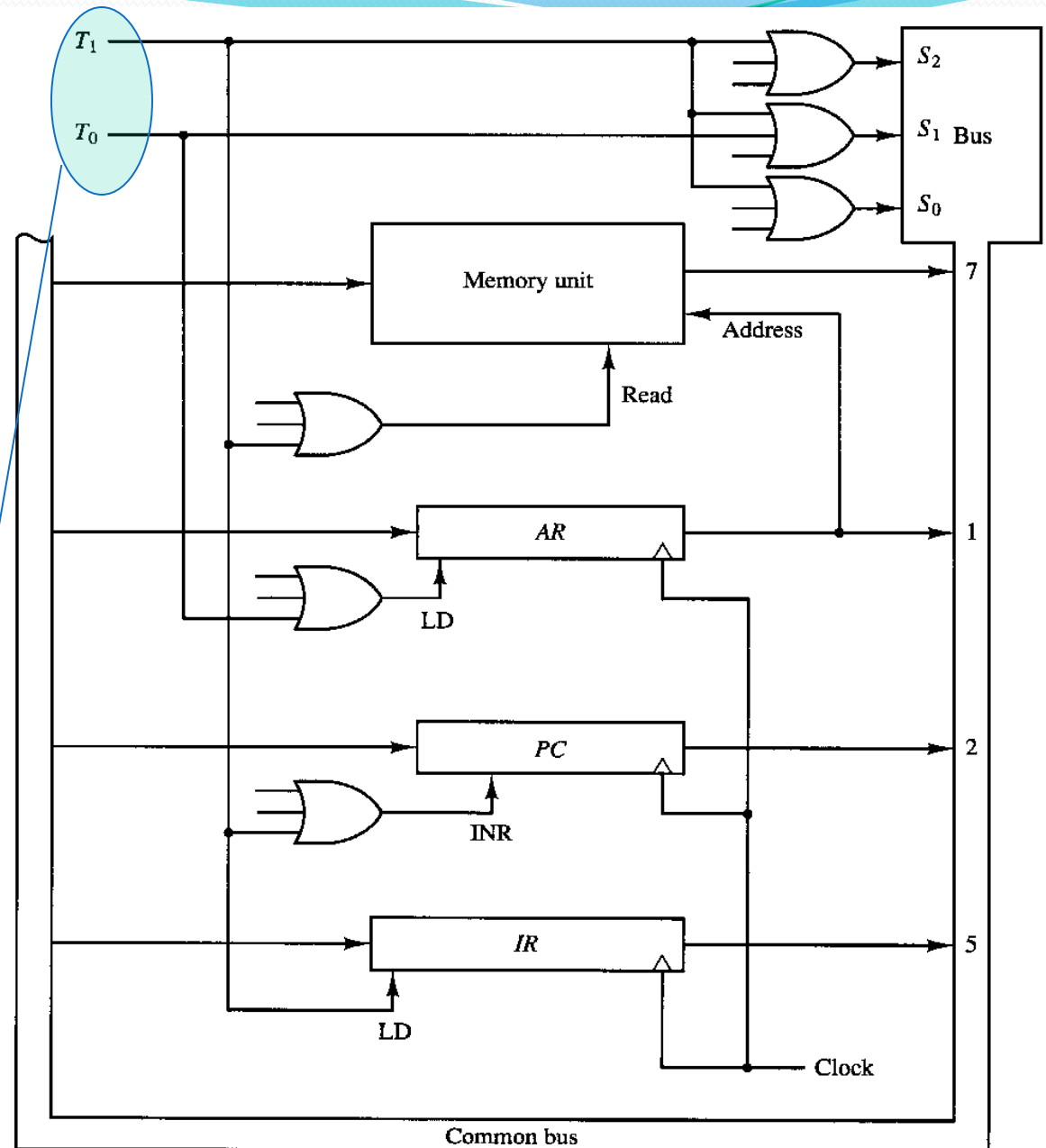
- An instruction always start with T0, then T1,**
During states T0 and T1,
instruction is fetched.
How to fetch an instruction?




What next?

During State T2:

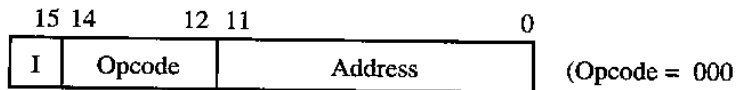
- **DECODE.** Set
 - $D_7 \leftarrow 1$ if opcode = 111
 - $I \leftarrow IR(15)$
 - $AR \leftarrow IR(0-11)$




(a) Memory – reference instruction

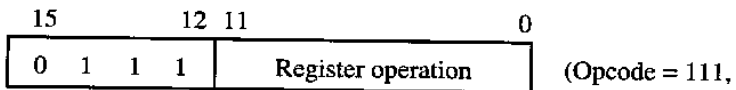

(b) Register – reference instruction

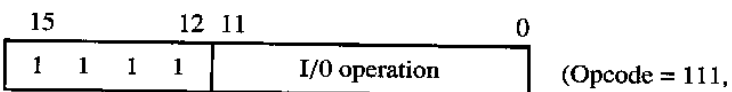

(c) Input – output instruction

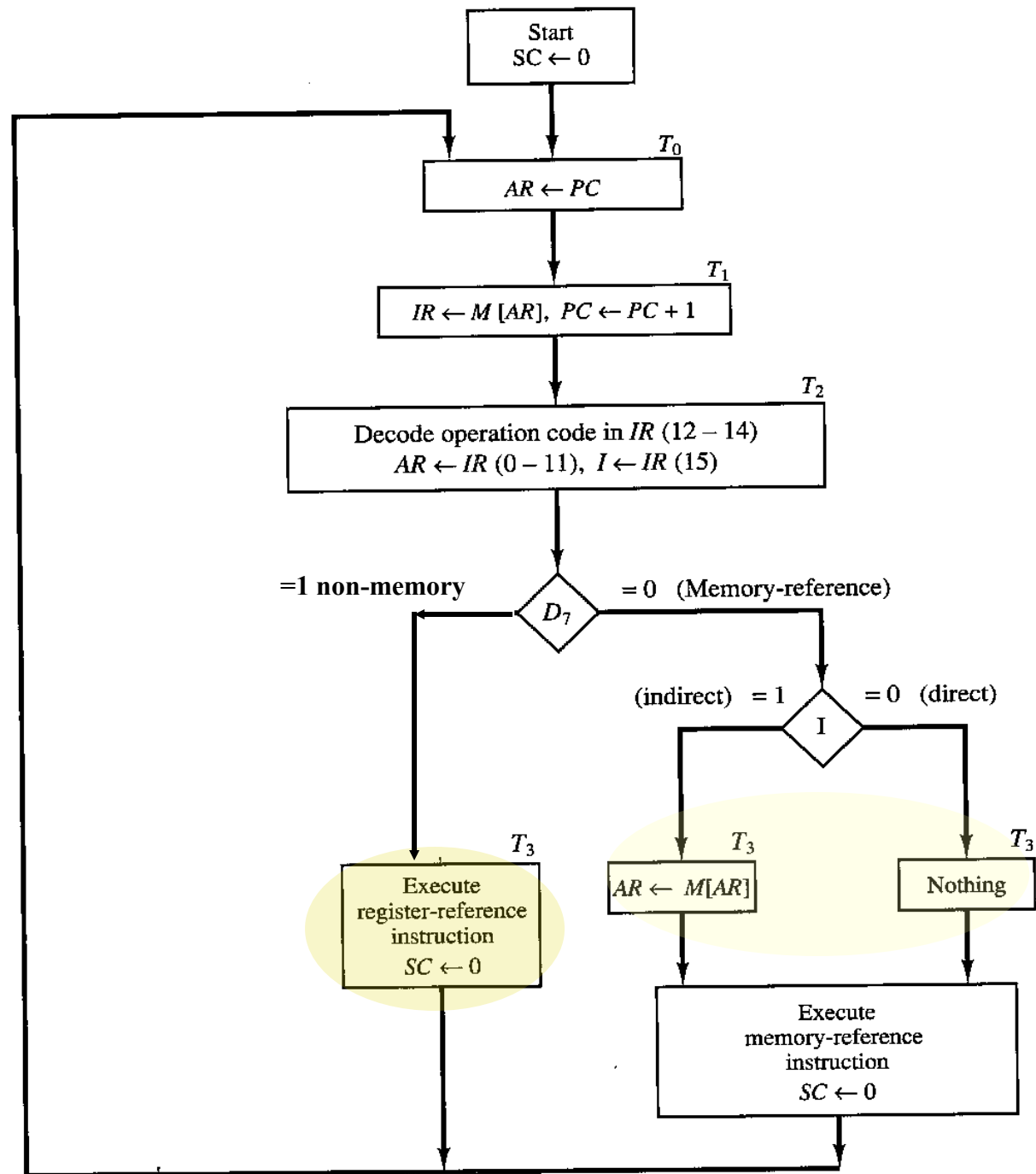

Memory reference instructions

- Do to D6 determine each one of the below instruction
- from flowchart effective address placed during T₂ or T₃ depending on whether direct or indirect addressing

LDB	0XXX 8XXX	D ₀ T ₄	BP ← M[AR], SC ← 0	Bus transfer
LDX	1XXX 9XXX	D ₁ T ₄	XR ← M[AR], SC ← 0	Bus transfer
LDA	2XXX AXXX	D ₂ T ₄ D ₂ T ₅	DR ← M[AR], AC ← 0 AC ← AC + DR, SC ← 0	Note that input to AC is connected to ALU, not bus.
STA	3XXX BXXX	D ₃ T ₄	M[AR] ← AC, SC ← 0	Bus transfer
BUN	4XXX CXXX	D ₄ T ₄	PC ← AR, SC ← 0	Branch address already in AR by T ₃
CALL	5XXX DXXX	D ₅ T ₄ D ₅ T ₅ D ₅ T ₆ D ₅ T ₇	SP ← SP - 1, TR ← AR AR ← SP M[AR] ← PC PC ← TR, SC ← 0	Store in TR the branch address that is in AR. Store current PC on stack. Transfer TR to PC to branch.
DSZ	6XXX EXXX	D ₆ T ₄ D ₆ T ₅ D ₆ T ₆ Y D ₆ T ₆ Y'	DR ← M[AR] DR ← DR - 1 M[AR] ← DR, PC ← PC + 1, SC ← 0 M[AR] ← DR, SC ← 0	Read in data to DR. Check for zero to branch

Register reference instruction in T3

Use a 3-8 decoder

			$D_7I'T_3=r$ $IR(i) = B_i \text{ (i=0 TO 11)}$ $K_0=B_2'B_1'B_0', K_1=B_2'B_1'B_0, \dots, K_7=B_2B_1B_0$	
		r	$SC \leftarrow 0$	
INC	7010	rB_4K_0	$AC \leftarrow AC + 1, SC \leftarrow 0$	Increment AC
DEC	7011	rB_4K_1	$AC \leftarrow AC - 1, SC \leftarrow 0$	Decrement AC
ADD	7012	$D_7I'T_3B_4K_2$ $D_7I'T_4B_4K_2$	$DR \leftarrow XR$ $AC \leftarrow AC + DR, SC \leftarrow 0$	$AC = AC + XR$
ADC	7013	$D_7I'T_3B_4K_3$ $D_7I'T_4B_4K_3$	$DR \leftarrow XR$ $AC \leftarrow AC + DR + C, SC \leftarrow 0$	$AC = AC + XR + C$
SUB	7014	$D_7I'T_3B_4K_4$ $D_7I'T_4B_4K_4$	$DR \leftarrow XR$ $AC \leftarrow AC - DR, SC \leftarrow 0$	$AC = AC - XR$
SBB	7015	$D_7I'T_3B_4K_5$ $D_7I'T_4B_4K_5$	$DR \leftarrow XR$ $AC \leftarrow AC - DR + C, SC \leftarrow 0$	$AC = AC - XR + 1$
AND	7016	$D_7I'T_3B_4K_6$ $D_7I'T_4B_4K_6$	$DR \leftarrow XR$ $AC \leftarrow AC \wedge DR, SC \leftarrow 0$	$AC = AC \text{ and } XR$
OR	7017	$D_7I'T_3B_4K_7$ $D_7I'T_4B_4K_7$	$DR \leftarrow XR$ $AC \leftarrow AC \vee DR, SC \leftarrow 0$	$AC = AC \text{ or } XR$
XOR	7020	$D_7I'T_3B_5K_0$ $D_7I'T_4B_5K_0$	$DR \leftarrow XR$ $AC \leftarrow AC \oplus DR, SC \leftarrow 0$	$AC = AC \text{ xor } XR$
SHR	7021	rB_5K_1	$AC \leftarrow \text{shr } AC, AC(15) \leftarrow E, E \leftarrow AC(0), SC \leftarrow 0$	Shift AC right
SHL	7022	rB_5K_2	$AC \leftarrow \text{shl } AC, AC(0) \leftarrow E, E \leftarrow AC(15), SC \leftarrow 0$	Shift AC left

Register reference instruction in T3


CLAC	7023	rB_5K_3	$AC \leftarrow 0, SC \leftarrow 0$	Clear AC
CMAC	7024	rB_5K_4	$AC \leftarrow AC', SC \leftarrow 0$	Complement AC
CLC	7025	rB_5K_5	$C \leftarrow 0, SC \leftarrow 0$	Clear C
CMC	7026	rB_8K_6	$C \leftarrow C', SC \leftarrow 0$	Complement C
STC	7027	rB_5K_7	$C \leftarrow 1, SC \leftarrow 0$	Set C
AC2SP	7040	rB_6K_0	$SP \leftarrow AC, SC \leftarrow 0$	Move content of AC to SP
SP2BP	7041	rB_6K_1	$BP \leftarrow SP, SC \leftarrow 0$	Move content of SP to BP
LDABP	7042	$D_7I' T_3 B_6K_2$ $D_7I' T_4 B_6K_2$ $D_7I' T_5 B_6K_2$	$AR \leftarrow BP, AC \leftarrow 0$ $DR \leftarrow M[AR]$ $AC \leftarrow AC + DR, SC \leftarrow 0$	Load AC indirect through BP

Register reference instruction in T3

IRET	7043	$D_7I' T_3 B_6K_3$ $D_7I' T_4 B_6K_3$ $D_7I' T_5 B_6K_3$ $D_7I' T_6 B_6K_3$	$AR \leftarrow SP$ $PC \leftarrow M[AR], SP \leftarrow SP + 1$ $AR \leftarrow SP$ $FLAGS \leftarrow M[AR], SP \leftarrow SP + 1, IEN \leftarrow 1, SC \leftarrow 0$	Restore address from stack onto PC and ION
RET	7044	$D_7I' T_3 B_6K_4$ $D_7I' T_4 B_6K_4$	$AR \leftarrow SP$ $PC \leftarrow M[AR], SP \leftarrow SP + 1, SC \leftarrow 0$	Restore address from stack onto PC
POP	7045	$D_7I' T_3 B_6K_5$ $D_7I' T_4 B_6K_5$	$AR \leftarrow SP, AC \leftarrow 0$ $DR \leftarrow M[AR], SP \leftarrow SP + 1$ $AC \leftarrow AC + DR, SC \leftarrow 0$	Pop word from the stack onto AC
PUSH	7046	$D_7I' T_3 B_6K_6$ $D_7I' T_4 B_6K_6$ $D_7I' T_5 B_6K_6$	$SP \leftarrow SP - 1$ $AR \leftarrow SP$ $M[AR] \leftarrow AC, SC \leftarrow 0$	Push AC onto the stack
SZAC	7047	rB_6K_7Z rB_6K_7Z'	$PC \leftarrow PC + 1, SC \leftarrow 0$ $SC \leftarrow 0$	Skip next instruction if AC zero
SNAC	7080	rB_7K_0S rB_7K_0S'	$PC \leftarrow PC + 1, SC \leftarrow 0$ $SC \leftarrow 0$	Skip next instruction if AC negative
SPAC	7081	$rB_7K_1S'Z'$ $rB_7K_1(S'Z')'$	$PC \leftarrow PC + 1, SC \leftarrow 0$ $SC \leftarrow 0$	Skip next instruction if AC positive
SSC	7082	rB_7K_2C rB_7K_2C'	$PC \leftarrow PC + 1, SC \leftarrow 0$ $SC \leftarrow 0$	Skip next instruction if C is set
SCC	7083	rB_7K_3C' rB_7K_3C	$PC \leftarrow PC + 1, SC \leftarrow 0$ $SC \leftarrow 0$	Skip next instruction if C is clear
ION	7084	rB_7K_4	$IEN \leftarrow 1, SC \leftarrow 0$	Interrupt on
IOF	7085	rB_7K_5	$IEN \leftarrow 0, SC \leftarrow 0$	Interrupt off

Interrupts

- R is an interrupt indicator flag
- request for I/O will interrupt uP
 - $IntI=1$ or $IntO=1$
 - Both signals are externally generated.
 - Signals tie to two D f/fs.
 - At each clock cycle, status is updated.
- During instruction execution, flags will be check and R set or clear accordingly
- R is check before every instruction to determine if uP should go into interrupt cycle or not
- Interrupt vector address at location 1

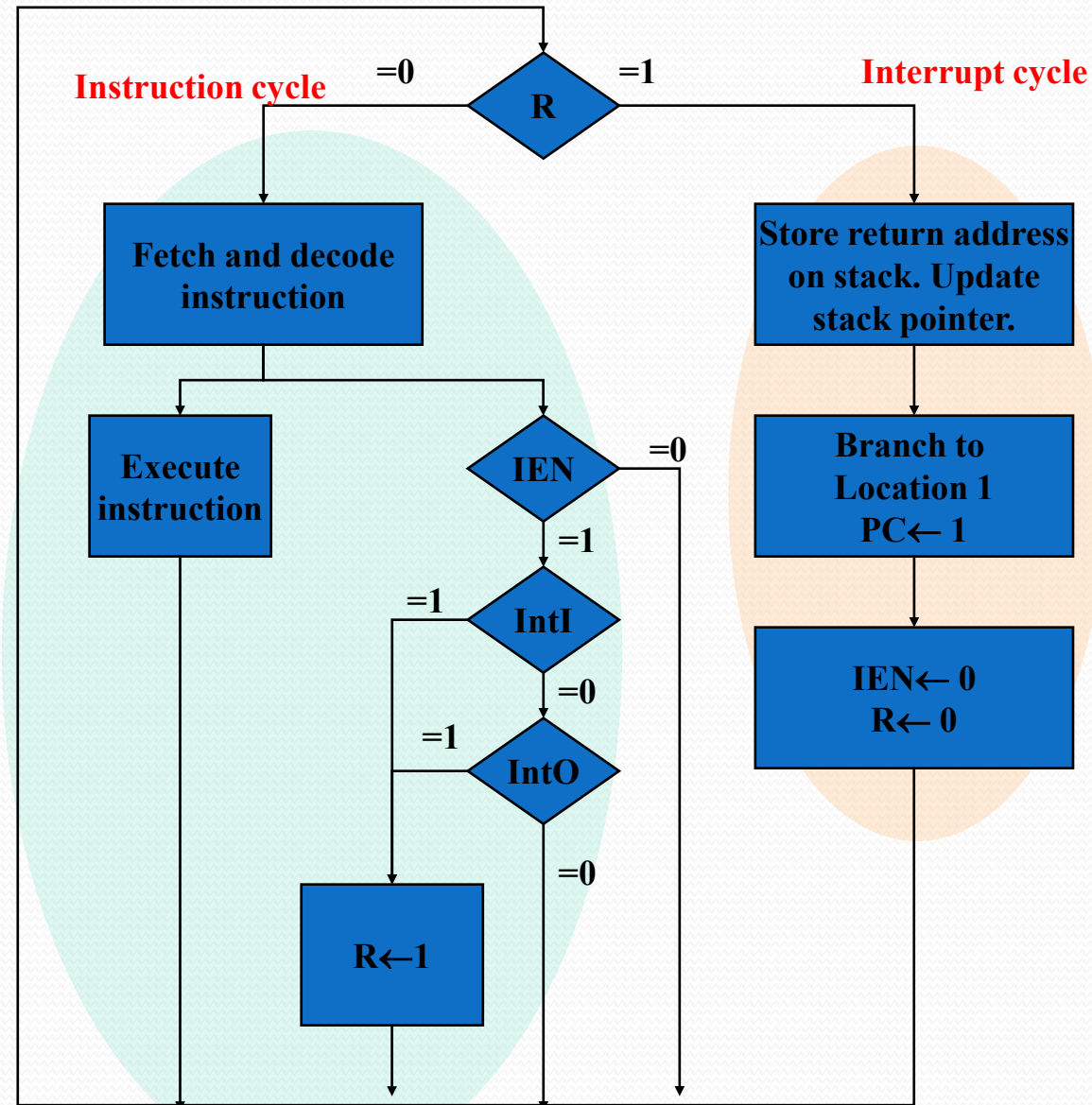



Interrupt cycles

Condition for a recognizable event

Set this flag

- Log the interrupt event during instruction cycle.
 - $T_0' T_1' T_2' (IEN)(INT_0 + INT_1): R \leftarrow 1$
- Interrupt occurs **asynchronously**. Need to save
 - Return address
 - Status of current execution
 - Eg: interrupt occurs between an arithmetic instruction that set a flag and conditional jump instruction that acts on that flag.
 - Determine the interrupt vector address and branch to that address
 - Disable further interrupts (clear IEN flag).
 - User may re-enable the interrupt in the interrupt service routine.
- When R is set, go into interrupt acknowledgement cycle
 - RT_0 : $SP \leftarrow SP - 1, TR \leftarrow PC$
 - RT_1 : $AR \leftarrow SP$
 - RT_2 : $M[AR] \leftarrow FLAGS, SP \leftarrow SP - 1$
 - RT_3 : $AR \leftarrow SP, PC \leftarrow 0$
 - RT_4 : $M[AR] \leftarrow TR, PC \leftarrow PC + 1, IEN \leftarrow 0, R \leftarrow 0, SC \leftarrow 0$

Interrupt vector address is at location 1

Listing of all control functions and microoperations

Fetch	R'T0	: $AR \leftarrow PC$
	R'T1	: $IR \leftarrow M[AR], PC \leftarrow PC+1$
Decode	R'T2	: $D0, \dots, D7 \leftarrow \text{Decode } IR(12-14), AR \leftarrow IR(0-11), I \leftarrow IR(15)$
Indirect	D7'IT3	: $AR \leftarrow M[AR]$
Interrupt	T0'T1'T2'(IEN)(FGI+FGO)	: $R \leftarrow 1$
Interrupt decode	RT0	: $SP \leftarrow SP-1, TR \leftarrow PC$
	RT1	: $AR \leftarrow SP$
	RT2	: $M[AR] \leftarrow \text{FLAGS}, SP \leftarrow SP-1$
	RT3	: $AR \leftarrow SP, PC \leftarrow 0$
	RT4	: $M[AR] \leftarrow TR, PC \leftarrow PC+1, IEN \leftarrow 0, R \leftarrow 0, SC \leftarrow 0$
Memory Reference Instruction (see table)		
Register Reference Instruction (see table)		
Initialization: Reset $RS=1$: clear all ($RS= D F/F$ with D input connected to reset pin. As long as D is high, Q output will remain high.		

Synthesizing the Control logic

- Signals for S_3, S_2, S_1 and S_0 to select which of the 11 registers drive the bus
- Signals to control the inputs (LD, INR, CLR, DEC) of the 11 registers
- Signals to control the read and write inputs of memory
- Signals to set, clear, or complement the bit addressable FF
- Signals to control the ALU circuit

Interpreting RTL into logic gates

When this condition occurs, perform the operation on the right.

RT1: $AR \leftarrow SP$

Load the content on the bus into AR.

Content of SP to be placed on the bus.

Select which of the 10 registers drive the bus

BUN	D ₄ T ₄	PC ← AR	X1: AR
CALL	D ₅ T ₄	TR ← AR	
Fetch	R'T ₀	AR ← PC	X2: PC
Interrupt	RT ₀	TR ← PC	
CALL	D ₅ T ₆	M[AR] ← PC	
DSZ	D ₆ T ₆	M[AR] ← DR	X3: DR
STA	D ₃ T ₄	M[AR] ← AC	X4: AC
PUSH	D ₇ I' T ₅ B ₆ K ₆	M[AR] ← AC	
AC2SP	rB ₆ K ₀	SP ← AC	
Decode	R'T ₂	AR ← IR(0-11)	X5: IR
Interrupt	RT ₄	M[AR] ← TR	X6: TR
CALL	D ₅ T ₇	PC ← TR	
Fetch	R'T ₁	IR ← M[AR]	X7: Memory
Indirect	D ₇ 'T ₃	AR ← M[AR]	
LDB	D ₀ T ₄	BP ← M[AR]	
LDX	D ₁ T ₄	XR ← M[AR]	
LDA	D ₂ T ₄	DR ← M[AR]	
DSZ	D ₆ T ₄	DR ← M[AR]	
LDABP	D ₇ I' T ₄ B ₆ K ₂	DR ← M[AR]	
IRET	D ₇ I' T ₄ B ₆ K ₃	PC ← M[AR]	
IRET	D ₇ I' T ₆ B ₆ K ₃	FLAGS ← M[AR]	
RET	D ₇ I' T ₄ B ₆ K ₄	PC ← M[AR]	
POP	D ₇ I' T ₄ B ₆ K ₅	DR ← M[AR]	

X8=OR(...)

Interrupt	RT ₁	AR ← SP	X8: SP
Interrupt	RT ₃	AR ← SP	
CALL	D ₅ T ₅	AR ← SP	
SP2BP	rB ₆ K ₁	BP ← SP	
IRET	D ₇ I' T ₃ B ₆ K ₃	AR ← SP	
IRET	D ₇ I' T ₅ B ₆ K ₃	AR ← SP	
RET	D ₇ I' T ₃ B ₆ K ₄	AR ← SP	
POP	D ₇ I' T ₃ B ₆ K ₅	AR ← SP	
PUSH	D ₇ I' T ₄ B ₆ K ₆	AR ← SP	X9: BP
LDABP	D ₇ I' T ₃ B ₆ K ₂	AR ← BP	
Interrupt	RT ₂	M[AR] ← FLAGS	X10: FLAGS
ADD	D ₇ I' T ₃ B ₄ K ₂	DR ← XR	X11: XR
ADC	D ₇ I' T ₃ B ₄ K ₃	DR ← XR	
SUB	D ₇ I' T ₃ B ₄ K ₄	DR ← XR	
SBB	D ₇ I' T ₃ B ₄ K ₅	DR ← XR	
AND	D ₇ I' T ₃ B ₄ K ₆	DR ← XR	
OR	D ₇ I' T ₃ B ₄ K ₇	DR ← XR	
XOR	D ₇ I' T ₃ B ₅ K ₀	DR ← XR	

Control of common bus via S0,S1,S2,S3

x ₁	x ₂	x ₃	x ₄	x ₅	x ₆	x ₇	x ₈	x ₉	x ₁₀	x ₁₁	S ₃	S ₂	S ₁	S ₀	
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	None
1	0	0	0	0	0	0	0	0	0	0	0	0	0	1	AR
0	1	0	0	0	0	0	0	0	0	0	0	0	1	0	PC
0	0	1	0	0	0	0	0	0	0	0	0	0	1	1	DR
0	0	0	1	0	0	0	0	0	0	0	0	1	0	0	AC
0	0	0	0	1	0	0	0	0	0	0	0	1	0	1	IR
0	0	0	0	0	1	0	0	0	0	0	0	1	1	0	TR
0	0	0	0	0	0	1	0	0	0	0	0	1	1	1	MEMORY
0	0	0	0	0	0	0	1	0	0	0	1	0	0	0	SP
0	0	0	0	0	0	0	0	1	0	0	1	0	0	1	BP
0	0	0	0	0	0	0	0	0	1	0	1	0	1	0	FLAGS
0	0	0	0	0	0	0	0	0	0	1	1	0	1	0	XR

- From table of control functions, pick out all functions requiring each register to drive bus
- Derive logic function for X
 - $X_n = \text{OR (corresponding conditions)}$
- Send X_n into a 16 to 4 encoder to derive S_0, S_1, S_2, S_3 .
- S_0, S_1, S_2, S_3 are then used to drive the bus selectors.

RET	$D_7I'T_3B_6K_4$	$AR \leftarrow SP$
IRET	$D_7I'T_3B_6K_3$	$AR \leftarrow SP$
CALL	D_5T_5	$AR \leftarrow SP$
PUSH	$D_7I'T_4B_6K_6$	$AR \leftarrow SP$
POP	$D_7I'T_3B_6K_5$	$AR \leftarrow SP$
Interrupt	RT_3	$AR \leftarrow SP$
Interrupt	RT_1	$AR \leftarrow SP$
IRET	$D_7I'T_5B_6K_3$	$AR \leftarrow SP$
Fetch	$R'T_0$	$AR \leftarrow PC$
LDABP	$D_7I'T_3B_6K_2$	$AR \leftarrow BP$
Indirect	$D_7'T_3$	$AR \leftarrow M[AR]$
Decode	$R'T_2$	$AR \leftarrow IR(0-11)$
Interrupt	RT_3	$PC \leftarrow 0$
Interrupt	RT_4	$PC \leftarrow PC + 1$
SZAC	rB_6K_7Z	$PC \leftarrow PC + 1$
SPAC	$rB_7K_1S'Z'$	$PC \leftarrow PC + 1$
SNAC	rB_7K_0S	$PC \leftarrow PC + 1$
SCC	rB_7K_3C'	$PC \leftarrow PC + 1$
DSZ	D_6T_6Y	$PC \leftarrow PC + 1$
Fetch	$R'T_1$	$PC \leftarrow PC + 1$
IRET	$D_7I'T_4B_6K_3$	$PC \leftarrow M[AR]$
RET	$D_7I'T_4B_6K_4$	$PC \leftarrow M[AR]$
CALL	D_5T_7	$PC \leftarrow TR$
BUN	D_4T_4	$PC \leftarrow AR$

Signals to control the
(LD,INR,CLR,DEC) of the
11 registers

CLR_{PC} = $RT_4 \vee$ reset

INR_{PC} = OR(...)

LD_{PC} = OR(...)

**Group all records with PC on the left.
Implies that under the conditions, PC is to
be changed accordingly.**

PUSH	$D_7I' T_5 B_6K_6$	$M[AR] \leftarrow AC$
STA	D_3T_4	$M[AR] \leftarrow AC$
Interrupt	RT_4	$M[AR] \leftarrow TR$
Interrupt	RT_2	$M[AR] \leftarrow \text{FLAGS}$
CALL	D_5T_6	$M[AR] \leftarrow PC$
DSZ	D_6T_6	$M[AR] \leftarrow DR$
Interrupt	RT_0	$TR \leftarrow PC$
CALL	D_5T_4	$TR \leftarrow AR$
LDX	D_1T_4	$XR \leftarrow M[AR]$
DSZ	D_6T_5	$DR \leftarrow DR - 1$
LDABP	$D_7I' T_4 B_6K_2$	$DR \leftarrow M[AR]$
POP	$D_7I' T_4 B_6K_5$	$DR \leftarrow M[AR]$
LDA	D_2T_4	$DR \leftarrow M[AR]$
DSZ	D_6T_4	$DR \leftarrow M[AR]$
XOR	$D_7I' T_3 B_5K_0$	$DR \leftarrow XR$
ADD	$D_7I' T_3 B_4K_2$	$DR \leftarrow XR$
ADC	$D_7I' T_3 B_4K_3$	$DR \leftarrow XR$
SBB	$D_7I' T_3 B_4K_5$	$DR \leftarrow XR$
SUB	$D_7I' T_3 B_4K_4$	$DR \leftarrow XR$
AND	$D_7I' T_3 B_4K_6$	$DR \leftarrow XR$
OR	$D_7I' T_3 B_4K_7$	$DR \leftarrow XR$


More controls

CALL	D_5T_4	$SP \leftarrow SP - 1$
PUSH	$D_7I' T_3 B_6K_6$	$SP \leftarrow SP - 1$
Interrupt	RT_2	$SP \leftarrow SP - 1$
Interrupt	RT_0	$SP \leftarrow SP - 1$
RET	$D_7I' T_4 B_6K_4$	$SP \leftarrow SP + 1$
IRET	$D_7I' T_4 B_6K_3$	$SP \leftarrow SP + 1$
IRET	$D_7I' T_6 B_6K_3$	$SP \leftarrow SP + 1$
POP	$D_7I' T_4 B_6K_5$	$SP \leftarrow SP + 1$
AC2SP	rB_6K_0	$SP \leftarrow AC$
SP2BP	rB_6K_1	$BP \leftarrow SP$
LDB	D_0T_4	$BP \leftarrow M[AR]$
Fetch	$R'T_1$	$IR \leftarrow M[AR]$
IRET	$D_7I' T_6 B_6K_3$	$\text{FLAGS} \leftarrow M[AR]$

Logic for control of F/F

CLC	rB_5K_5	$C \leftarrow 0$
CMC	rB_8K_6	$C \leftarrow C'$
STC	rB_5K_7	$C \leftarrow 1$
IRET	$D_7I'T_6B_6K_3$	$IEN \leftarrow 1$
ION	rB_7K_4	$IEN \leftarrow 1$
IOF	rB_7K_5	$IEN \leftarrow 0$
Interrupt	RT_4	$IEN \leftarrow 0$
Interrupt	RT_4	$R \leftarrow 0$
Interrupt	$T_0'T_1'T_2'(IEN(FGI + FGO))$	$R \leftarrow 1$
Decode	$R'T_2$	$I \leftarrow IR(15)$

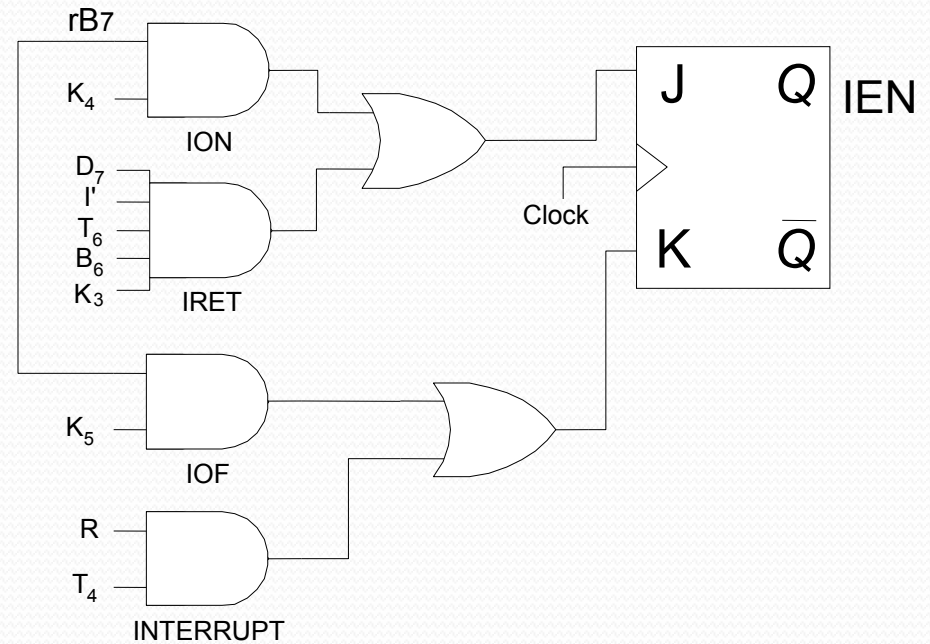Link to ALU. To be considered with ALU design



Circuit for IEN F/F

Completing the picture for the F/F

SHR	rB_5K_1	$SC \leftarrow 0$
SHL	rB_5K_2	$SC \leftarrow 0$
CLAC	rB_5K_3	$SC \leftarrow 0$
IRET	$D_7I' T_6 B_6K_3$	$SC \leftarrow 0$
LDABP	$D_7I' T_5 B_6K_2$	$SC \leftarrow 0$
CMAC	rB_5K_4	$SC \leftarrow 0$
CLC	rB_5K_5	$SC \leftarrow 0$
CMC	rB_8K_6	$SC \leftarrow 0$
STC	rB_5K_7	$SC \leftarrow 0$
AC2SP	rB_6K_0	$SC \leftarrow 0$
SP2BP	rB_6K_1	$SC \leftarrow 0$
BUN	D_4T_4	$SC \leftarrow 0$
LDA	D_2T_5	$SC \leftarrow 0$
LDB	D_0T_4	$SC \leftarrow 0$
LDX	D_1T_4	$SC \leftarrow 0$
Interrupt	RT_4	$SC \leftarrow 0$
CALL	D_5T_7	$SC \leftarrow 0$
DSZ	D_6T_6	$SC \leftarrow 0$
INC	rB_4K_0	$SC \leftarrow 0$
DEC	rB_4K_1	$SC \leftarrow 0$
ADD	$D_7I' T_4 B_4K_2$	$SC \leftarrow 0$
STA	D_3T_4	$SC \leftarrow 0$

RET	$D_7I' T_4 B_6K_4$	$SC \leftarrow 0$
IOF	rB_7K_5	$SC \leftarrow 0$
ION	rB_7K_4	$SC \leftarrow 0$
SCC	rB_7K_3C'	$SC \leftarrow 0$
SCC	rB_7K_3C	$SC \leftarrow 0$
SPAC	rB_7K_1	$SC \leftarrow 0$
SNAC	rB_7K_0	$SC \leftarrow 0$
SZAC	rB_6K_7	$SC \leftarrow 0$
PUSH	$D_7I' T_5 B_6K_6$	$SC \leftarrow 0$
POP	$D_7I' T_4 B_7K_5$	$SC \leftarrow 0$
SUB	$D_7I' T_4 B_4K_4$	$SC \leftarrow 0$
ADC	$D_7I' T_4 B_4K_3$	$SC \leftarrow 0$
XOR	$D_7I' T_4 B_5K_0$	$SC \leftarrow 0$
OR	$D_7I' T_4 B_4K_7$	$SC \leftarrow 0$
AND	$D_7I' T_4 B_4K_6$	$SC \leftarrow 0$
SBB	$D_7I' T_4 B_4K_5$	$SC \leftarrow 0$

The ALU and the accumulator


CLAC	rB_5K_3	$AC \leftarrow 0$
LDABP	$D_7I' T_3 B_6K_2$	$AC \leftarrow 0$
POP	$D_7I' T_3 B_6K_5$	$AC \leftarrow 0$
LDA	D_2T_4	$AC \leftarrow 0$
LDABP	$D_7I' T_5 B_6K_2$	$AC \leftarrow AC + DR$
POP	$D_7I' T_4 B_7K_5$	$AC \leftarrow AC + DR$
ADD	$D_7I' T_4 B_4K_2$	$AC \leftarrow AC + DR$
LDA	D_2T_5	$AC \leftarrow AC + DR$
INC	rB_4K_0	$AC \leftarrow AC + 1$
DEC	rB_4K_1	$AC \leftarrow AC - 1$
ADC	$D_7I' T_4 B_4K_3$	$AC \leftarrow AC + DR + C$
SBB	$D_7I' T_4 B_4K_5$	$AC \leftarrow AC - DR + C$
SUB	$D_7I' T_4 B_4K_4$	$AC \leftarrow AC - DR$
AND	$D_7I' T_4 B_4K_6$	$AC \leftarrow AC \wedge DR$
OR	$D_7I' T_4 B_4K_7$	$AC \leftarrow AC \vee DR$
XOR	$D_7I' T_4 B_5K_0$	$AC \leftarrow AC \oplus DR$
SHR	rB_5K_1	$AC \leftarrow \text{shr } AC, AC(15) \leftarrow C, C \leftarrow AC(0)$
SHL	rB_5K_2	$AC \leftarrow \text{shl } AC, AC(0) \leftarrow C, C \leftarrow AC(15)$
CMAC	rB_5K_4	$AC \leftarrow AC'$

We have not seen this. However before we go on to interpret this, we need to look at the design of the ALU.


Summary so far

- Derive the control logic in RTL format
 - To allow us to move data around on the local bus that we have created in according to the step needed to execute an instruction.
 - Produce the signal to select the ALU at the appropriate time
 - Signal to start the arithmetic/logic operation
 - Get the operands into the correct location
- Next
 - Look into the design of the ALU
 - The connection of the signal to the ALU

Implementation of arithmetic operations

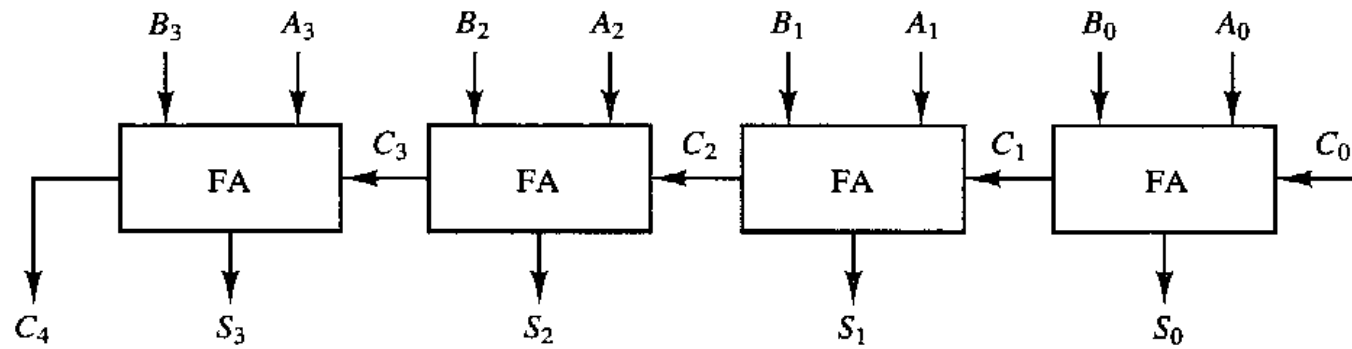


4-bit binary adder.

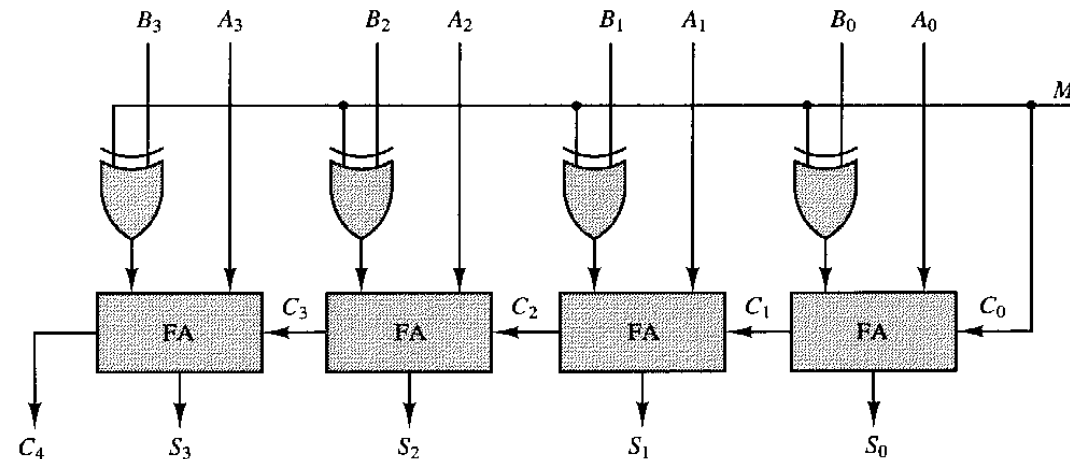

4-bit adder-subtractor.

Arithmetic micro-operations

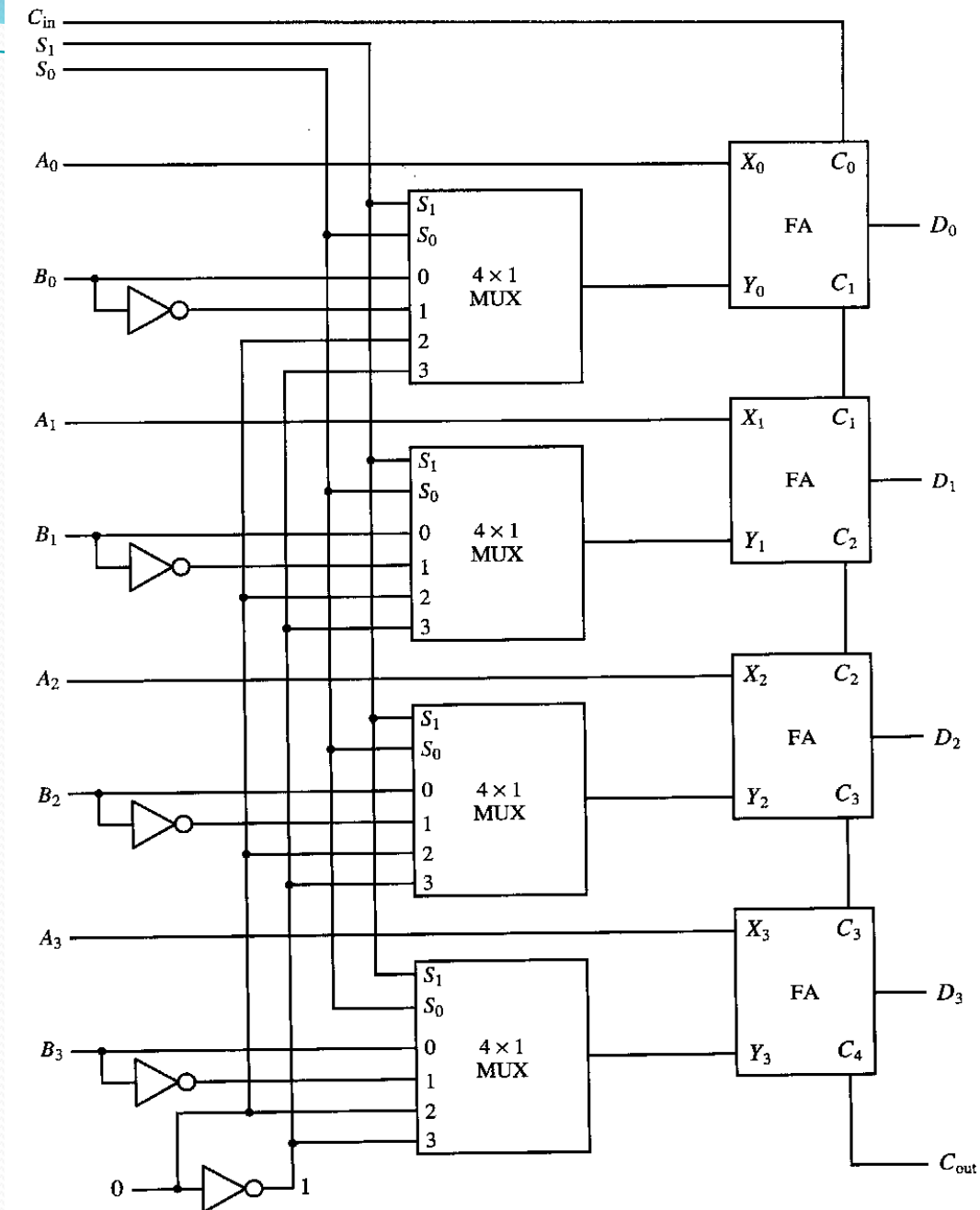- A combination of the previous elementary circuits
 - add, adc, sub, sbb, inc, dec




Arithmetic Circuit Function Table

Select			Input Y	Output $D = A + Y + C_{in}$	Microoperation
S_1	S_0	C_{in}			
0	0	0	B	$D = A + B$	Add
0	0	1	B	$D = A + B + 1$	Add with carry
0	1	0	\overline{B}	$D = A + \overline{B}$	Subtract with borrow
0	1	1	\overline{B}	$D = A + \overline{B} + 1$	Subtract
1	0	0	0	$D = A$	Transfer A
1	0	1	0	$D = A + 1$	Increment A
1	1	0	1	$D = A - 1$	Decrement A
1	1	1	1	$D = A$	Transfer A

Implementation of logic micro-operations

One stage of logic circuit

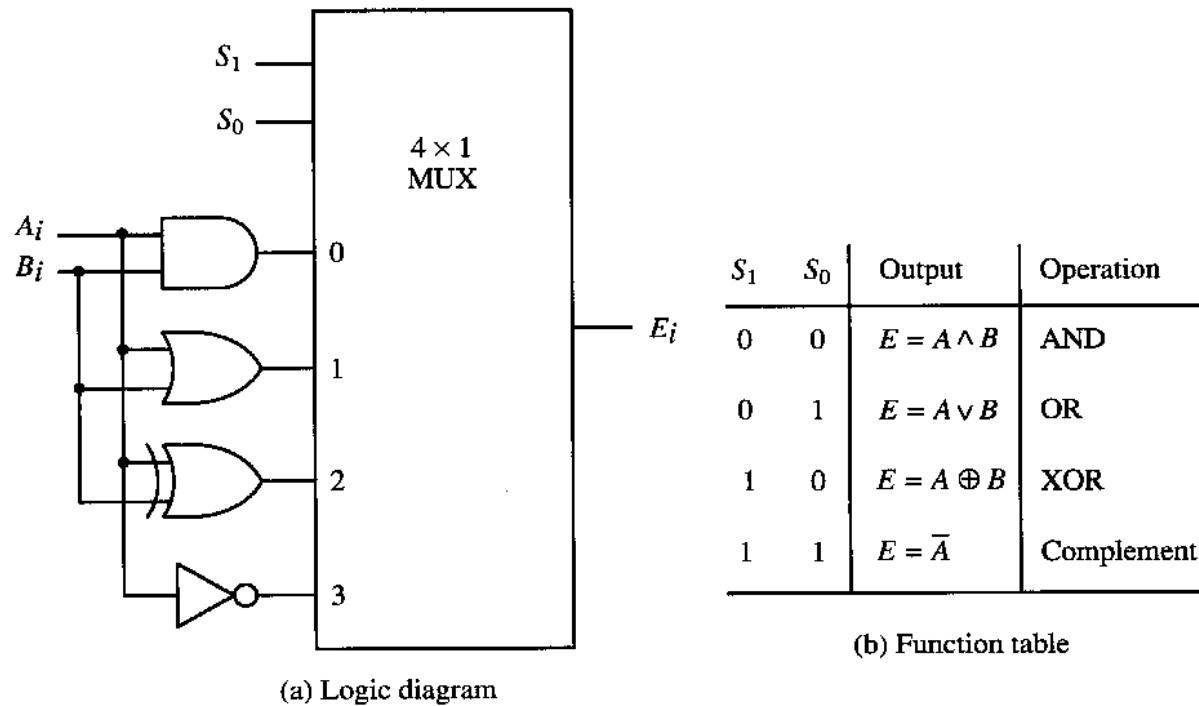


Shift micro-operations

Shift Microoperations

Symbolic designation	Description
$R \leftarrow \text{shl } R$	Shift-left register R
$R \leftarrow \text{shr } R$	Shift-right register R
$R \leftarrow \text{cil } R$	Circular shift-left register R
$R \leftarrow \text{cir } R$	Circular shift-right register R
$R \leftarrow \text{ashl } R$	Arithmetic shift-left R
$R \leftarrow \text{ashr } R$	Arithmetic shift-right R



Arithmetic shift right.

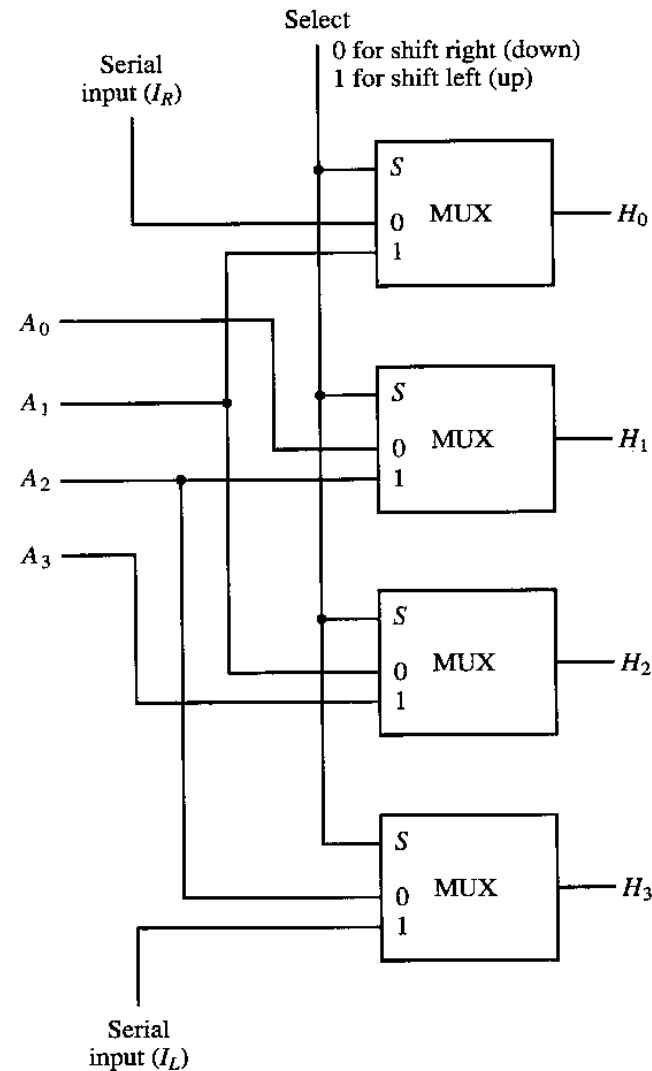


4-bit combinational circuit shifter.

Function table

Select	Output			
	H_0	H_1	H_2	H_3
0	I_R	A_0	A_1	A_2
1	A_1	A_2	A_3	I_L

Arithmetic logic shift micro-operations

S3	S2	S1	S0	Operation	Function
0	0	0	0	$F=A+1$	INC
0	0	0	1	$F=A+B+C_{in}$	ADD
0	0	1	0	$F=A-B+C_{in}$	SUB
0	0	1	1	$F=A-1$	DEC
0	1	0	0	$F=A \wedge B$	AND
0	1	0	1	$F=A \vee B$	OR
0	1	1	0	$F=A \oplus B$	XOR
0	1	1	1	$F=A'$	COM
1	0	x	x	$F=\text{shr } A$	SHR
1	1	x	x	$F=\text{shl } A$	SHL

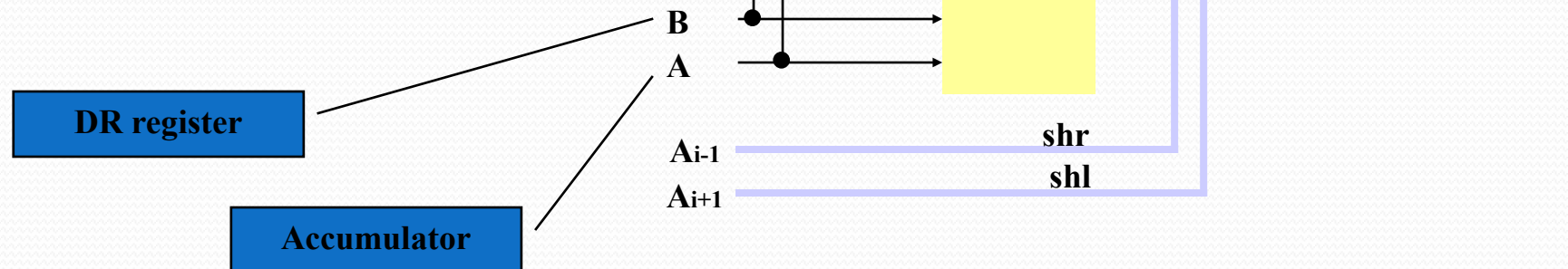

The ALU and the accumulator

CLAC	rB_5K_3	$AC \leftarrow 0$
LDABP	$D_7I' T_3 B_6K_2$	$AC \leftarrow 0$
POP	$D_7I' T_3 B_6K_5$	$AC \leftarrow 0$
LDA	D_2T_4	$AC \leftarrow 0$
INC	rB_4K_0	$AC \leftarrow AC + 1$
ADC	$D_7I' T_4 B_4K_3$	$AC \leftarrow AC + DR + C$
LDABP	$D_7I' T_5 B_6K_2$	$AC \leftarrow AC + DR + 0$
POP	$D_7I' T_4 B_7K_5$	$AC \leftarrow AC + DR + 0$
ADD	$D_7I' T_4 B_4K_2$	$AC \leftarrow AC + DR + 0$
LDA	D_2T_5	$AC \leftarrow AC + DR + 0$
SBB	$D_7I' T_4 B_4K_5$	$AC \leftarrow AC - DR + C$
SUB	$D_7I' T_4 B_4K_4$	$AC \leftarrow AC - DR + 0$
DEC	rB_4K_1	$AC \leftarrow AC - 1$
AND	$D_7I' T_4 B_4K_6$	$AC \leftarrow AC \wedge DR$
OR	$D_7I' T_4 B_4K_7$	$AC \leftarrow AC \vee DR$
XOR	$D_7I' T_4 B_5K_0$	$AC \leftarrow AC \oplus DR$
CMAC	rB_5K_4	$AC \leftarrow AC'$
SHR	rB_5K_1	$AC \leftarrow \text{shr } AC,$ $AC(15) \leftarrow C, C \leftarrow AC(0)$
SHL	rB_5K_2	$AC \leftarrow \text{shl } AC,$ $AC(0) \leftarrow C, C \leftarrow AC(15)$

$AC_{clr} = OR(\dots)$

Decoding Table

S3	S2	S1	S0	
0	0	0	0	N0
0	0	0	1	N1
0	0	1	0	N2
0	0	1	1	N3
0	1	0	0	N4
0	1	0	1	N5
0	1	1	0	N6
0	1	1	1	N7
1	0	x	x	N8
1	1	x	x	N12

N0

$N1=OR(\dots)$

$N2=OR(\dots)$

N3

N4

N5


N6

N7

N8


N12

ALU and Accumulator logic

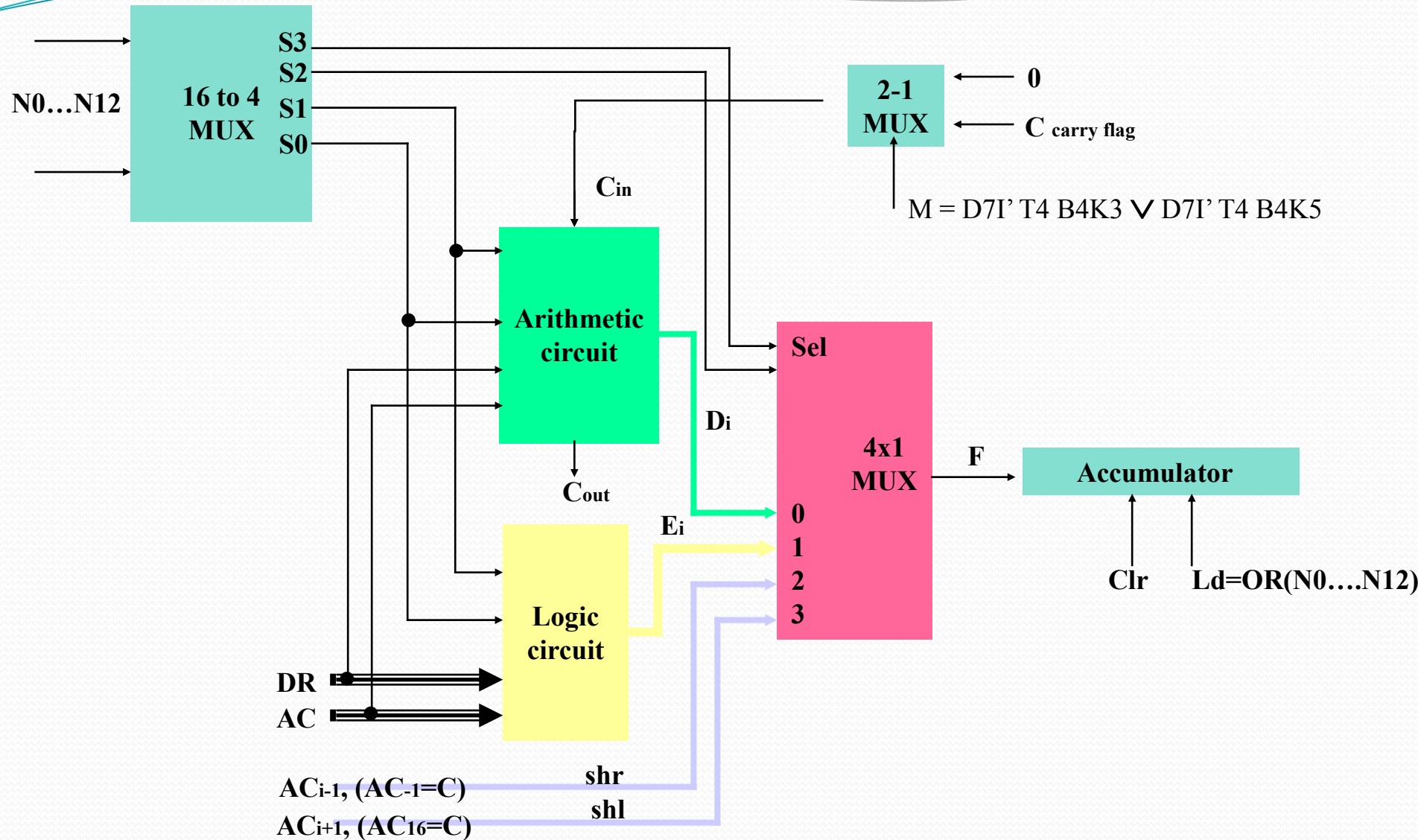

Condition	Q_{k+1}	J	K
rB5K5	0	0	1
rB8K6	Q_k'	1	1
rB5K7	1	1	0
$(N0 \vee N1 \vee N2 \vee N3) \wedge \text{Cout}$	1	1	0
$(N0 \vee N1 \vee N2 \vee N3) \wedge \text{Cout}'$	0	0	1
$N8 \wedge \text{AC}(0)$	1	1	0
$N8 \wedge \text{AC}(0)'$	0	0	1
$N9 \wedge \text{AC}(15)$	1	1	0
$N9 \wedge \text{AC}(15)'$	0	0	1
NOR(above conditions)	Q_k	0	0

g F/F

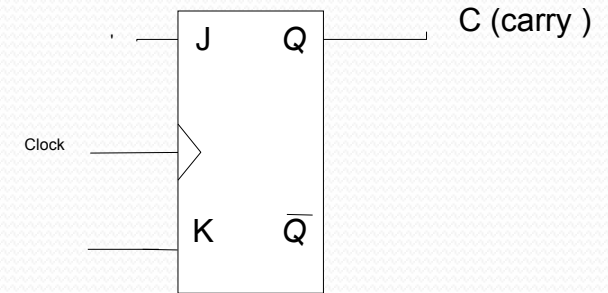


The logic for J and K input can now be derive using a sum of product or a product of sum method.

You have the logical design. Now it is a matter of coding them into VHDL/Verilog and then go through the placement and routing process.

General Specification of CPUs

General Specification of CPUs

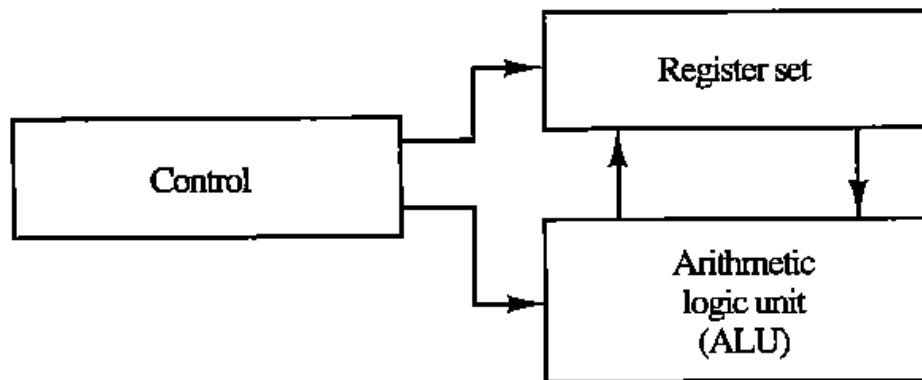
- General register organization
- Stack organization
- Instruction formats
- Addressing modes
- Data transfer and manipulation
- Program control
- Reduced instruction set computer



Major components of CPU

General register organization

- Registers for intermediate results
 - bus interconnection
 - eg: $R_1 \leftarrow R_2 + R_3$
- MUX A selector (SELA): to place the content of R_2 into bus A.
 - MUX B selector (SELB): to place the content of R_3 into bus B.
 - ALU operation selector (OPR): to provide the arithmetic addition $A + B$.
 - Decoder destination selector (SELD): to transfer the content of the output bus into R_1 .
- Activated by control word

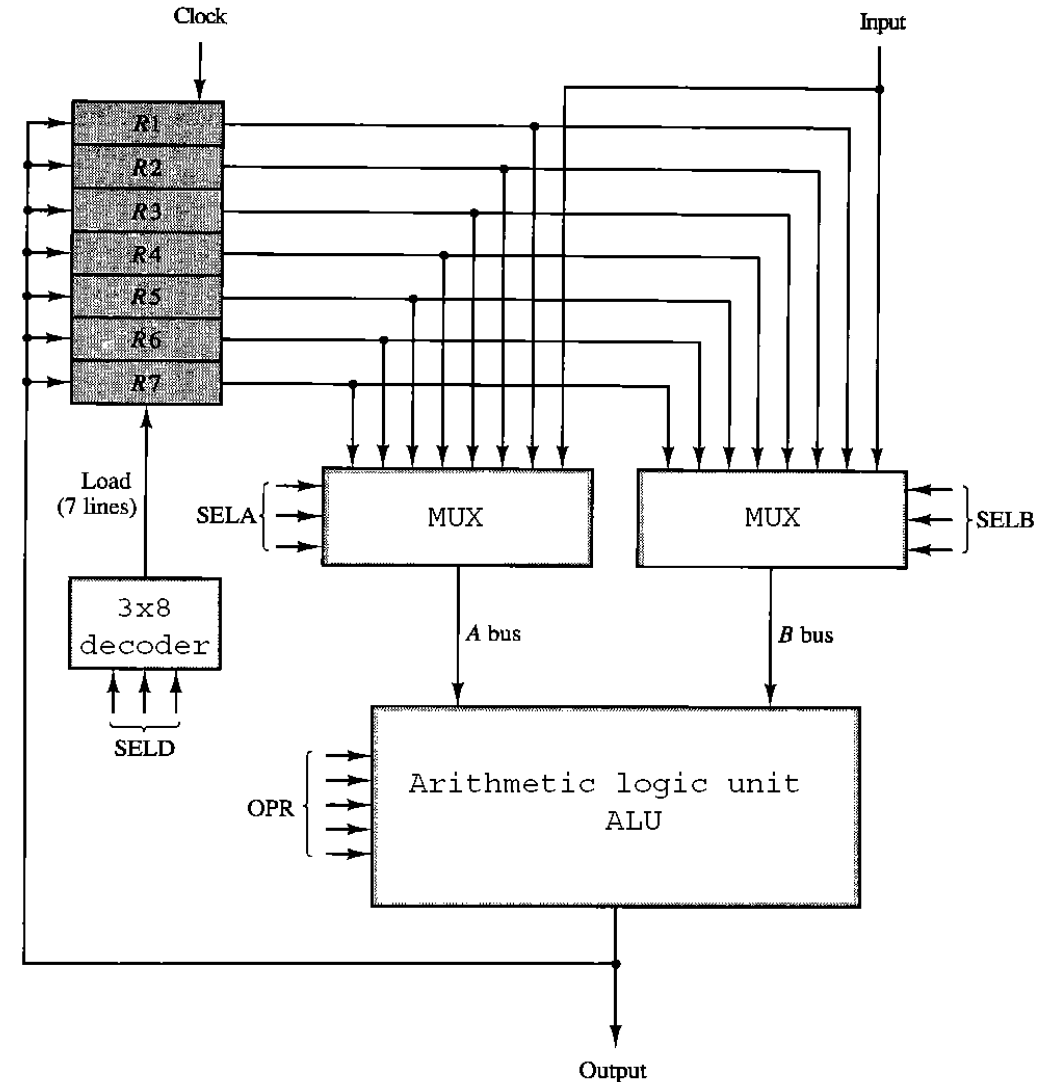


(a) Block diagram



(b) Control word

Control word

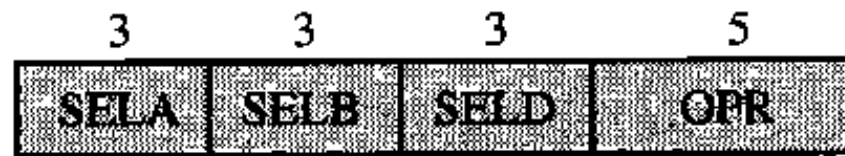

Encoding of register selection fields

Binary Code	SELA	SELB	SELD
000	Input	Input	None
001	R1	R1	R1
010	R2	R2	R2
011	R3	R3	R3
100	R4	R4	R4
101	R5	R5	R5
110	R6	R6	R6
111	R7	R7	R7


Encoding of ALU operations

OPR Select	Operation	Symbol
00000	Transfer A	TSFA
00001	Increment A	INCA
00010	Add $A + B$	ADD
00101	Subtract $A - B$	SUB
00110	Decrement A	DECA
01000	AND A and B	AND
01010	OR A and B	OR
01100	XOR A and B	XOR
01110	Complement A	COMA
10000	Shift right A	SHRA
11000	Shift left A	SHLA

Stack Organization


- LIFO
- Typical for temporary storage of variables/parameters
- 2 operations
 - push (for registers)
 - $SP \leftarrow SP + 1$
 - $M[SP] \leftarrow DR$
 - if ($SP = 0$) then ($FULL \leftarrow 1$)
 - $EMPTY \leftarrow 0$
 - pop (for registers)
 - $DR \leftarrow M[SP]$
 - $SP \leftarrow SP - 1$
 - if ($SP = 0$) then ($EMPTY \leftarrow 1$)
 - $FULL \leftarrow 0$
- type
 - registers
 - memory
 - normally do not provide checks for overflows
 - normally grows downwards

64 word stack registers

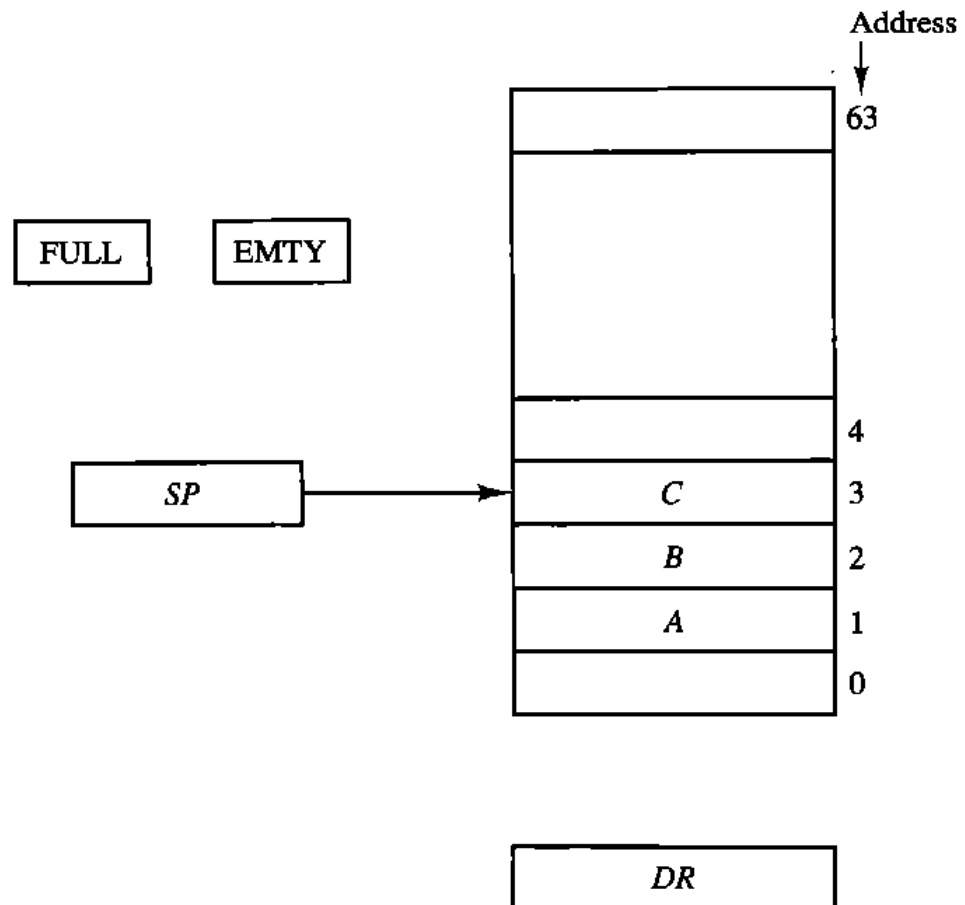

Reverse polish notation

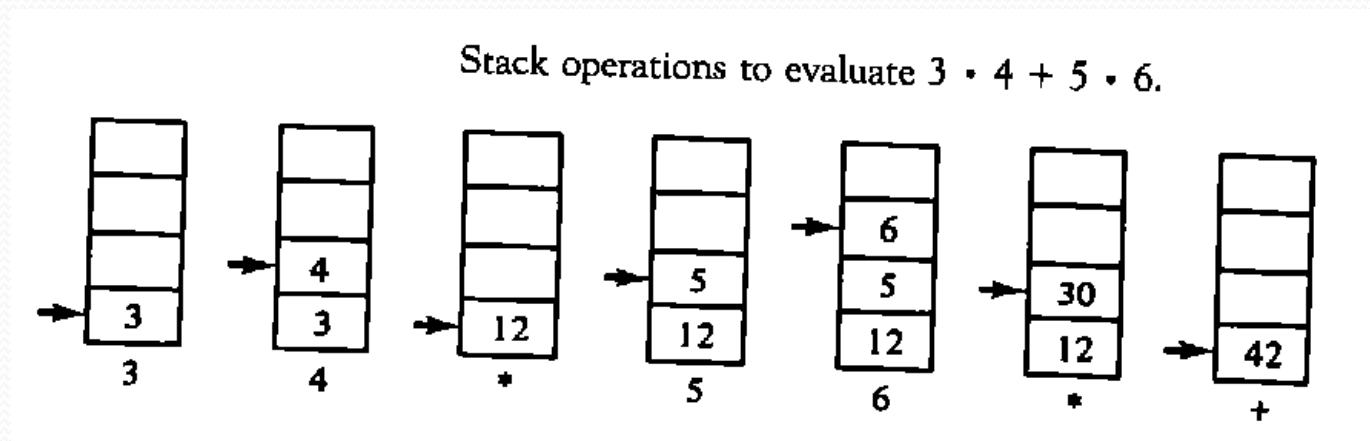- Notation:
 - Infix: $A+B$ RPN: $AB+$
 - infix: $(A+B)*[C*(D+E)+F]$ RPN: $AB+DE+C*F+*$
- Effective for arithmetic notation
 - any arithmetic expression can be expressed in parentheses-free polish notation
 - ideal for stack implementation





CPU organisation: 3 types

- Single accumulator organisation
 - all instruction performed with an implied accumulator
 - `ADD X`
- General register organisation
 - will require in general 3 register specification
 - `ADD R1, R2, R3, R1 ← R2 + R3`
 - or 2 register specification, if destination is same as one of the source
 - `ADD R2, R3, R2 ← R2 + R3`
- Stack organisation
 - as discussed before where the main instruction is the PUSH
 - no need for address field
 - `ADD`
 - the operands are pop off the stack, result are push back automatically on to the stack as well

Instruction formats

$$X = (A + B) * (C + D)$$

Three address instruction

ADD	R1, A, B	$R1 \leftarrow M[A] + M[B]$
ADD	R2, C, D	$R2 \leftarrow M[C] + M[D]$
MUL	X, R1, R2	$M[X] \leftarrow R1 * R2$

Two address instruction

MOV	R1, A	$R1 \leftarrow M[A]$
ADD	R1, B	$R1 \leftarrow R1 + M[B]$
MOV	R2, C	$R2 \leftarrow M[C]$
ADD	R2, D	$R2 \leftarrow R2 + M[D]$
MUL	R1, R2	$R1 \leftarrow R1 * R2$
MOV	X, R1	$M[X] \leftarrow R1$

One address instruction

LOAD	A	$AC \leftarrow M[A]$
ADD	B	$AC \leftarrow AC + M[B]$
STORE	T	$M[T] \leftarrow AC$
LOAD	C	$AC \leftarrow M[C]$
ADD	D	$AC \leftarrow AC + M[D]$
MUL	T	$AC \leftarrow AC * M[T]$
STORE	X	$M[X] \leftarrow AC$

Zero address instruction

PUSH	A	$TOS \leftarrow A$
PUSH	B	$TOS \leftarrow B$
ADD		$TOS \leftarrow (A + B)$
PUSH	C	$TOS \leftarrow C$
PUSH	D	$TOS \leftarrow D$
ADD		$TOS \leftarrow (C + D)$
MUL		$TOS \leftarrow (C + D) * (A + B)$
POP	X	$M[X] \leftarrow TOS$

RISC instructions

- Load-store architecture:
 - Use of only load and store instructions only to access memory
- All other instructions are register type
- Simplifies decoding – allow less work to be done in a clock cycle
 - Leads to better potential for higher frequency operation.

$$X = (A + B) * (C + D)$$

LOAD	R1, A	$R1 \leftarrow M[A]$
LOAD	R2, B	$R2 \leftarrow M[B]$
LOAD	R3, C	$R3 \leftarrow M[C]$
LOAD	R4, D	$R4 \leftarrow M[D]$
ADD	R1, R1, R2	$R1 \leftarrow R1 + R2$
ADD	R3, R3, R4	$R3 \leftarrow R3 + R4$
MUL	R1, R1, R3	$R1 \leftarrow R1 * R3$
STORE	X, R1	$M[X] \leftarrow R1$

Addressing modes

- To give programming versatility
- to reduce the number of bits in the addressing field of the instruction
- The various modes
 - Implied mode
 - Immediate mode
 - Register mode
 - Register indirect mode
 - Autoincrement or autodecrement mode
 - Direct address mode
 - Indirect address mode
 - Relative address mode
 - Indexed addressing mode
 - Base register addressing mode



Classification of instructions

- Data transfer instructions
- Data manipulation instructions
- Program control instructions

Data transfer instructions

Typical data transfer instructions

Recommended assembly language convention

Name	Mnemonic
Load	LD
Store	ST
Move	MOV
Exchange	XCH
Input	IN
Output	OUT
Push	PUSH
Pop	POP

Mode	Assembly Convention	Register Transfer
Direct address	LD ADR	$AC \leftarrow M[ADR]$
Indirect address	LD @ADR	$AC \leftarrow M[M[ADR]]$
Relative address	LD \$ADR	$AC \leftarrow M[PC + ADR]$
Immediate operand	LD #NBR	$AC \leftarrow NBR$
Index addressing	LD ADR(X)	$AC \leftarrow M[ADR + XR]$
Register	LD R1	$AC \leftarrow R1$
Register indirect	LD (R1)	$AC \leftarrow M[R1]$
Autoincrement	LD (R1)+	$AC \leftarrow M[R1], R1 \leftarrow R1 + 1$

Various addressing modes

Data manipulation instructions

TABLE 8-8 Typical Logical and Bit Manipulation Instructions

Name	Mnemonic
Clear	CLR
Complement	COM
AND	AND
OR	OR
Exclusive-OR	XOR
Clear carry	CLRC
Set carry	SETC
Complement carry	COMC
Enable interrupt	EI
Disable interrupt	DI

TABLE 8-7 Typical Arithmetic Instructions

Name	Mnemonic
Increment	INC
Decrement	DEC
Add	ADD
Subtract	SUB
Multiply	MUL
Divide	DIV
Add with carry	ADDC
Subtract with borrow	SUBB
Negate (2's complement)	NEG


TABLE 8-9 Typical Shift Instructions

Name	Mnemonic
Logical shift right	SHR
Logical shift left	SHL
Arithmetic shift right	SHRA
Arithmetic shift left	SHLA
Rotate right	ROR
Rotate left	ROL
Rotate right through carry	RORC
Rotate left through carry	ROLC

Program control

Typical Program Control Instructions

Name	Mnemonic
Branch	BR
Jump	JMP
Skip	SKP
Call	CALL
Return	RET
Compare (by subtraction)	CMP
Test (by ANDing)	TST

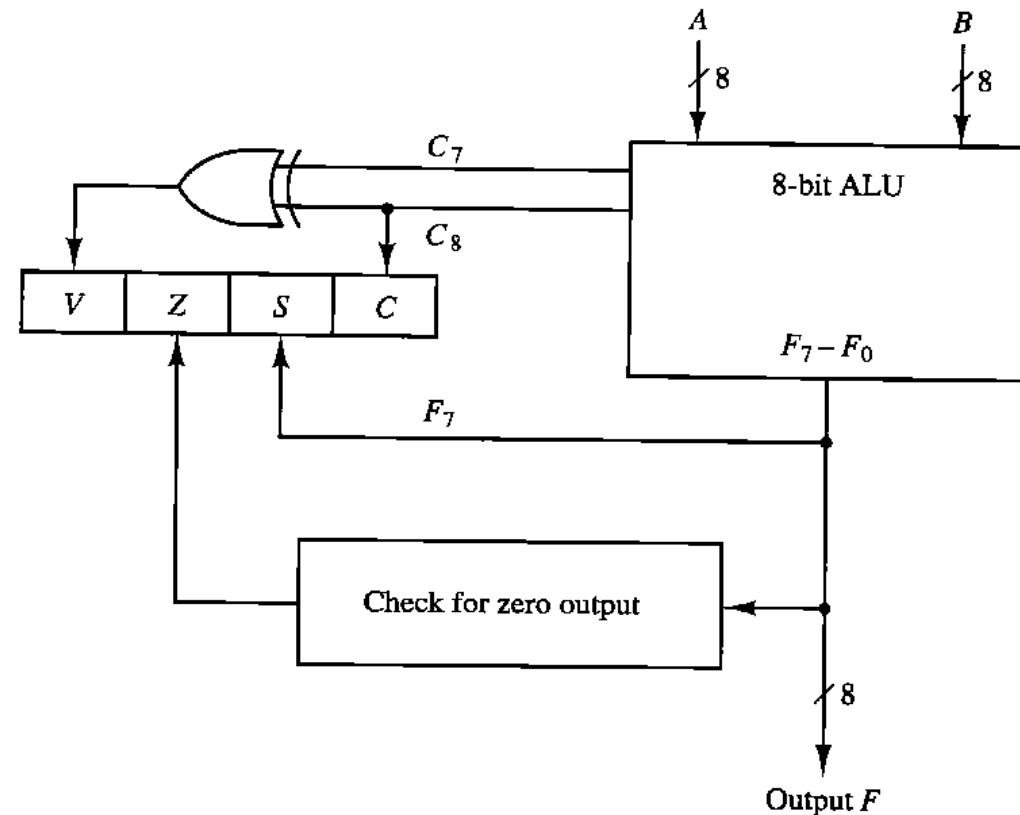

Status register bits.

$$\begin{array}{r}
 A: \quad 11110000 \\
 \bar{B} + 1: +11101100 \\
 \hline
 A - B: \quad 11011100
 \end{array}$$

$$C = 1 \quad S = 1 \quad V = 0 \quad Z = 0$$

Conditional branch instructions

Mnemonic	Branch condition	Tested condition
BZ	Branch if zero	$Z = 1$
BNZ	Branch if not zero	$Z = 0$
BC	Branch if carry	$C = 1$
BNC	Branch if no carry	$C = 0$
BP	Branch if plus	$S = 0$
BM	Branch if minus	$S = 1$
BV	Branch if overflow	$V = 1$
BNV	Branch if no overflow	$V = 0$
<i>Unsigned compare conditions ($A - B$)</i>		
BHI	Branch if higher	$A > B$
BHE	Branch if higher or equal	$A \geq B$
BLO	Branch if lower	$A < B$
BLOE	Branch if lower or equal	$A \leq B$
BE	Branch if equal	$A = B$
BNE	Branch if not equal	$A \neq B$
<i>Signed compare conditions ($A - B$)</i>		
BGT	Branch if greater than	$A > B$
BGE	Branch if greater or equal	$A \geq B$
BLT	Branch if less than	$A < B$
BLE	Branch if less or equal	$A \leq B$
BE	Branch if equal	$A = B$
BNE	Branch if not equal	$A \neq B$