


EE2023 TUTORIAL 5 (SOLUTIONS)

Solution to Q.1

Consider $t = 0^-$:

Assume that circuit has been in the same state for an extended period of time. Since the inductor acts as a short circuit in steady-state, we have
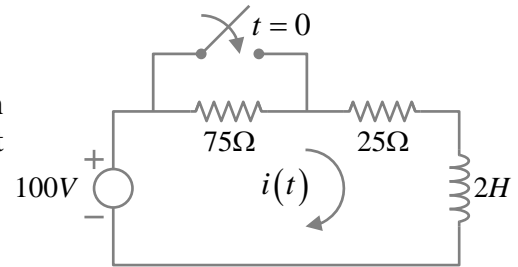
$$\left[i(t) = \frac{100}{75 + 25} = 1A \right] \rightarrow \mathbf{i(0^-) = 1A}$$



Consider $t \geq 0$:

At $t = 0$, the switch is closed, shorting out the 75Ω resistor. Applying Kirchoff voltage law:

$$2 \frac{di(t)}{dt} + 25i(t) = 100 \quad \dots\dots (\clubsuit)$$


Using Laplace transform

Transforming (\clubsuit) into the s -domain using Laplace transform:

$$\left(2 \frac{di(t)}{dt} + 25i(t) = 100 \right) \leftrightarrow \left(2[sI(s) - i(0^-)] + 25I(s) = \frac{100}{s} \right)$$

With $i(0^-) = 1$, we get

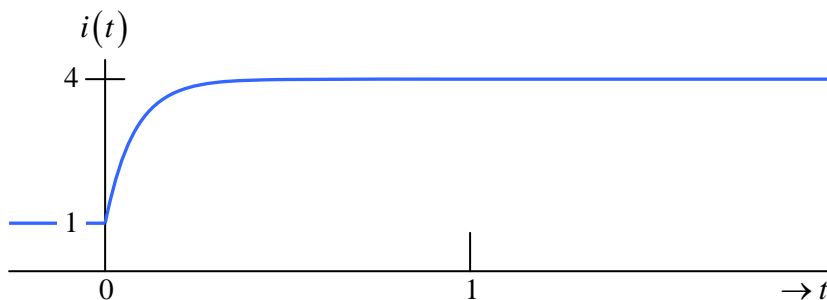
$$\left[I(s) = \frac{2s + 100}{s(2s + 25)} = \frac{4}{s} - \frac{3}{s + 12.5} \right] \rightarrow \mathbf{i(t) = 4 - 3\exp(-12.5t)}.$$



Solution to Q.2

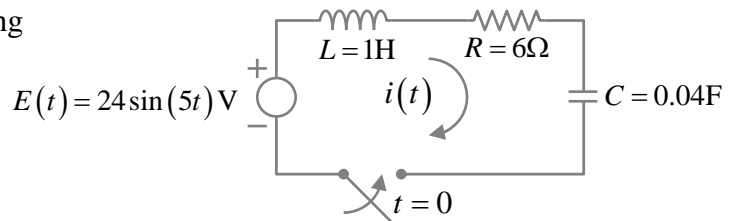- (a) Using KVL, the differential equation relating $i(t)$ to $E(t)$ is

$$L \frac{di(t)}{dt} + Ri(t) + \frac{1}{C} \int_{0^-}^t i(\tau) d\tau = E(t)$$



Differentiating both sides with respect to t :

$$L \frac{d^2 i(t)}{dt^2} + R \frac{di(t)}{dt} + \frac{1}{C} i(t) = \frac{dE(t)}{dt} \quad \dots (\clubsuit)$$

- (b) Substituting $L = 1$, $R = 6$, $C = 0.04$, and $E(t) = 24 \sin(5t)$ into (\clubsuit) , we have

$$\frac{d^2 i(t)}{dt^2} + 6 \frac{di(t)}{dt} + 25 i(t) = 120 \cos(5t) \quad \dots (\heartsuit)$$

Transforming (\heartsuit) into the s -domain using Laplace transform:

$$\left(\frac{d^2 i(t)}{dt^2} + 6 \frac{di(t)}{dt} + 25 i(t) = 120 \cos(5t) \right)$$

$$\Downarrow$$


$$\left(\left[s^2 I(s) - si(0^-) - i'(0^-) \right] + 6 \left[sI(s) - i(0^-) \right] + 25 I(s) = \frac{120s}{s^2 + 25} \right)$$

Since the initial conditions $i(0^-)$ and $i'(0^-)$ are zero, we have

$$I(s) (s^2 + 6s + 25) = \frac{120s}{s^2 + 25}$$

$$I(s) = \frac{120s}{(s^2 + 6s + 25)(s^2 + 25)} = -\frac{20}{s^2 + 6s + 25} + \frac{20}{s^2 + 25} = -5 \frac{4}{(s+3)^2 + 16} + 4 \frac{5}{s^2 + 25}$$
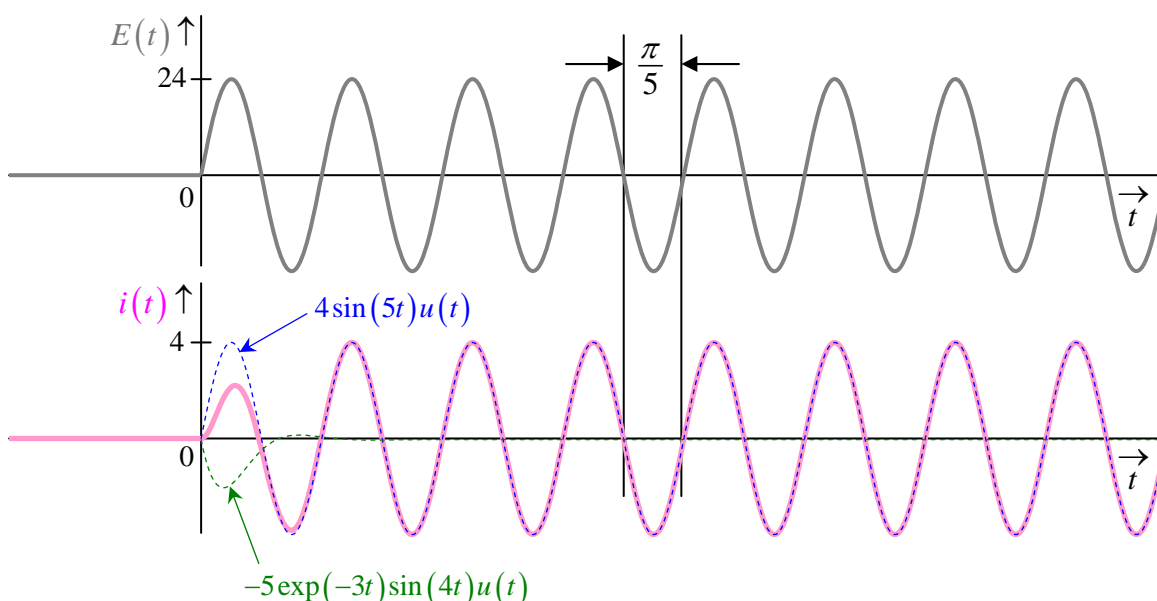
$$\therefore i(t) = -5 \exp(-3t) \sin(4t) + 4 \sin(5t)$$




Solution to Q.3

- (a) Assume that Ah Kow ingests that first tablet at $t = 0$. The cumulative amount of drug administered up till time t should thus be

$$q(t) = 100u(t) + 50u(t-1).$$

The system input $f(t)$, which is defined as the rate at which drug was administered, is therefore given by
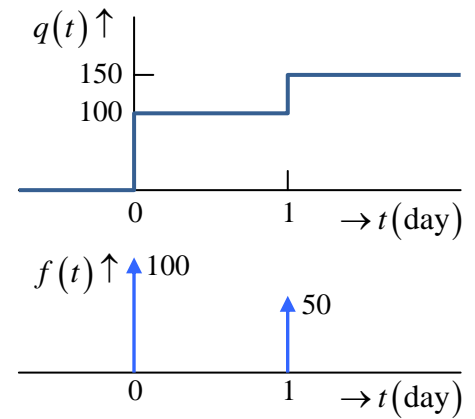
$$f(t) = \frac{dq(t)}{dt} = 100\delta(t) + 50\delta(t-1).$$



- (b) Given that there are no stress relief drug in Ah Kow's bloodstream when the first tablet was ingested, the initial conditions of the system are

$$y(0^-) = 0 \text{ and } y'(0^-) = 0.$$

- (c) The DE describing the quantity of drug in Ah Kow's body given as

$$\frac{d^2 y(t)}{dt^2} + 3\frac{dy(t)}{dt} + 2y(t) = 100\delta(t) + 50\delta(t-1).$$


Applying Laplace transformation (with all initial conditions set to zero):

$$s^2 Y(s) + 3sY(s) + 2Y(s) = 100 + 50\exp(-s)$$

$$Y(s) = \frac{(2 + \exp(-s))50}{s^2 + 3s + 2} = (2 + \exp(-s)) \left[\frac{50}{s+1} - \frac{50}{s+2} \right]$$

Therefore,
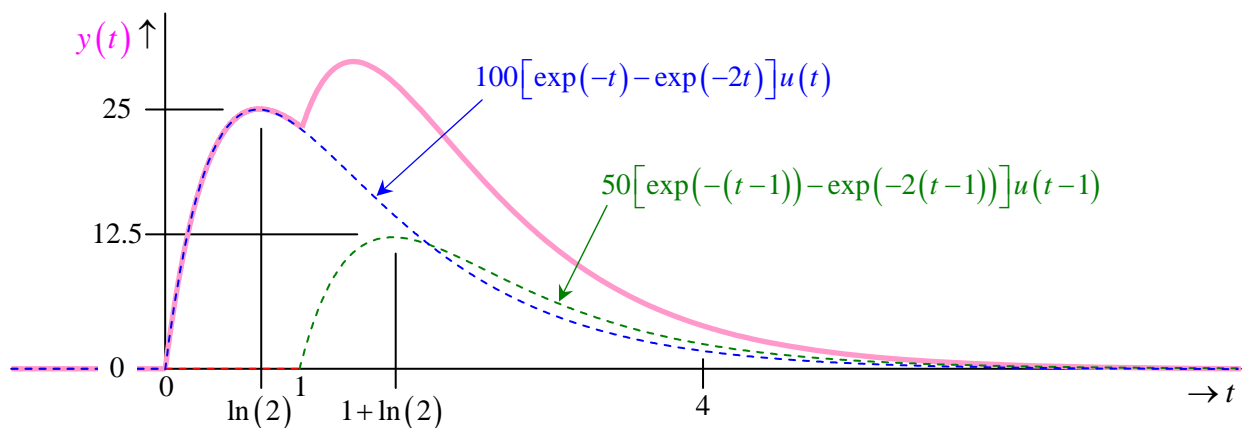
$$\begin{aligned} y(t) &= \mathcal{L}^{-1}\{Y(s)\} = \mathcal{L}^{-1}\left\{100\left[\frac{1}{s+1} - \frac{1}{s+2}\right] + 50\left[\frac{1}{s+1} - \frac{1}{s+2}\right]\exp(-s)\right\} \\ &= 100[\exp(-t) - \exp(-2t)]u(t) + 50[\exp(-(t-1)) - \exp(-2(t-1))]u(t-1) \end{aligned}$$



Amount of medicine in Ah Kow's body by the time of the exam is

$$y(4) = 100[\exp(-4) - \exp(-8)] + 50[\exp(-3) - \exp(-6)] = 4.1634 \text{ mg}.$$