

## CG1108 – Lab 2 : KVL and KCL Verification

<b>Name:</b> _____  <b>Matric. No.</b> _____  <b>Group:</b> _____	<b>Activities Completed</b>	<b>Verified By</b>	<b>Marks From 3</b>
	a		
	b		
	c		
	d		
	e		

### 1. Objectives of the Experiment

- a) To build circuits on breadboard from circuit schematics.
- b) To apply and verify KVL and KCL.

### 2. Equipment to be used


- Lab DC power supply
- Digital multi-meter
- Breadboard

### 3. Components

- Resistors

## In-lab activities

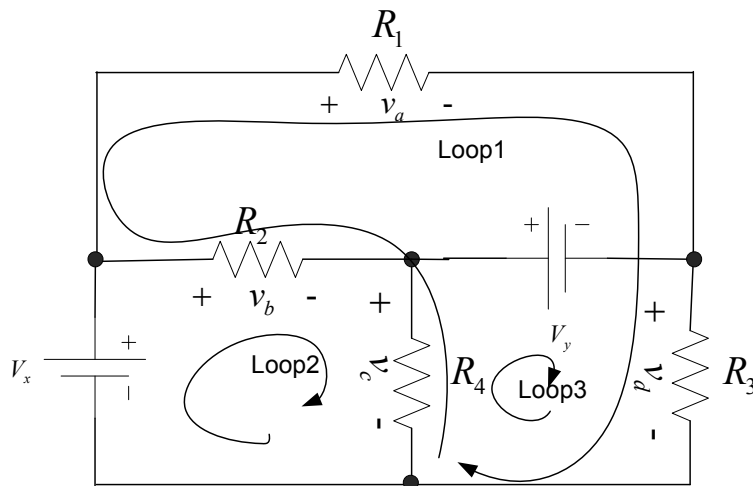- a) **Pick four resistors from the component rack and build the circuit on the bread-board according to the schematic.** You may choose the source voltages yourself.  
(Please ask the GA to check your circuit after you have completed the circuit.)



**Note down the values** of the voltage sources and the resistors :

$$V_x =$$

$$V_y =$$

$$R_1 =$$

$$R_2 =$$

$$R_3 =$$

$$R_4 =$$

**Measure the voltages** using the multimeter and note down below:

$$V_a =$$

$$V_b =$$

$$V_c =$$

$$V_d =$$

**Write KVL equations for the following loops and verify that KVL is satisfied.**

Loop 1:


Loop 2:

Loop 3:

Conclusion:

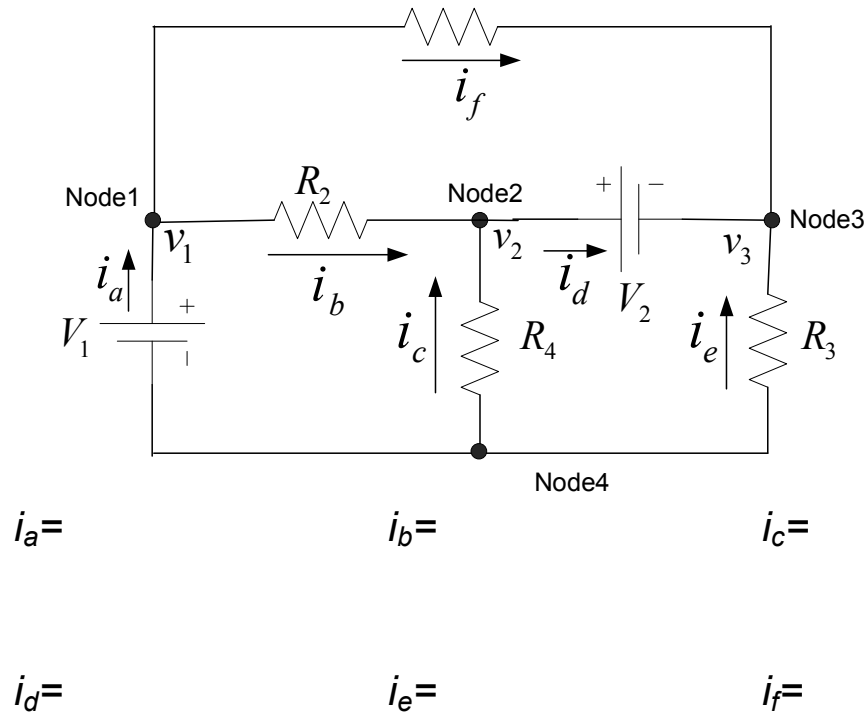- b) For the same circuit as in (a), **measure the current in each branch using the multimeter.**

(Connect the ammeter and ask the GA to check before you power up the circuit.)



**Write KCL equations for the following loops and verify that KCL is satisfied.**

Node 1:

Node 2:

Node 3:

Node 4:

Conclusion:

- c) **Measure the node voltages  $v_1$ ,  $v_2$ ,  $v_3$  with respect to ground** and note them down. (Assume Node 4 is ground.)

$$V_1 =$$

$$V_2 =$$

$$V_3 =$$

**Calculate the currents using the node voltages and the resistor values.**

$$I_a =$$

$$I_b =$$

$$I_c =$$

$$I_d =$$

$$I_e =$$

$$I_f =$$

**Conclusion:**

( Compare the calculated currents in part (c) with the measured currents in part (b).)