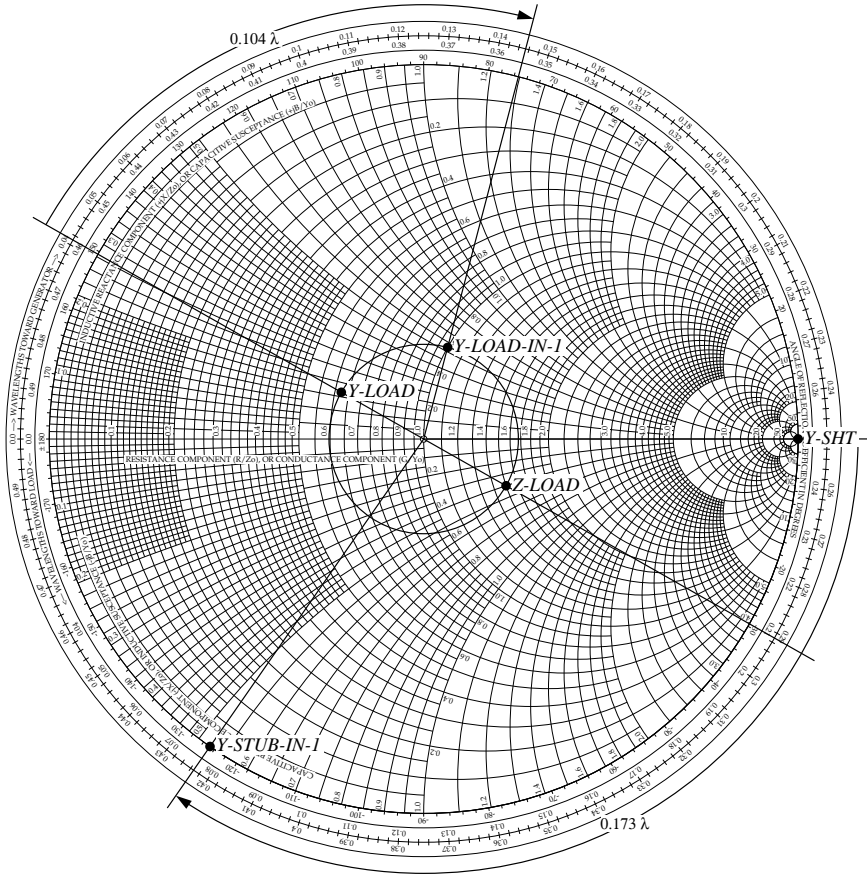


**Problem 2.68** A  $50\text{-}\Omega$  lossless line is to be matched to an antenna with  $Z_L = (75 - j20)\text{ }\Omega$  using a shorted stub. Use the Smith chart to determine the stub length and distance between the antenna and stub.




**Figure P2.68:** (a) First solution to Problem 2.68.

**Solution:** Refer to Fig. P2.68(a) and Fig. P2.68(b), which represent two different solutions.

$$z_L = \frac{Z_L}{Z_0} = \frac{(75 - j20)\text{ }\Omega}{50\text{ }\Omega} = 1.5 - j0.4$$

and is located at point *Z-LOAD* in both figures. Since it is advantageous to work in admittance coordinates,  $y_L$  is plotted as point *Y-LOAD* in both figures. *Y-LOAD* is at  $0.041\lambda$  on the WTG scale.

For the first solution in Fig. P2.68(a), point *Y-LOAD-IN-1* represents the point at which  $g = 1$  on the SWR circle of the load. *Y-LOAD-IN-1* is at  $0.145\lambda$  on the WTG scale, so the stub should be located at  $0.145\lambda - 0.041\lambda = 0.104\lambda$  from the load (or some multiple of a half wavelength further). At *Y-LOAD-IN-1*,  $b = 0.52$ , so a stub with an input admittance of  $y_{\text{stub}} = 0 - j0.52$  is required. This point is *Y-STUB-IN-1* and is at  $0.423\lambda$  on the WTG scale. The short circuit admittance is denoted by point *Y-SHT*, located at  $0.250\lambda$ . Therefore, the short stub must be  $0.423\lambda - 0.250\lambda = 0.173\lambda$  long (or some multiple of a half wavelength longer).

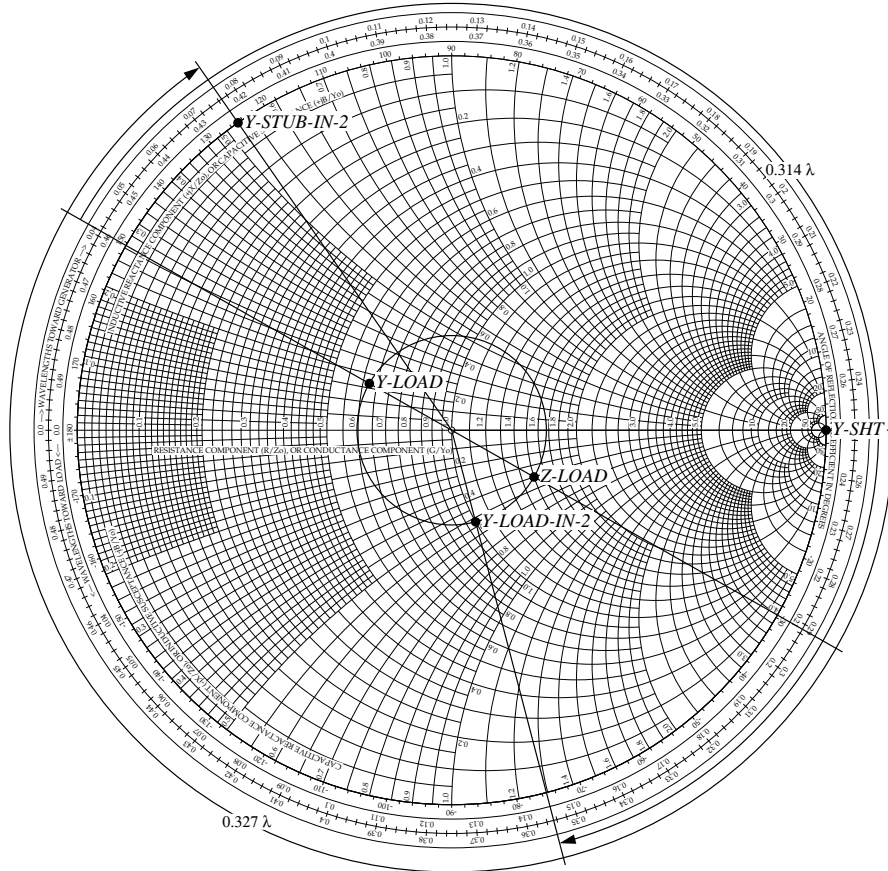

**Figure P2.68:** (b) Second solution to Problem 2.68.

For the second solution in Fig. P2.68(b), point *Y-LOAD-IN-2* represents the point at which  $g = 1$  on the SWR circle of the load. *Y-LOAD-IN-2* is at  $0.355\lambda$  on the WTG scale, so the stub should be located at  $0.355\lambda - 0.041\lambda = 0.314\lambda$  from the

load (or some multiple of a half wavelength further). At *Y-LOAD-IN-2*,  $b = -0.52$ , so a stub with an input admittance of  $y_{\text{stub}} = 0 + j0.52$  is required. This point is *Y-STUB-IN-2* and is at  $0.077\lambda$  on the WTG scale. The short circuit admittance is denoted by point *Y-SHT*, located at  $0.250\lambda$ . Therefore, the short stub must be  $0.077\lambda - 0.250\lambda + 0.500\lambda = 0.327\lambda$  long (or some multiple of a half wavelength longer).

---

## Problem 2

First normalize the load impedance to the system impedance.

$$z_L = \frac{Z_L}{Z_0} = \frac{1}{3}$$

Identify  $z_L$  on the Smith Chart.


Find  $y_L$  on the Smith Chart

Move along the SWR circle until you intersect the  $r=1$  circle at point A.


Find out the imaginary part of the admittance at point A. In this case, it's **-j1.15**. That means you an admittance of **y=j1.15** for matching.

Therefore, the required shunt impedance is
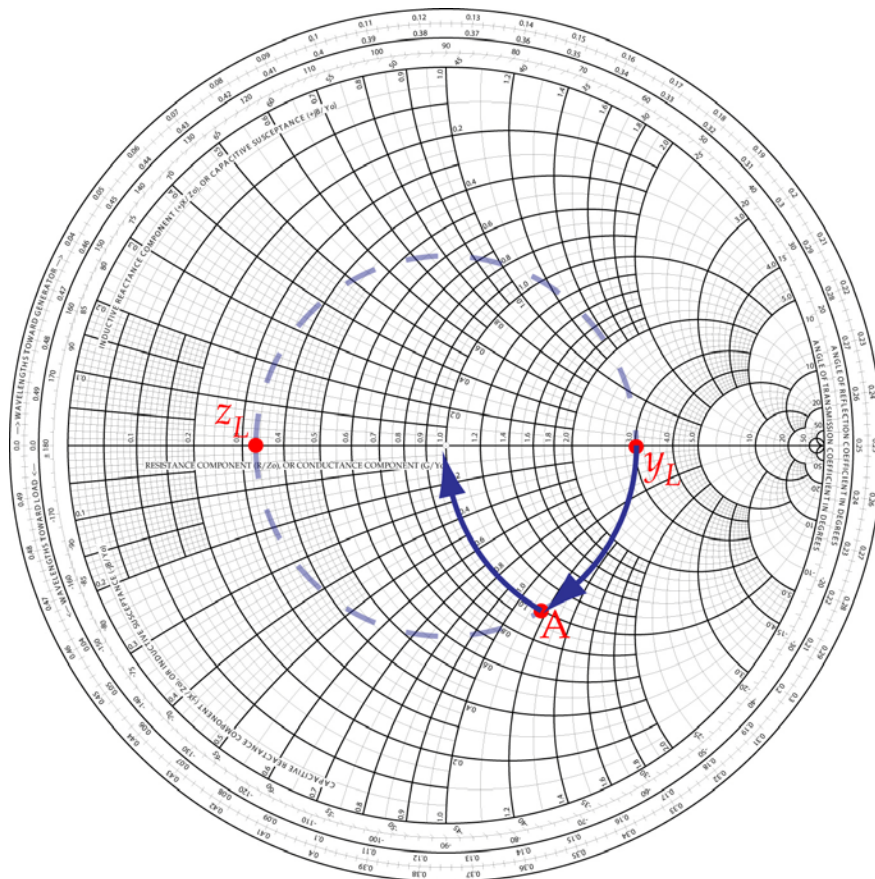
$$Z = Z_0 \frac{1}{y} = 75 \frac{1}{j1.15} = -j65.2 (\Omega)$$



**Problem 2.78** In response to a step voltage, the voltage waveform shown in Fig. P2.78 was observed at the sending end of a shorted line with  $Z_0 = 50 \, \Omega$  and  $\epsilon_r = 4$ . Determine  $V_g$ ,  $R_g$ , and the line length.

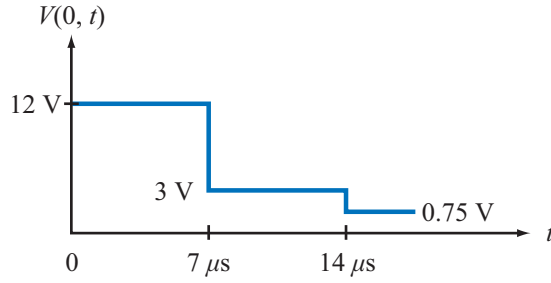

**Figure P2.78:** Voltage waveform of Problem 2.78.

**Solution:**

$$u_p = \frac{c}{\sqrt{\epsilon_r}} = \frac{3 \times 10^8}{\sqrt{4}} = 1.5 \times 10^8 \, \text{m/s},$$

$$7 \, \mu\text{s} = 7 \times 10^{-6} \, \text{s} = \frac{2l}{u_p} = \frac{2l}{1.5 \times 10^8}.$$

Hence,  $l = 525 \, \text{m}$ .

From the voltage waveform,  $V_1^+ = 12 \, \text{V}$ . At  $t = 7 \, \mu\text{s}$ , the voltage at the sending end is

$$V(z=0, t=7 \, \mu\text{s}) = V_1^+ + \Gamma_L V_1^+ + \Gamma_g \Gamma_L V_1^+ = -\Gamma_g V_1^+ \quad (\text{because } \Gamma_L = -1).$$

Hence,  $3 \, \text{V} = -\Gamma_g \times 12 \, \text{V}$ , or  $\Gamma_g = -0.25$ . From Eq. (2.153),

$$R_g = Z_0 \left( \frac{1 + \Gamma_g}{1 - \Gamma_g} \right) = 50 \left( \frac{1 - 0.25}{1 + 0.25} \right) = 30 \, \Omega.$$

Also,

$$V_1^+ = \frac{V_g Z_0}{R_g + Z_0}, \quad \text{or} \quad 12 = \frac{V_g \times 50}{30 + 50},$$


which gives  $V_g = 19.2 \, \text{V}$ .

---

**Problem 2.80** A generator circuit with  $V_g = 200 \text{ V}$  and  $R_g = 25 \Omega$  was used to excite a  $75\text{-}\Omega$  lossless line with a rectangular pulse of duration  $\tau = 0.4 \mu\text{s}$ . The line is  $200 \text{ m}$  long, its  $u_p = 2 \times 10^8 \text{ m/s}$ , and it is terminated in a load  $R_L = 125 \Omega$ .

- (a) Synthesize the voltage pulse exciting the line as the sum of two step functions,  $V_{g_1}(t)$  and  $V_{g_2}(t)$ .
- (b) For each voltage step function, generate a bounce diagram for the voltage on the line.
- (c) Use the bounce diagrams to plot the total voltage at the sending end of the line.

**Solution:**

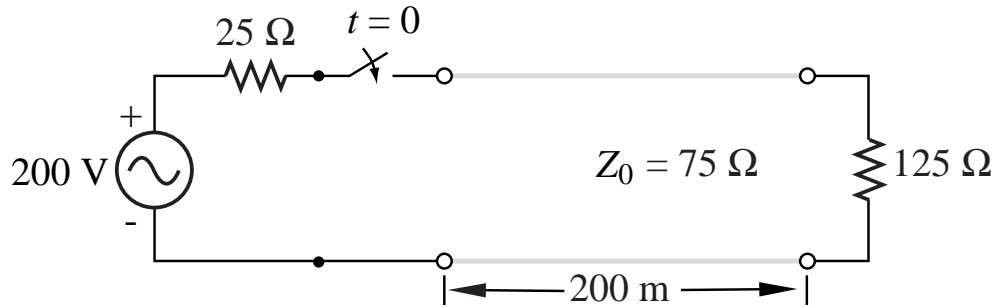

**Figure P2.80:** (a) Circuit for Problem 2.80.

- (a) pulse length  $= 0.4 \mu\text{s}$ .

$$V_g(t) = V_{g_1}(t) + V_{g_2}(t),$$

with


$$V_{g_1}(t) = 200U(t) \quad (\text{V}),$$

$$V_{g_2}(t) = -200U(t - 0.4 \mu\text{s}) \quad (\text{V}).$$

- (b)

$$T = \frac{l}{u_p} = \frac{200}{2 \times 10^8} = 1 \mu\text{s}.$$

We will divide the problem into two parts, one for  $V_{g_1}(t)$  and another for  $V_{g_2}(t)$  and then we will use superposition to determine the solution for the sum. The solution for  $V_{g_2}(t)$  will mimic the solution for  $V_{g_1}(t)$ , except for a reversal in sign and a delay by  $0.4 \mu\text{s}$ .

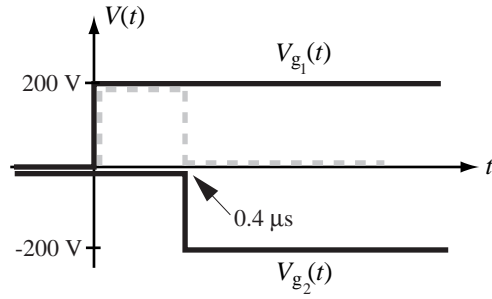

**Figure P2.80:** (b) Solution of part (a).

For  $V_{g1}(t) = 200U(t)$ :


$$\Gamma_g = \frac{R_g - Z_0}{R_g + Z_0} = \frac{25 - 75}{25 + 75} = -0.5,$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{125 - 75}{125 + 75} = 0.25,$$

$$V_1^+ = \frac{V_1 Z_0}{R_g + Z_0} = \frac{200 \times 75}{25 + 75} = 150 \text{ V},$$

$$V_\infty = \frac{V_g Z_L}{R_g + Z_L} = \frac{200 \times 125}{25 + 125} = 166.67 \text{ V}.$$


(i)  $V_1(0, t)$  at sending end due to  $V_{g1}(t)$ :

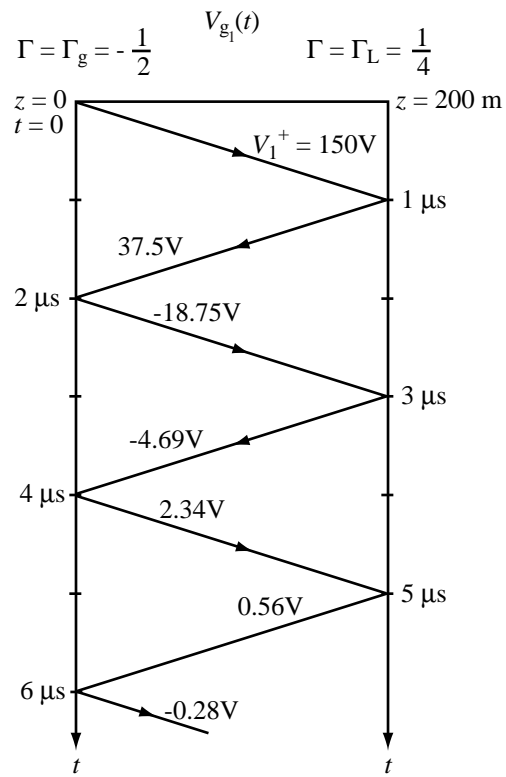

**Figure P2.80:** (c) Bounce diagram for voltage in reaction to  $V_{g_1}(t)$ .

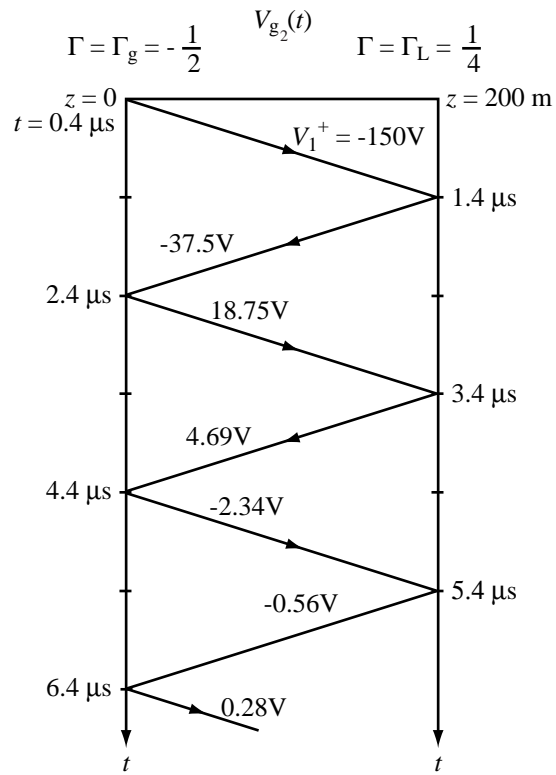(ii)  $V_2(0, t)$  at sending end due to  $V_{g_2}(t)$ :

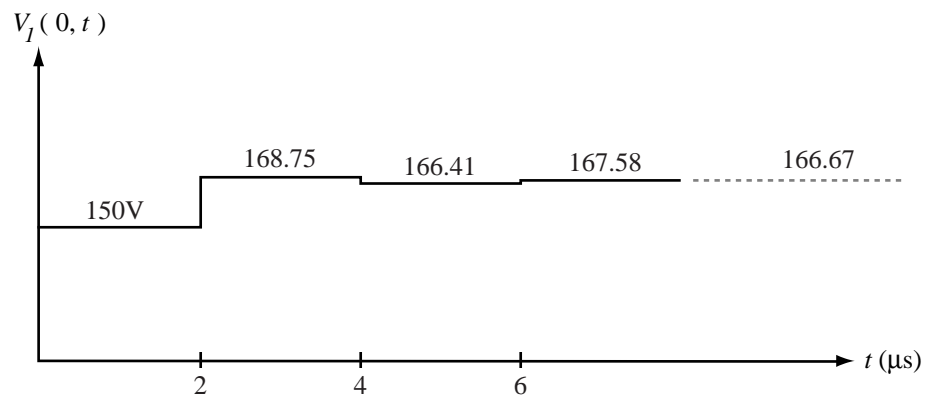





**Figure P2.80:** (d) Bounce diagram for voltage in reaction to  $V_{g_2}(t)$ .

(b)

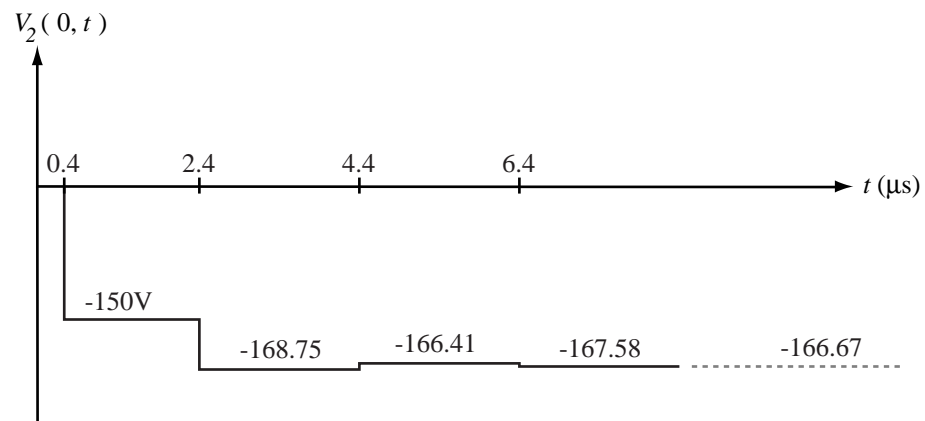- (i)  $V_1(0, t)$  at sending end due to  $V_{g_1}(t)$ : see Fig. P2.80(e).
- (ii)  $V_2(0, t)$  at sending end: see Fig. P2.80(f).

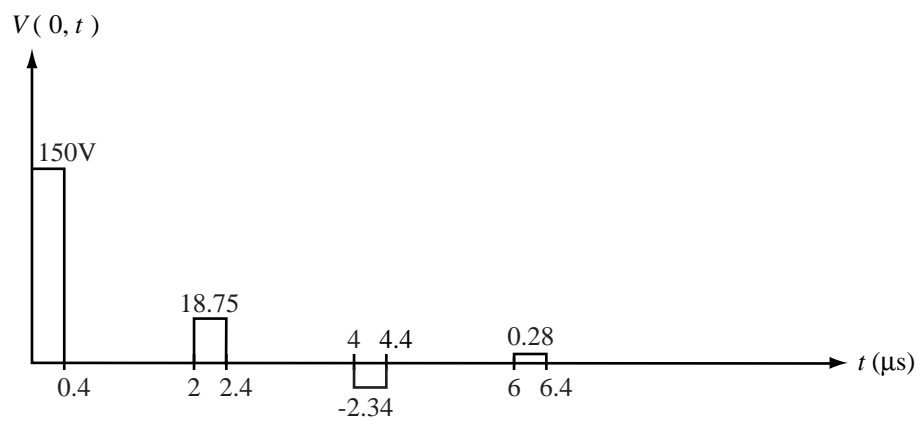


**Figure P2.80:** (e)  $V_1(0, t)$ .



**Figure P2.80:** (f)  $V_2(0, t)$ .

(iii) Net voltage  $V(0, t) = V_1(0, t) + V_2(0, t)$ : see Fig. P2.80(g).



**Figure P2.80:** (g) Net voltage  $V(0, t)$ .

---


**Problem 2.81** For the circuit of Problem 2.80, generate a bounce diagram for the current and plot its time history at the middle of the line.

**Solution:** Using the values for  $\Gamma_g$  and  $\Gamma_L$  calculated in Problem 2.80, we reverse their signs when using them to construct a bounce diagram for the current.


$$I_1^+ = \frac{V_1^+}{Z_0} = \frac{150}{75} = 2 \text{ A},$$

$$I_2^+ = \frac{V_2^+}{Z_0} = \frac{-150}{75} = -2 \text{ A},$$

$$I_\infty^+ = \frac{V_\infty}{Z_L} = 1.33 \text{ A}.$$

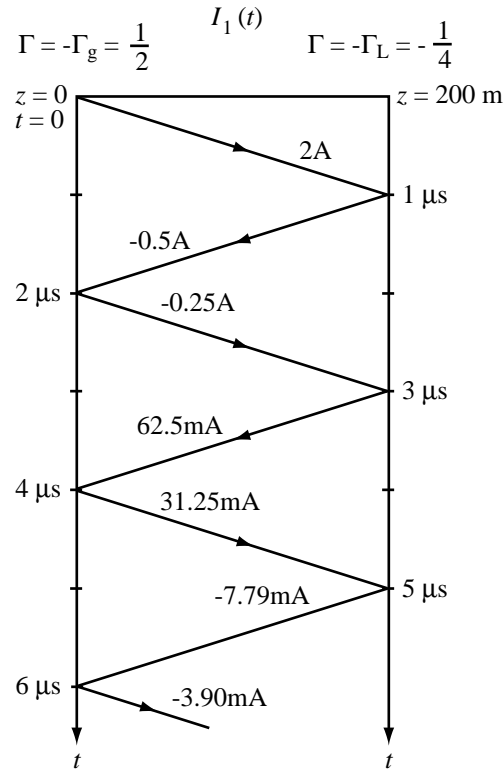


**Figure P2.81:** (a) Bounce diagram for  $I_1(t)$  in reaction to  $V_{g_1}(t)$ .

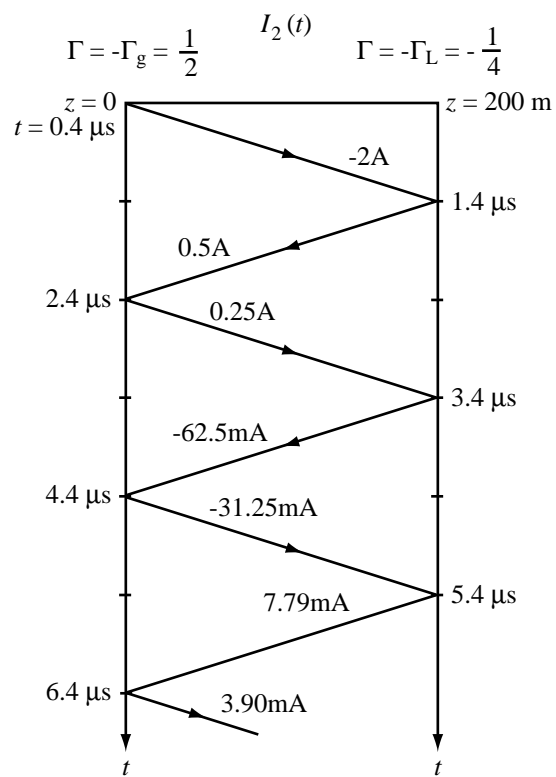


**Figure P2.81:** (b) Bounce diagram for current  $I_2(t)$  in reaction to  $V_{g_2}(t)$ .

(i)  $I_1(l/2, t)$  due to  $V_{g1}(t)$ :

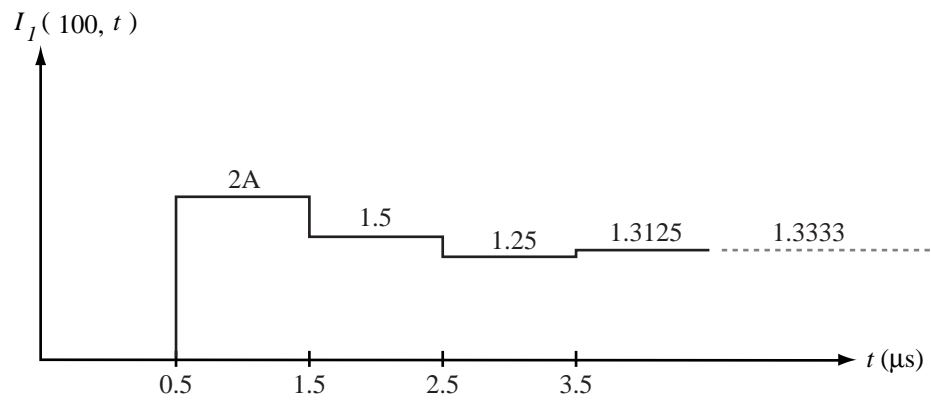


**Figure P2.81:** (c)  $I_1(l/2, t)$ .

(ii)  $I_2(l/2, t)$  due to  $V_{g2}(t)$ :

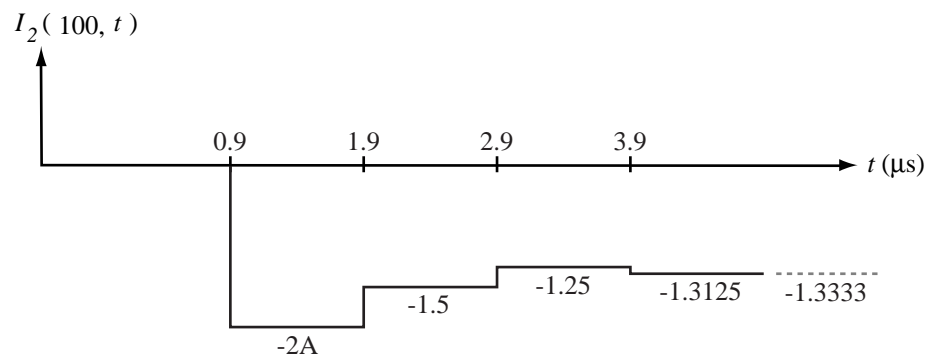

**Figure P2.81:** (d)  $I_2(l/2, t)$ .

(iii) Net current  $I(l/2, t) = I_1(l/2, t) + I_2(l/2, t)$ :

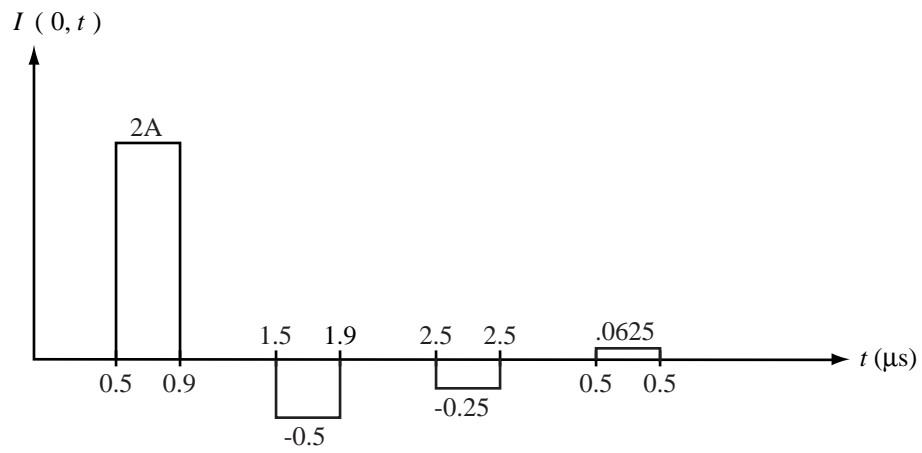

**Figure P2.81:** (e) Total  $I(l/2, t)$ .

---