

# EEC 130A: Homework 4

Due: 3:30 pm, Feb. 7th, 2013

1. (4 points) (FAE P2.68) **Single-stub Matching** A  $50\text{-}\Omega$  lossless line is to be matched to an antenna with  $Z_L = (75 - j20)\text{ }\Omega$  using a shorted stub. Use the Smith chart to determine the stub length and distance between the antenna and stub.
2. (4 points) (FAE P2.74) A  $25\text{-}\Omega$  antenna is connected to a  $75\text{-}\Omega$  lossless transmission line. Reflections back toward the generator can be eliminated by placing a shunt **reactance**  $Z$  at a distance  $l$  from the load (Fig. 1). Determine the values of  $Z$  and  $l$ .

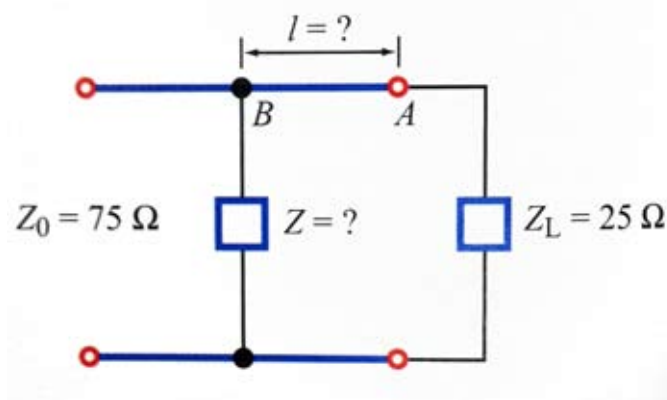


Figure 1: Circuit for Problem 2.

3. (4 points) (FAE P2.78) In response to a step voltage, the voltage waveform shown in Fig. 2 was observed at the sending end of a shorted line with  $Z_0 = 50\text{ }\Omega$  and  $\epsilon_r = 4$ . Determine  $V_g$ ,  $R_g$ , and the line length.

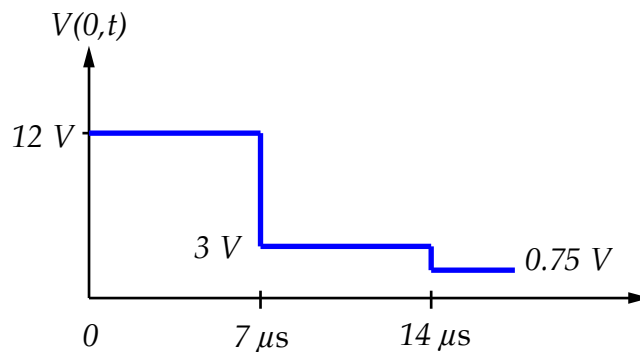


Figure 2: Voltage waveform of Problem 3.

4. (4 points) (FAE P2.80) A generator circuit with  $V_g = 200\text{ V}$  and  $R_g = 25\text{ }\Omega$  was used to excite a  $75\text{-}\Omega$  lossless line with a rectangular pulse of duration  $\tau = 0.4\text{ }\mu\text{s}$ . The line is  $200\text{ m}$  long, its  $u_p = 2 \times 10^8\text{ m/s}$ , and it is terminated in a load  $R_L = 125\text{ }\Omega$ .

- (a) Synthesize the voltage pulse exciting the line as the sum of two step functions,  $V_{g1}(t)$  and  $V_{g2}(t)$ .
  - (b) For each voltage step function, generate a bounce diagram for the voltage on line.
  - (c) Use the bounce diagrams to plot the total voltage at the sending end of the line.
5. (4 points) (FAE P2.81) For the circuit of Problem 2 (FAE P2.80), generate a bounce diagram for the current and plot its time history at the middle of the line.